

Experiment 8 Handout  
ECE203 SS25

Names: Xiangbo Cai

Answer questions and turn these pages in to your TA at the end of your lab period.

Section 5.2

10. Why isn't there any current? *There is no load part, only one voltage*

13. Node 2 voltage = *59.5489 V*

14. Power =  $I^2 R = (1.8045 \cdot 10^{-4})^2 \cdot (10^6) = 32.56 \text{ mW}$

Will a 0.125W resistor work here? *Yes.  $32.56 \text{ mW} < 125 \text{ mW}$*

15. 330kOhm current  *$1.8045 \times 10^{-4} \text{ A}$*

Is it the same as the 1MOhm? *It is the same*

Should it be? *Yes. Because they are in series*

18. 330kOhm current  *$1.445 \times 10^{-4} \text{ A}$*

How does it compare to above?

*It decrease*

How does this explain the change in voltage at node 2?

*Because capacitor stores some charge*

19. Does the capacitance matter? Explain.

*No. It does not affect. Because it's DC. open circuit*

22. Does the 10MOhm probe make a difference? Why or why not?

*Yes. It makes difference. It now  $V(2) = 58.107 \text{ V}$ . It drain less*

Section 5.3

9. Explain the shape difference

*Node 2 connect to CS & RS. Charging need a time  $\tau = RC$ . So  $V(2)$*

10. Time constant estimation  *$2.5 \mu\text{s}$*

*need some time to*

13. Average value and width of the current pulse.

*achieve. It curved a bit.*

Estimated change in voltage.

*Average:  $100 \mu\text{A}$*

*width:  $6 \mu\text{s}$*

*$V(1)$  is a sharp leap.*

$$\Delta V = \frac{I}{C} \cdot \Delta t = \frac{100 \mu\text{A}}{10 \text{ pF}} \cdot 6 \mu\text{s} = 60 \text{ V}$$

**Experiment 8 Handout**  
**ECE203 SS25**

14. How would we charge this capacitor faster? What part of the circuit would we change?

less resistance Smaller  $R_1$ ,  $R_2$  / Smaller Capacitor.

15. Estimated cutoff frequency  $f_c = 1/(2\pi \cdot \text{time constant})$

$$f_c = \frac{1}{2\pi(2.5\mu)} = 63 \text{ KHz}$$

Would this work with a 50kHz square wave?

Yes.  $50 \text{ KHz} < 63 \text{ KHz}$ , but some parts might not work well.

What about a 60Hz sinusoid?

Yes  $60 \text{ Hz} \ll 63 \text{ KHz}$ . It will work well

20. RMS voltage =  $58.17 \text{ V}$

21. Is there a phase delay or amplitude change?

Yes.  $1.8 \text{ V}$  amplitude change

Section 5.4

5. Are nodes 2 and 3 the same voltage? Should they be?

Yes. They should be because we are defining ideal op-amp

6. Are nodes 1 and 4 the same voltage? Should they be?

No. Similar but not same. Because phase and filter, they should not be

Section 5.5

5. Did your AC sweep work correctly?

Yes

Section 5.6

7. Did you get the odd behavior you saw in the lab?

Yes