

# Post Lab of.

Frequency	$V_{out} (V_{rms})$	Phase
3.4 Hz	30.7 mV	85°
34 Hz	294.4 mV	82.3°
340 Hz	2.09 V	42°
3.4 kHz	2.95 V	0°
34 kHz	2.05 V	-49°
340 kHz	267.4 mV	-113.9°

$$V_{in} = 3 V_{rms} \quad d\beta = 20 \log_{10} \frac{V_{out}}{V_{in}}$$

$$d\beta = 20 \log_{10} \frac{30.7}{3} \times 10^{-3} = -39.79$$



$$d\beta = 20 \log_{10} \frac{294.4}{3} \times 10^{-3} = -20.16$$

$$d\beta = 20 \log_{10} \frac{2.09}{3} = -3.13$$

$$d\beta = 20 \log_{10} \frac{2.95}{3} = -0.146$$

$$d\beta = 20 \log_{10} \frac{2.05}{3} = -3.3$$
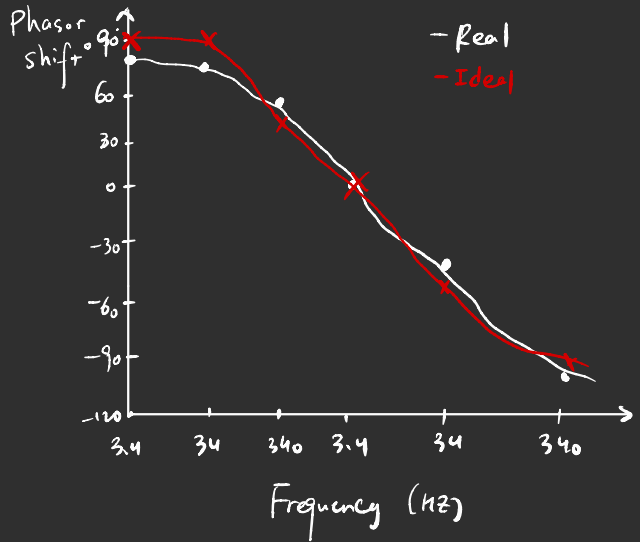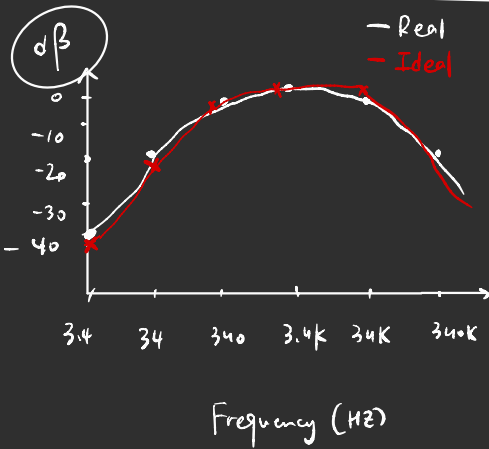
$$d\beta = 20 \log_{10} \frac{267.4}{3} \times 10^{-3} = -20.99$$



Explain: No matter the resistor, capacitor, or op-amp, they are all non-ideal circuit component. therefore, the result will always having some error.

Extra Credit: Even though the function generator was initially set to output  $3 V_{rms}$ , once the filter is connected, its impedance interacts with finite output impedance of the function generator. This interaction forms a voltage divider, which reduce the voltage that actually appears at ch1. Importantly, this drop is not due to the scope's bandwidth or any parasitic effect. — it's solely because the filter's input impedance combined with the generator's output impedance, divides the voltage, causing the measured value on ch1 to be less than  $3 V_{rms}$ .