1.  $3600 \text{ rpm} = \frac{3600}{60} \text{ rps} = 60 \text{ rps}$ 

$$f_{HPC} = 50 \text{ Hz.}$$
  $f_{LPC} = 70 \text{ Hz.}$  Also  $f = \frac{1}{2\pi RC}$  Suppose  $R = 33 \text{ k}\Omega$ 

$$C_{HP} = \frac{1}{2\pi \cdot 50.33 \text{k}} = 0.96 \text{ \muF}$$
  $C_{LP} = \frac{1}{2\pi \cdot 70.33 \text{k}} = 0.68 \text{ \muF}$ 

$$C_{\mu\rho} = \frac{1}{2\pi \cdot 50.33 \text{k}} = 0.96 \,\mu\text{F}$$
  $C_{L\rho} = \frac{1}{2\pi \cdot 70.33 \text{k}} = 0.68 \,\mu\text{F}$