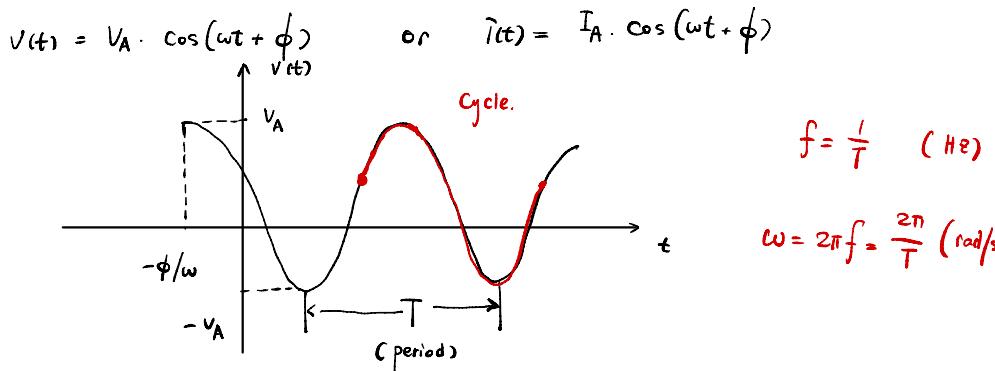


# ECE 202

Xiangbo Cai

## Chapter 8 : Sinusoids Steady-state response.

### 8.1 Sinusoids and phasors



Conversion between radian & degrees :  $x^\circ = \left(\frac{180}{\pi}\right) \times y \rightsquigarrow$  in radians

$V_A$  &  $I_A$   $\Rightarrow$  "Amplitude"       $2V_A$  &  $2I_A$   $\Rightarrow$  "peak-to-peak amplitude"


\*  $-\phi$  ( $\phi > 0$ ) the graph shift right ;  $+\phi$  ( $\phi > 0$ ) the graph shift left

### Complex algebra

① Euler's Formula.  $e^{j\theta} = \cos\theta + j\sin\theta$ .  $j \stackrel{\Delta}{=} \sqrt{-1}$ .

② Complex number. a. rectangular form.  $n = a + jb$

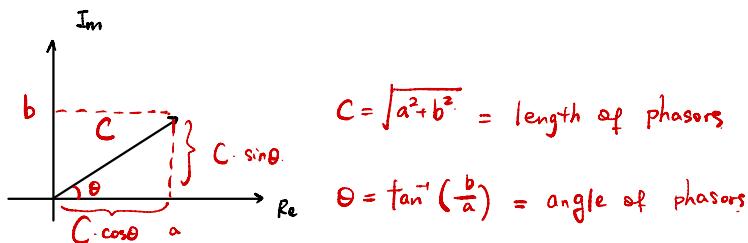b. polar form.  $n = C \cdot e^{j\theta} = C \angle \theta$



$\cos\theta = \text{Re}\{e^{j\theta}\}$

$\sin\theta = \text{Im}\{e^{j\theta}\}$

phasor transform:

$$v(t) = V_A \cos(\omega t + \phi) = V_A \cdot \operatorname{Re} \{ e^{j(\omega t + \phi)} \} = V_A \cdot \operatorname{Re} \{ e^{j\omega t} \cdot e^{j\phi} \}$$

$$= \operatorname{Re} \left\{ \underbrace{(V_A \cdot e^{j\phi})}_{\text{phasors}} e^{j\omega t} \right\} \xrightarrow{\text{Phasor: } \vec{V} = V_A \cdot e^{j\phi}} v(t) = \operatorname{Re} \{ \vec{V} \cdot e^{j\omega t} \}$$


Back transform:

$$\begin{aligned} v(t) &= \operatorname{Re} \{ \vec{V} \cdot e^{j\omega t} \} = \operatorname{Re} \{ V_A \cdot e^{j\phi} \cdot e^{j\omega t} \} = \operatorname{Re} \{ V_A \cdot e^{j(\omega t + \phi)} \} = \operatorname{Re} \{ V_A (\cos(\omega t + \phi) + j \sin(\omega t + \phi)) \} \\ &= \cos(\omega t + \phi) \quad \Rightarrow \quad v(t) = \cos(\omega t + \phi) \end{aligned}$$

(A) Addition of two complex number

$$\vec{x}_1 + \vec{x}_2 \quad \vec{x}_1 = 10 \angle -45^\circ \quad \vec{x}_2 = 5 \angle 30^\circ$$

< Solution >:

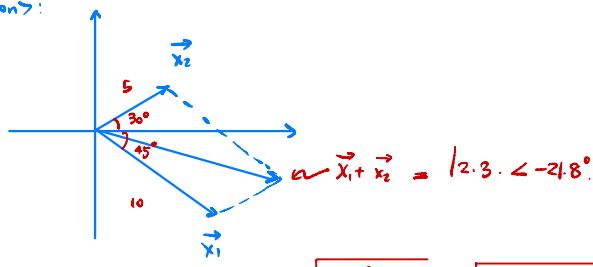

$$C = \sqrt{(k \cos \theta)^2 + (c \sin \theta)^2} = \sqrt{(11.4)^2 + (-4.57)^2} = 12.28$$

$$\theta = \tan^{-1} \left( \frac{-4.57}{11.4} \right) = -21.84^\circ$$

$$\begin{aligned} \vec{x}_1 &= 10 \cos(-45^\circ) + j \cdot 10 \sin(-45^\circ) \\ &= 7.07 - j \cdot 7.07 \end{aligned}$$

$$\begin{aligned} \vec{x}_2 &= 5 \cos(30^\circ) + j \cdot 5 \sin(30^\circ) \\ &= 4.33 + j \cdot 2.5 \end{aligned}$$

$$\begin{aligned} \vec{x}_1 + \vec{x}_2 &= (7.07 - j \cdot 7.07) + (4.33 + j \cdot 2.5) \\ &= (7.07 + 4.33) + j(-7.07 + 2.5) \\ &= \underbrace{11.4}_{C \cdot \cos \theta} - j \underbrace{4.57}_{C \cdot \sin \theta} \end{aligned}$$

(B) Multiplication of two Complex number. ( Division just reverse)

$$\vec{x}_1 \cdot \vec{x}_2 \quad \vec{x}_1 = 7 \angle 60^\circ \quad \vec{x}_2 = 11 \angle -85^\circ$$

$$\vec{x}_1 \cdot \vec{x}_2 = (7 \cdot e^{j(60^\circ)}) \cdot (11 \cdot e^{j(-85^\circ)})$$

$$= 77 e^{j(60-85)^\circ}$$

$$= 77 e^{-j(25)^\circ}$$

$$= 77 \angle -25^\circ$$

Product magnitude  
addition angle

$$\left\{ \begin{array}{l} 7 \times 11 = 77 \\ 60 - 85 = -25 \end{array} \right.$$

## 8.2 Phasor Circuit analysis

(A) Connection Constraints in phasor form.

$$(1) \text{ KVL} \quad (\text{rise} = \text{drop}) \quad \vec{V}_1 + \vec{V}_2 + \dots + \vec{V}_j = \vec{V}_k + \vec{V}_l + \dots + \vec{V}_N$$

$$\text{Proof: If } V_1 \cos(\omega t + \phi_1) + V_2 \cos(\omega t + \phi_2) + \dots + V_j \cos(\omega t + \phi_j)$$

$$= V_k \cos(\omega t + \phi_k) + V_l \cos(\omega t + \phi_l) + \dots + V_N \cos(\omega t + \phi_N)$$

$$\Rightarrow \operatorname{Re}\{V_1 e^{j\phi_1} e^{j\omega t}\} + \operatorname{Re}\{V_2 e^{j\phi_2} e^{j\omega t}\} + \dots + \operatorname{Re}\{V_j e^{j\phi_j} e^{j\omega t}\}$$

$$= \operatorname{Re}\{V_k e^{j\phi_k} e^{j\omega t}\} + \operatorname{Re}\{V_l e^{j\phi_l} e^{j\omega t}\} + \dots + \operatorname{Re}\{V_N e^{j\phi_N} e^{j\omega t}\}$$


$$\Rightarrow \operatorname{Re}\{(V_1 e^{j\phi_1} + V_2 e^{j\phi_2} + \dots + V_j e^{j\phi_j}) e^{j\omega t}\} = \operatorname{Re}\{(V_k e^{j\phi_k} + V_l e^{j\phi_l} + \dots + V_N e^{j\phi_N}) e^{j\omega t}\}$$

$$\therefore \vec{V}_1 + \vec{V}_2 + \dots + \vec{V}_j = \vec{V}_k + \vec{V}_l + \dots + \vec{V}_N$$

$$(B) \text{ KCL} \quad (\text{Input} = \text{Output}) \quad \vec{I}_1 + \vec{I}_2 + \dots + \vec{I}_j = \vec{I}_k + \vec{I}_l + \dots + \vec{I}_N \quad (\text{Same})$$

$$\operatorname{Re}\{C_1 < \theta_1\} + \operatorname{Re}\{C_2 < \theta_2\}$$
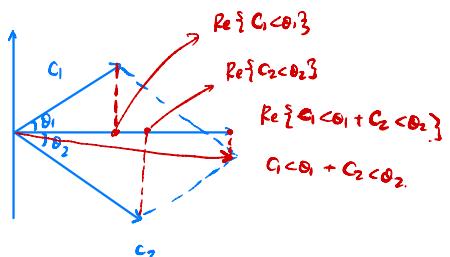
$$= \operatorname{Re}\{C < \theta_1 + C < \theta_2\}$$



(B) Device constraints in phasors form.


(1) Resistance



$$v(t) = R [I_A \cos(\omega t + \phi)] = RI_A \cdot \cos(\omega t + \phi) = \operatorname{Re} \{ RI_A e^{j(\omega t + \phi)} \}$$


$$= \operatorname{Re} \{ \underbrace{RI_A e^{j\phi}}_{\vec{V}} \cdot e^{j\omega t} \} \quad \vec{V} = RI_A e^{j\phi} = RI_A \angle \phi \quad \vec{I} = I_A \angle \phi$$

$\therefore \boxed{\vec{V} = R \vec{I}}$

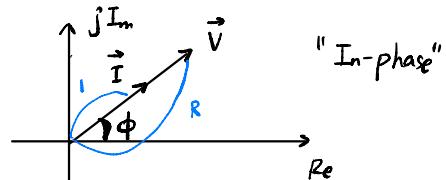

phasor diagram of a resistor

(2) Inductance

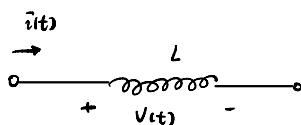


$$i(t) = I_A \cos(\omega t + \phi) \quad v(t) = L \frac{di(t)}{dt} = L (-\omega) I_A \sin(\omega t + \phi) = -L\omega I_A \sin(\omega t + \phi)$$

$$\therefore v(t) = -\omega L I_A \cos(\omega t + \phi - 90^\circ) = \operatorname{Re} \{ -\omega L I_A e^{j(\omega t + \phi - 90^\circ)} \} = \operatorname{Re} \{ -\omega L I_A e^{j\phi} e^{j(-90^\circ)} e^{j\omega t} \}$$

$$e^{j(-90^\circ)} = \cos(-90^\circ) + j \sin(-90^\circ) = -j \Rightarrow v(t) = \operatorname{Re} \{ \underbrace{j\omega L I_A e^{j\phi}}_{\vec{V}} e^{j\omega t} \}$$

$$\therefore \vec{V} = j\omega L \cdot I_A \cdot e^{j\phi}$$
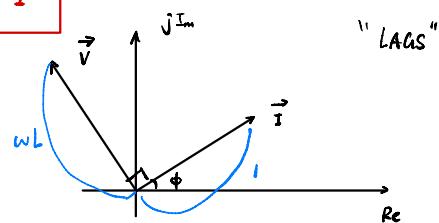
$$= j\omega L \cdot I_A \angle \phi \quad \Rightarrow \quad \boxed{\vec{V} = j\omega L \cdot \vec{I}}$$




$$\text{As } e^{j(-90^\circ)} = \cos(-90^\circ) + j \sin(-90^\circ) = -j = 1 \angle -90^\circ$$

$$\therefore \vec{V} = (\omega L \angle -90^\circ) \cdot I_A \angle \phi = (\omega L I_A) \angle (\phi + 90^\circ)$$

phasor diagram of Inductance

### (3) Capacitance

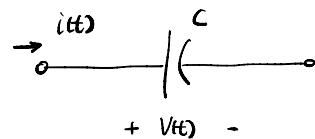

$$V(t) = V_A \cos(\omega t + \phi) \quad i(t) = C \frac{dV(t)}{dt} = C V_A (-\omega) \sin(\omega t + \phi) = -\omega C V_A \sin(\omega t + \phi)$$

$$\Rightarrow \bar{i}(t) = -\omega C V_A \cos(\omega t + \phi - 90^\circ) = \operatorname{Re} \{ -\omega C V_A e^{j(\omega t + \phi - 90^\circ)} \} = \operatorname{Re} \{ \underbrace{j\omega C V_A e^{j\phi}}_{\text{phasor}} \cdot e^{j\omega t} \}$$

$$\Rightarrow \bar{i}(t) = \operatorname{Re} \{ j\omega C V_A e^{j\phi} \cdot e^{j\omega t} \} \Rightarrow \vec{I} = j\omega C V_A e^{j\phi} = j\omega C \cdot \vec{V}$$





$$\Rightarrow \boxed{\vec{V} = \frac{1}{j\omega C} \vec{I}}$$

$$\Rightarrow \vec{V} = \frac{-j}{\omega C} \vec{I}$$

As  $e^{j(-90^\circ)} = \cos(-90^\circ) + j \sin(-90^\circ) = -j \Rightarrow <-90^\circ$

$$\Rightarrow \vec{V} = \left( \frac{1}{\omega C}, <-90^\circ \right) (I_A \angle \phi) = \frac{1}{\omega C} I_A \angle \phi - 90^\circ$$

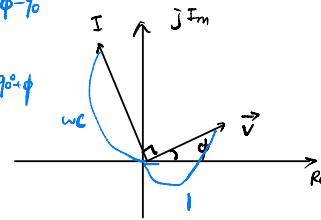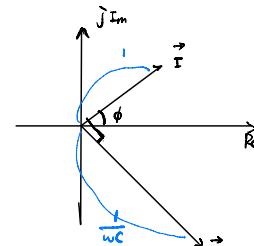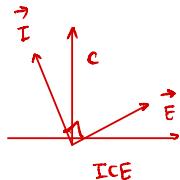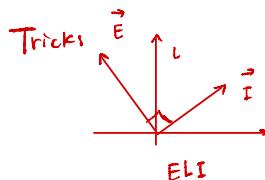Another:  $\vec{I} = (j\omega C) \vec{V} = (\omega C, <90^\circ) (V_A \angle \phi) = \omega C V_A \angle 90^\circ + \phi$



phasor diagram of Capacitor

(c).

Summarize: The Impedance - Admittance Concept.

(1)  $\vec{V} = Z \cdot \vec{I}$  (impedance)

For resistor.  $\vec{V} = R \vec{I}$ .

$Z = R$

(2)  $\vec{I} = Y \vec{V}$  (admittance)

$Y = \frac{1}{R} = G$

For inductance  $\vec{V} = j\omega L \vec{I}$

$Z = j\omega L$

$Y = \frac{1}{j\omega L} = -j \frac{1}{\omega L}$


For capacitance  $\vec{V} = \frac{1}{j\omega C} \vec{I} = \frac{-j}{\omega C} \vec{I}$

$Z = -j \frac{1}{\omega C}$

$Y = j\omega C$

## 8.3 Basic circuit analysis with phasors


### (A) Series equivalence of impedance

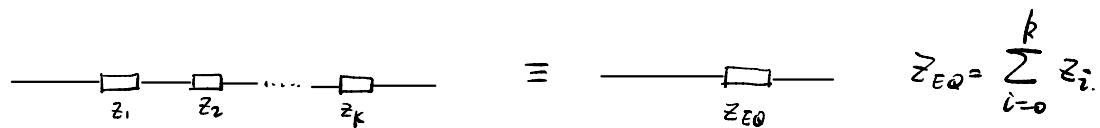

Proof:  $\vec{V}_S = \vec{V}_1 + \vec{V}_2 + \dots + \vec{V}_k = I_s z_1 + I_s z_2 + \dots + I_s z_k = I_s (z_1 + z_2 + \dots + z_k) \triangleq I_s Z_{EQ}$

$$Z_{EQ} = R + jX \quad R \text{ is resistance.}$$

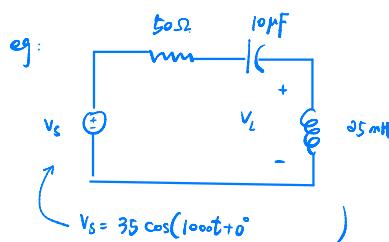positive  $X \rightarrow$  inductive reactance  
negative  $X \rightarrow$  capacitive reactance



$$\begin{aligned} & \vec{V}_S = 35 \angle 0^\circ \quad \omega = 1000 \\ & R = 50 \Omega \quad Z_L = j(1k)(25m) = j25 \\ & Z_C = -j \frac{1}{(1k)(10\mu)} = -j \cdot 100 \end{aligned}$$

$$\Rightarrow Z_{EQ} = 50 - j75$$

$$= 90.14 \angle -56.31^\circ$$

$$\vec{I}_s = \frac{\vec{V}_S}{Z_{EQ}} = \frac{35 \angle 0^\circ}{90.14 \angle -56.31^\circ} = 0.388 \angle 56.31^\circ$$

$$\Rightarrow i_s(t) = 388m \cos(1kt + 56.31^\circ) A$$

$$\vec{V}_L = (j25) \cdot \vec{I}_s = (25 \angle 90^\circ) (0.388 \angle 56.31^\circ) = 9.707 \angle 146.31^\circ$$

$$V_L(t) = 9.707 \cos(1kt + 146.31^\circ) V$$

Voltage divide rule:  $\vec{V}_j = \vec{V}_S \cdot \frac{Z_j}{Z_1 + Z_2 + \dots + Z_j}$

### (B) parallel equivalence and circuit division


(1) parallel equivalence.  $Z_{EQ} = \frac{1}{Y_{EQ}} = \frac{1}{y_1 + y_2 + \dots + y_k} = \frac{1}{\frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_k}}$

(2) admittance  $Y_{EQ} = G + jB$        $G$  is conductance and  $B$  is susceptance

(3) Current divide rule: (parallel circuit)

$$\vec{I}_j = \vec{I}_s \cdot \frac{y_j}{y_1 + y_2 + \dots + y_k}$$

SPICE Example:

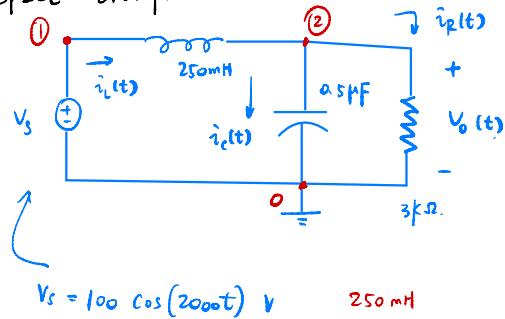

$$\vec{V}_S = 100 \angle 0^\circ$$

$$\vec{Z}_L = j\omega L = j(2000)(250m) = j500\Omega$$

$$\vec{Z}_C = -j\frac{1}{\omega C} = -j\frac{1}{(2000)(0.5\mu)} = -j1000\Omega$$

$$\vec{Z}_{EQ} = \vec{Z}_L + \frac{\vec{Z}_C \cdot R}{\vec{Z}_C + R} = j500 + \frac{(j1000)(3k)}{3k - j1000}$$

$$= 500 \angle -53.13^\circ$$

$$\vec{I}_L = \frac{\vec{V}_S}{\vec{Z}_{EQ}} = \frac{100 \angle 0^\circ}{500 \angle -53.13^\circ} = 200m \angle 53.13^\circ$$

$$\vec{I}_C = \frac{3k}{3k - j1000} \cdot 200m \angle 53.13^\circ = 189.71m \angle 71.565^\circ$$

$$\Rightarrow \vec{I}_R = \vec{I}_L - \vec{I}_C = 200m \angle 53.13^\circ - 189.71m \angle 71.565^\circ = 63.25m \angle -18.435^\circ$$

$$\text{By Ohm law: } \vec{V}_o = \vec{I}_R \cdot R = (63.25m \angle -18.435^\circ) \cdot (3k) = 189.75 \angle -18.435^\circ$$

$$\vec{i}_L(t) = 200m \cos(2kt + 53.13^\circ) A$$


$$\vec{i}_C(t) = 189.71m \cos(2kt + 71.565^\circ) A$$

$$\vec{i}_R(t) = 63.25m \cos(2kt - 18.435^\circ) A \quad V_o(t) = 189.75m \cos(2kt - 18.435^\circ) V$$

EXAMPLE 8.10  
 $f = \frac{2000}{2\pi}$  → DELAY → DAMPING FACTOR  
 VS 1 0 SIN (0 100 318.31 0 0 90)  
 L 1 2 250M ↑  $V_A$  ↑ PHASE SHIFT  
 C 2 0 0.5U ↑ CEILING STEP  
 R 2 0 3K AVE  
 .PROBE  
 .TRAV 94.25U 18.845M 0 94.25U  
 .END  
 $\frac{18.845M}{200} \rightarrow 6 \text{ CYCLES} = 6 \cdot \frac{1}{318.31}$   
 ↴ MINIMUM PLOTTED POINTS

Voltage: N+ → N-


Current: tail → head

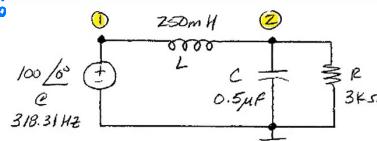

X-Axis points are:  
 $318.31 \cdot 10^{0/200}, 318.31 \cdot 10^{1/200}$   
 ....  $318.31 \cdot 10^{200/200}$

MAGNITUDE  
 EXAMPLE 8.10  
 VS 1 0 AC 100 0 ← PHASE (DEFAULT IS 0°)  
 I 1 2 250M  
 C 2 0 0.5U  
 R 2 0 3K  
 .PROBE  
 .AC DEC 200 318.31 3.1831K ← STOP FREQ.  
 .END  
 ↴ POINTS/DECade  
 SWEEP IN DECADES

Resonance:

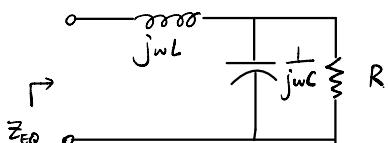

$$Z_{RC} = \frac{R \cdot \frac{1}{jwC}}{R + \frac{1}{jwC}} = \frac{R}{1 + (wRC)^2} - j \frac{\omega R^2 C}{1 + (wRC)^2}$$



$$Z_{EQ} = jwL + Z_{RC} = \frac{R}{1 + (wRC)^2} + j \left[ \omega L - \frac{\omega R^2 C}{1 + (wRC)^2} \right]$$

when  $X_{EQ}=0 \Rightarrow$  "resonant frequency"


$$X_{EQ} (\omega = \omega_0) = \omega_0 L - \frac{\omega_0 R^2 C}{1 + (\omega_0 R C)^2} \Rightarrow \omega_0 = \sqrt{\frac{1}{LC} - \frac{1}{(RC)^2}}$$

## 8.14. Circuit theorems with phasors

### (A) Superposition

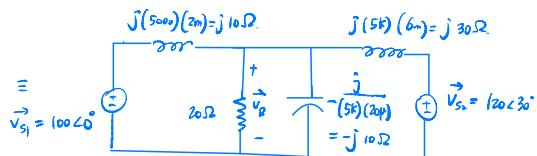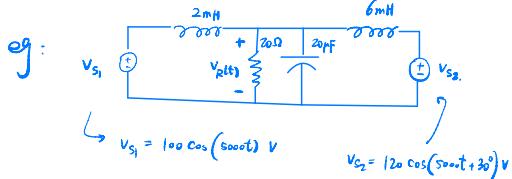


Find  $V_R(t)$

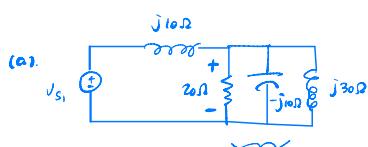

$$\vec{Z} = \frac{1}{\frac{1}{20} + \frac{1}{j10} + \frac{1}{j30}} = 7.2 - j.96$$
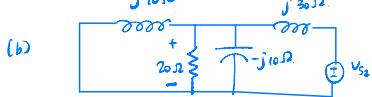
$$\vec{V}_R' = 100 \angle 0^\circ \cdot \frac{7.2 - j.96}{(7.2 - j.96) + j10} = 166.4 \angle -56.3^\circ = 92.3 - j138.5$$



$$\vec{Z} = \frac{1}{\frac{1}{j10} + \frac{1}{j10} + \frac{1}{20}} = 20\Omega$$


$$\vec{V}_R'' = 120 \angle 30^\circ \cdot \frac{20}{20 + j30} = 66.48 \angle -26.3^\circ = 59.6 - j.2946$$

$$\vec{V}_R = \vec{V}_R' + \vec{V}_R'' = 151.9 - j.167.96$$

$$= 226.46 \angle -47.87^\circ$$

$$V_R(t) = 226.46 \cos(500t - 47.87^\circ)$$

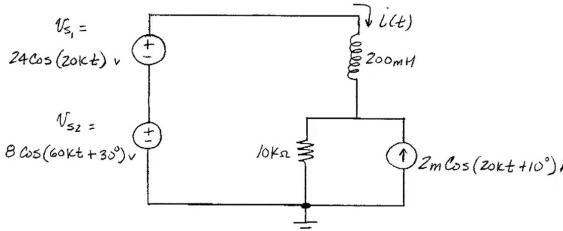
2) **EXAMPLE** SOURCES OF DIFFERENT FREQUENCIES



FIND THE STEADY-STATE VALUE OF  $I(t)$

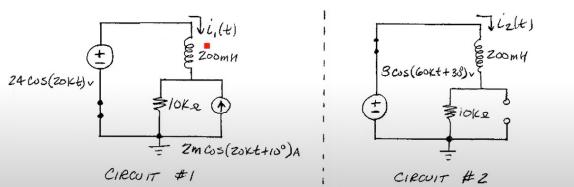**SOLUTION :**

- APPLY SUPERPOSITION IN THE TIME DOMAIN FOR SOURCES OF THE SAME FREQUENCY, THAT IS,



$$\text{By SUPERPOSITION, } I(t) = I_1'(t) + I_1''(t) + I_2(t)$$

(43)

CIRCUIT #1  
- STEP 1)  

$$I_1' = \frac{24\angle 0^\circ}{10k + j4k} = \frac{24\angle 0^\circ}{10.71k \angle 21.8^\circ}$$

$$= 2.228m \angle -21.8^\circ$$

$$= 2.069m - j0.8274m \frac{1}{j1k}$$

$$\omega = 20k$$

- STEP 2)  

$$\hat{I}_1' = \frac{24\angle 0^\circ}{10k + j4k} = \frac{24\angle 0^\circ}{10.71k \angle 21.8^\circ}$$

$$= 2.228m \angle -21.8^\circ$$

$$= 2.069m - j0.8274m \frac{1}{j1k}$$

$$= 2m \angle 10^\circ \frac{10k \angle 180^\circ}{10.71k \angle 21.8^\circ}$$

$$= 1.857m \angle 160.2^\circ$$

$$= -1.8173m + j0.3797m$$

$$\therefore \hat{I}_1 = \hat{I}_1' + \hat{I}_1''$$

$$= 0.251m - j0.4477m$$

$$= 513.3\mu \angle -60.7^\circ$$

- STEP 3)

$$I_1(t) = 513.3\mu \cos(20kt - 60.7^\circ)$$

CIRCUIT #2  
- STEP 1)  

$$I_2 = \frac{8\angle 30^\circ}{10k + j12k} = \frac{8\angle 30^\circ}{15.62k \angle 50.19^\circ}$$

$$= 512\mu \angle -20.19^\circ$$

$$\omega = 60k$$

- STEP 2)  

$$\hat{I}_2 = \frac{8\angle 30^\circ}{10k + j12k} = \frac{8\angle 30^\circ}{15.62k \angle 50.19^\circ}$$

$$= 512\mu \angle -20.19^\circ$$

$$I_2(t) = 512\mu \cos(60kt - 20.19^\circ) A$$

- STEP 3)

$$I(t) = 513.3\mu \cos(20kt - 60.7^\circ) +$$

$$512\mu \cos(60kt - 20.19^\circ) A$$

Another Sub

Superposition

here

$$\hat{I}_1'' = -Zm \frac{1}{10k + j4k}$$

$$= -Zm \frac{1}{10k \angle 180^\circ + j4k}$$

$$= -Zm \frac{1}{10.71k \angle 21.8^\circ}$$

$$= -1.8173m + j0.3797m$$

$$\therefore \hat{I}_1 = \hat{I}_1' + \hat{I}_1''$$

$$= 0.251m - j0.4477m$$

$$= 513.3\mu \angle -60.7^\circ$$

$$I_1(t) = 513.3\mu \cos(20kt - 60.7^\circ)$$


### (B) Source Transformation

#### 1) EXAMPLE 8.17


DO EX. 8.14 USING SOURCE TRANSFORMATIONS

SOLUTION :

- STEP 1)

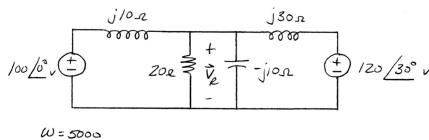

- STEP 2)

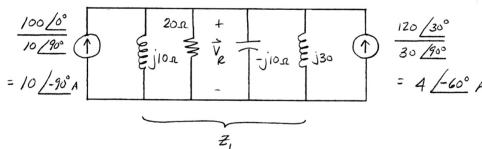

Since  $(j10) // (-j10) = \infty$  THEN

$$Z_L = \frac{20(j30)}{20+j30} = \frac{600 \angle 90^\circ}{36.06 \angle 52.3^\circ} = 16.639 \angle 33.69^\circ$$

$$\begin{aligned}\vec{V}_R &= (10 \angle -90^\circ + 4 \angle -60^\circ) (16.639 \angle 33.69^\circ) \\ &= (-j10 + 2 - j3.464) (16.639 \angle 33.69^\circ)\end{aligned}$$

$$\begin{aligned}\vec{V}_R &= (Z - j13.464) (16.639 \angle 33.69^\circ) \\ &= (13.612 \angle -81.55^\circ) (16.639 \angle 33.69^\circ) \\ &= 226.49 \angle -47.86^\circ\end{aligned}$$

- STEP 3)




$$V_R(t) = 226.49 \cos(5kt - 47.86^\circ) \text{ V}$$

$\leftarrow$  Same as p 41

ECE 202 e-Notes..... Copyright © 2021 by Gregory M. Wierzbka. All rights reserved..... Summer 2021.

### (c) Theven & Norton equivalent circuits

Review :

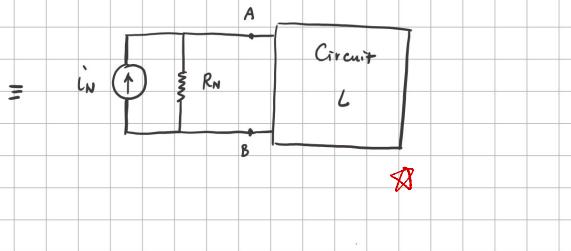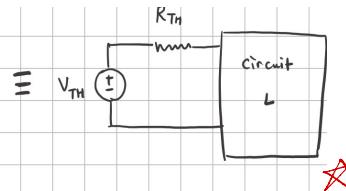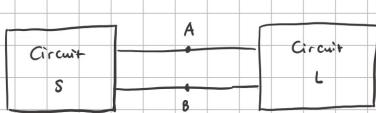


### C) THEVENIN AND NORTON EQUIVALENT CIRCUITS

#### 1) EXAMPLE

THEVENIZE THE CIRCUIT OF EX. B.10 WITH RESPECT TO THE  $3\text{k}\Omega$  LOAD. FIND  $V_o(t)$  IN STEADY - STATE.

SOLUTION :

- STEP 1)

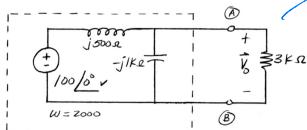

Another understanding



$\equiv$

- STEP 2)

a)  $\vec{V}_{TH}$

$$\vec{V}_{oc} = \vec{V}_{TH} = \frac{100 \angle 0^\circ}{j500 + j1k} = \frac{100 \angle 0^\circ}{-j1k + j500} = 200 \angle 60^\circ$$

b)  $Z_{TH}$

$$Z_{TH} = \frac{(j500)(j1k)}{j500 + j1k} = \frac{500k}{-j500} = j1000$$


c)

$$\vec{V}_o = \frac{200 \angle 20^\circ}{j500 + j1k} = \frac{200 \angle 20^\circ}{3.162k \angle 18.45^\circ} = 189.75 \angle -18.44^\circ$$



$$I = \frac{100 \angle 0^\circ}{500 \angle 90^\circ} = 200m \angle -90^\circ$$
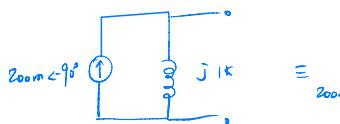
$$Z_{EQ} = \frac{(j0.5k)(-j1k)}{j0.5k + j(-1k)} = \frac{j0.5 \times 10^6}{-j25 \times 10^{-3}} = j1k$$



$$V = (200m \angle -90^\circ) \cdot (1k \angle 90^\circ)$$

$$= 200 \angle 0^\circ$$


- STEP 3)

$$V_o(t) = 189.75 \cos(2kt - 18.44^\circ) V$$


$\leftarrow$  Same as P26

## 8.5 General Circuit Analysis with Phasors

### (A) Node Voltage

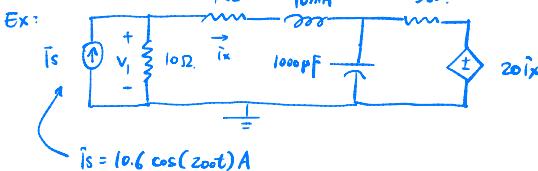

Find the steady-state value of  $V_1(t)$

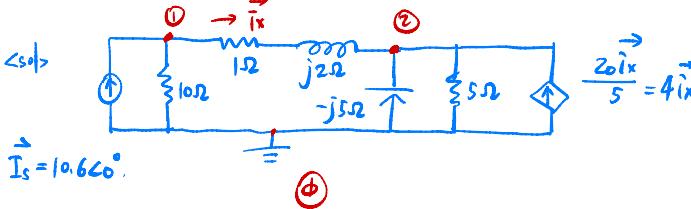

$$\omega = 2000$$

$$\begin{pmatrix} 10.6 \\ 4i_x \end{pmatrix} = \begin{pmatrix} \left(\frac{1}{10} + \frac{1}{1+j2}\right) & -\left(\frac{1}{1+j2}\right) \\ -\left(\frac{1}{1+j2}\right) & \left(\frac{1}{1+j2} + \frac{1}{-j5} + \frac{1}{5}\right) \end{pmatrix} \begin{pmatrix} \vec{V}_1 \\ \vec{V}_2 \end{pmatrix}$$

$$\vec{I}_x = \frac{\vec{V}_1 - \vec{V}_2}{1+j2} \Rightarrow -4\vec{I}_x = -4 - \frac{\vec{V}_1 - \vec{V}_2}{1+j2} = \frac{-4}{1+j2} \vec{V}_1 + \frac{4}{1+j2} \vec{V}_2$$

$$\Rightarrow \begin{pmatrix} 10.6 \\ 0 \end{pmatrix} = \begin{pmatrix} \left(\frac{1}{10} + \frac{1}{1+j2}\right) & -\left(\frac{1}{1+j2}\right) \\ \left(\frac{-5}{1+j2}\right) & \left(\frac{1}{1+j2} + \frac{j}{5} + \frac{1}{5}\right) \end{pmatrix} \begin{pmatrix} \vec{V}_1 \\ \vec{V}_2 \end{pmatrix}$$

$$\begin{bmatrix} 10.6 \\ 0 \end{bmatrix} = \begin{bmatrix} \left(\frac{11+j2}{10+j20}\right) & -\left(\frac{1}{1+j2}\right) \\ -\left(\frac{5}{1+j2}\right) & \left(\frac{24+j3}{5+j10}\right) \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}$$

$$\vec{V}_1 = \frac{\begin{vmatrix} 10.6 & -\left(\frac{1}{1+j2}\right) \\ 0 & \left(\frac{24+j3}{5+j10}\right) \end{vmatrix}}{\begin{vmatrix} \left(\frac{11+j2}{10+j20}\right) & -\left(\frac{1}{1+j2}\right) \\ -\left(\frac{5}{1+j2}\right) & \left(\frac{24+j3}{5+j10}\right) \end{vmatrix}} = \frac{(10.6)\left(\frac{24+j3}{5+j10}\right)}{\left(\frac{11+j2}{10+j20}\right)\left(\frac{24+j3}{5+j10}\right) - \left(\frac{5}{1+j2}\right)\left(\frac{1}{1+j2}\right)}$$

$$= \frac{10.6 \angle 0^\circ}{27.36 \angle 63.43^\circ} \frac{24.19 \angle 7.13^\circ}{11.18 \angle 63.43^\circ} - \frac{5 \angle 0^\circ}{2.236 \angle 63.43^\circ} \frac{1 \angle 0^\circ}{2.236 \angle 63.43^\circ}$$

$$= \frac{22.94 \angle -56.3^\circ}{1.032 \angle -107.57^\circ - 1.00 \angle -126.86^\circ} = \frac{22.94 \angle -56.3^\circ}{(-0.36 - j1.02) - (-0.6 - j0.8)}$$

$$= \frac{22.94 \angle -56.3^\circ}{0.24 - j0.22} = \frac{22.94 \angle -56.3^\circ}{0.3256 \angle -42.5^\circ} = 70.45 \angle -13.8^\circ$$

# MATLAB:

R

**COEFFICIENT FIRST**

**SUPPRESS PRINTING ON SCREEN**

$\left\{ \begin{array}{l} Y(1,1) = 1/10 + 1/(1+2j); \\ Y(1,2) = -1/(1+2j); \\ Y(2,1) = -5/(1+2j); \\ Y(2,2) = 5/(1+2j) + 1/5 + j/5; \end{array} \right.$

$\left. \begin{array}{l} \\ \\ \\ \end{array} \right\} 2 \times 2 Y \text{ MATRIX}$

**INVERSE OF Y**

$I = [10.6; 0];$

$V = Y \setminus I$

**MAGNITUDE OF A COMPLEX NUMBER**  
(CASE SENSITIVE - USE LOWER CASE)

$VM = \text{abs}(V)$

$VP = \text{angle}(V) * 180/\pi$

**ANGLE IN DEGREES**

**ANGLE IN RADIANS**

APPEND:


$$\begin{aligned} EDU &\gg \\ V &= \begin{pmatrix} 68.4000 & -16.8000i \\ 68.0000 & -26.0000i \end{pmatrix} = \begin{pmatrix} \vec{V}_1 \\ \vec{V}_2 \end{pmatrix} \end{aligned}$$

$$\begin{aligned} VM &= \begin{pmatrix} 70.4329 \\ 72.8011 \end{pmatrix} = \begin{pmatrix} |V_1| \\ |V_2| \end{pmatrix} \end{aligned}$$

$$\begin{aligned} VP &= \begin{pmatrix} -13.7995 \\ -20.9245 \end{pmatrix} = \begin{pmatrix} \angle V_1 \\ \angle V_2 \end{pmatrix} \end{aligned}$$

$$\therefore \vec{V}_1 = 70.4329 \angle -13.7995^\circ \quad \text{← Same result as p50}$$

## (B) Mesh Current

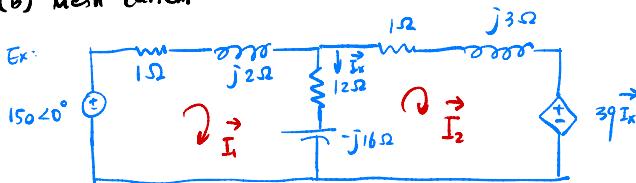

$$\begin{pmatrix} +150 \\ -39\vec{I}_x \end{pmatrix} = \begin{pmatrix} (1+j2+12-j16) & -(12-j16) \\ -(12-j16) & (12-j16+1+j3) \end{pmatrix} \begin{pmatrix} \vec{I}_1 \\ \vec{I}_2 \end{pmatrix}$$

$$\vec{I}_x = \vec{I}_1 - \vec{I}_2$$

$$\Rightarrow +39\vec{I}_x = +39\vec{I}_1 - 39\vec{I}_2$$

$$\Rightarrow \begin{pmatrix} 150 \\ 0 \end{pmatrix} = \begin{pmatrix} 13-j14 & 12-j16 \\ -12+j16+39 & 13-j13-39 \end{pmatrix} \begin{pmatrix} \vec{I}_1 \\ \vec{I}_2 \end{pmatrix}$$

SCRIPT FILE "MESH.m"

```
Z(1,1) = 13-14j;
Z(1,2) = -12+j16;
Z(2,1) = 27+j16;
Z(2,2) = -26-j13;

V = [150;0];
I = Z\V;
IM=abs(I);
IP=angle(I)*180/pi;
```

SCREEN OUTPUT

```
EDU>>
I =
-26.0000 -52.0000i =  $\frac{\vec{I}_1}{\vec{I}_2}$ 
-24.0000 -58.0000i =  $\frac{\vec{I}_2}{\vec{I}_1}$ 

IM =
58.1378 =  $|\vec{I}_1|$ 
62.7694 =  $|\vec{I}_2|$ 


IP =
-116.5651 =  $\angle \vec{I}_1$ 
-112.4794 =  $\angle \vec{I}_2$ 
```

## 8.6 Energy And Power

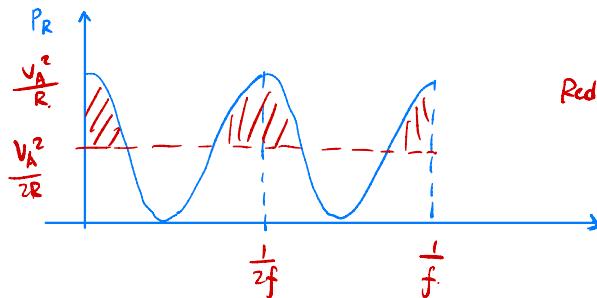(A) Resistance




$$P_R(t) = \frac{V(t)^2}{R} = \frac{V_A^2 \cos^2(\omega t)}{R} = \frac{V_A^2}{2R} (1 + \cos(2\omega t))$$




Red: always > 0

$$\begin{aligned} P_R(\text{avg}) &\triangleq P_R = \frac{1}{T} \int_0^T \frac{V_A^2}{2R} (1 + \cos(2\omega t)) dt \\ &= \frac{V_A^2}{2RT} \int_0^T (1 + \cos(2\omega t)) dt \\ &= \frac{V_A^2}{2RT} \left( t \Big|_0^T + \frac{1}{2\omega} \sin(2\omega t) \Big|_0^T \right) \\ &= \frac{V_A^2}{2RT} \left[ (T - 0) + \frac{1}{2\omega} \sin(2\pi f \cdot \frac{T}{f}) \right] \\ &= \boxed{\frac{V_A^2}{2R}} \end{aligned}$$

$$\begin{aligned} w_R(t) &= \int_0^t P_R(x) dx = \int_0^t \frac{V_A^2}{2R} (1 + \cos 2\omega x) dx = \frac{V_A^2}{2R} \int_0^t (1 + \cos 2\omega x) dx \\ &= \frac{V_A^2}{2R} \left[ x \Big|_0^t + \frac{1}{2\omega} \sin(2\omega x) \Big|_0^t \right] = \frac{V_A^2}{2R} \left[ t + \frac{1}{2\omega} \sin(2\omega t) \right] \\ &= \boxed{\frac{V_A^2}{2R} t + \frac{V_A^2}{4R\omega} \sin(2\omega t)} \end{aligned}$$

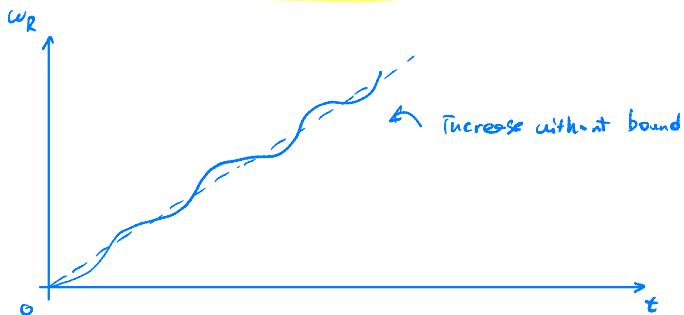



(B) Inductance

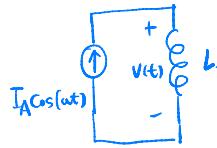


$$W_L(t) = \frac{1}{2} L [i(t)]^2 = \frac{1}{2} L \cdot I_A^2 \cos^2 \omega t$$

$$= \frac{1}{4} L I_A^2 (1 + \cos(2\omega t))$$
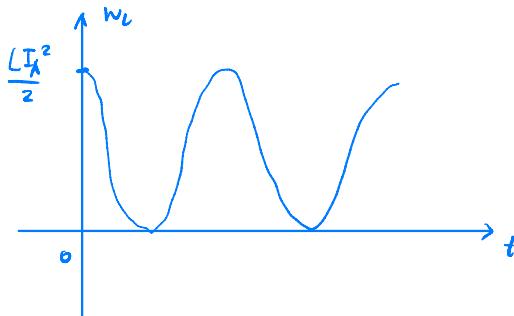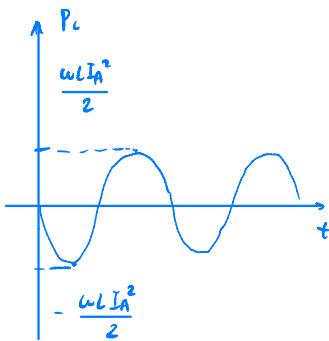
$$P_L(t) = \frac{dW_L(t)}{dt} = \frac{1}{4} L I_A^2 [0 + (-2\omega) \sin(2\omega t)] = -\frac{\omega L I_A^2}{2} \sin(2\omega t)$$





(c) Capacitance

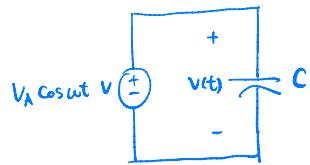

$$W_C(t) = \frac{1}{2} C V(t)^2 = \frac{1}{2} C V_A^2 \cos^2(\omega t) = \frac{1}{4} C V_A^2 (1 + \cos(2\omega t))$$


$$P_C(t) = \frac{dW_C(t)}{dt} = \frac{1}{4} C V_A^2 [0 + (-2\omega) \sin(2\omega t)]$$
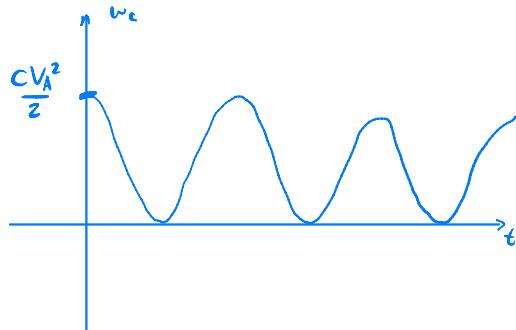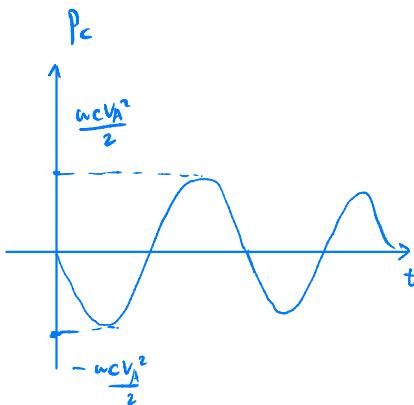
$$= -\frac{\omega C V_A^2}{2} \sin(2\omega t)$$



Equating AC and DC Power

Since we know  $P_R = \frac{V_A^2}{2R}$  (Avg)

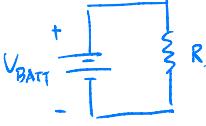
$$V_{BATT} + \boxed{\text{---}} \quad \boxed{R}$$
$$P_R(t) = \frac{V_{BATT}^2}{R} = \frac{V_A^2}{2R} \Rightarrow V_{BATT} = \frac{V_A}{\sqrt{2}}$$


$$\frac{V_{BATT}^2}{R} = \frac{1}{T} \int_0^T \frac{[V_A \cos \omega t]^2}{R} dt \Rightarrow V_{BATT} \triangleq V_{EFFECTIVE} \triangleq V_{RMS} = \sqrt{\frac{1}{T} \int_0^T [V_A \cos \omega t]^2 dt}$$

In general  $F_{RMS} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}$


# Chapter 9: Laplace Transformation

(A) Def:  $\mathcal{L}\{f(t)\} \triangleq F(s) = \int_{0^-}^{\infty} f(t)e^{-st} dt$ , where  $s = \sigma + j\omega$ , and  $f(t) = 0$  for  $t < 0$


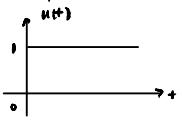
(B) Step wave form.  $u(t) \triangleq \begin{cases} 0 & \text{For } t < 0 \\ 1 & \text{For } t > 0 \end{cases}$



Also  $Ku(t)$

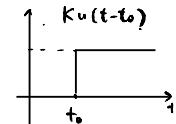

(C) Example 5.1

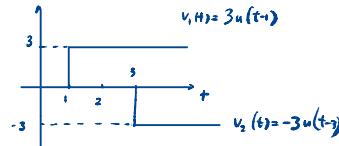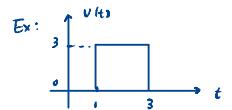


$$v(t) = v_1(t) + v_2(t) = 3u(t-1) - 3u(t-3) \quad v$$


(D)  $f(t) = u(t) \Rightarrow F(s) = \frac{1}{s}$

$$f(t) = e^{-st} u(t) \Rightarrow F(s) = \frac{1}{s - a}$$

(E) The impulse function.

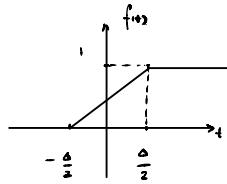


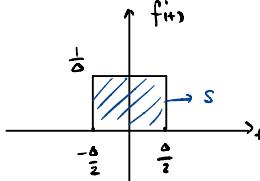$f(t) \rightarrow u(t)$   
As  $\Delta \rightarrow 0$



$$S = \frac{1}{\Delta} \left[ \frac{\Delta}{2} - (-\frac{\Delta}{2}) \right] = 1$$

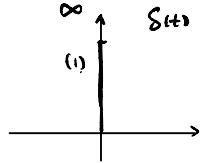- The unit impulse function  $\delta(t)$  is defined as  $f(t)$  as  $\Delta \rightarrow 0$  and  $\delta(t) = 0$  for  $t \neq 0$



$$\int_{-\infty}^t \delta(x) dx = u(t)$$

$$\begin{aligned} f(t) &= \delta(t), \\ F(s) &= \int_{0^-}^{\infty} \delta(t) e^{-st} dt = \underbrace{\int_{0^+}^{0^+} \delta(t) e^{-st} dt}_{\text{Area of 1}} + \int_{0^+}^{\infty} \delta(t) e^{-st} dt \end{aligned}$$

$$= 1$$

(G) Inverse Transformation:

$$\mathcal{L}^{-1}\{F(s)\} \triangleq f(t) = \frac{1}{2\pi j} \int_{a-j\infty}^{a+j\infty} F(s) e^{st} ds$$

$$\operatorname{Re}\{s\} = a$$

(H) Uniqueness Property  $\mathcal{L}^{-1}\{\mathcal{L}\{f(t)\}\} = \mathcal{L}^{-1}\{F(s)\} = f(t)$

Some Laplace transformation:

$$\mathcal{L}\{1\} = \frac{1}{s}$$

$$\mathcal{L}\{e^{at}\} = \frac{1}{s-a}$$

$$\mathcal{L}\{\sin(bt)\} = \frac{b}{s^2 + b^2}$$

$$\mathcal{L}\{\cos(bt)\} = \frac{s}{s^2 + b^2}$$

$$\mathcal{L}\{t^n\} = \frac{n!}{s^{n+1}}$$

Properties:

$$L\{af(t) + bg(t)\} = aF(s) + bG(s) \Leftrightarrow L^{-1}\{aF(s) + bG(s)\} = af(t) + bg(t)$$

$$L\{f'(t)\} = sF(s) - f(0) \quad \text{For higher derivative} \quad L\{f^{(n)}(t)\} = s^n F(s) - s^{n-1} f^{(1)}(0) - \dots - f^{(n-1)}(0)$$

$$L\{e^{at} f(t)\} = F(s-a)$$

$$L\{(f*g)(t)\} = F(s) \cdot G(s) \quad \text{where } (f*g)(t) = \int_0^t f(\tau) \cdot g(t-\tau) d\tau$$

Some prep:

$$\textcircled{1} \text{ Show that } L\{A(1-e^{-at}) u(t)\} = \frac{Ad}{s(s+a)}$$

$$L\{A(1-e^{-at}) u(t)\} = A L\{u(t)\} - A L\{e^{-at} u(t)\} = \frac{A}{s} - \frac{A}{s+a} = \frac{Aa}{s(s+a)}$$

$$\textcircled{2} \text{ Show that } L\{A[\sin(\beta t)] u(t)\} = \frac{A\beta}{s^2 + \beta^2}$$

$$\text{For } e^{j\beta t} = \cos \beta t + j \sin \beta t, \quad e^{-j\beta t} = \cos \beta t - j \sin \beta t \Rightarrow \sin \beta t = \frac{e^{j\beta t} - e^{-j\beta t}}{2j}$$

$$f(t) = A \sin \beta t = \frac{A}{2j} e^{j\beta t} - \frac{A}{2j} e^{-j\beta t} \Rightarrow L\{f(t)\} = \frac{A}{2j} L\{e^{j\beta t} u(t)\} - \frac{A}{2j} L\{e^{-j\beta t} u(t)\}$$

$$\Rightarrow L\{f(t)\} = \frac{A}{2j} \cdot \frac{1}{s-j\beta} - \frac{A}{2j} \cdot \frac{1}{s+j\beta} = \frac{A\beta}{s^2 + \beta^2}$$

$$\text{Integration Property: } L\left[\int_0^t f(x) dx\right] = \frac{F(s)}{s}$$

$$\text{Proof: } L\left\{\int_0^t f(x) dx\right\} = \int_{0^-}^{\infty} \left[ \int_0^t f(x) dx \right] e^{-st} dt$$


$$\text{Since: } \int_a^b u dv = uv \Big|_a^b - \int_a^b v du. \Rightarrow \text{let } u = \int_0^t f(x) dx \quad dv = e^{-st} dt$$

$$\text{therefore } du = f(t) dt \quad v = -\frac{1}{s} e^{-st} \Rightarrow \text{RHS} = \left[ \int_0^t f(x) dx \right] \left[ -\frac{1}{s} e^{-st} \right] \Big|_{0^-}^{\infty} - \int_{0^-}^{\infty} \left( -\frac{1}{s} \right) e^{-st} f(t) dt.$$

$$\Rightarrow \text{RHS} = \frac{1}{s} \int_{0^-}^{\infty} f(t) e^{-st} dt = \frac{1}{s} \cdot F(s) \quad \boxed{\text{Q.E.D}}$$

The ramp function
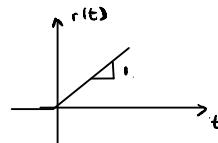
$$r(t) \stackrel{\Delta}{=} \int_{-\infty}^t u(x) dx = t u(t)$$



$$\begin{aligned} L\{r(t)\} &= L\left\{\int_{-\infty}^t u(x) dx\right\} = L\left\{\int_0^t u(x) dx\right\} \\ &= \frac{1}{s} F(s) = \boxed{\frac{1}{s^2}} \end{aligned}$$

Differential Property.

$$L\left\{ \frac{df(t)}{dt} \right\} = sF(s) - f(0)$$

Proof:  $L\left\{ \frac{df(t)}{dt} \right\} = \int_0^\infty \frac{df(t)}{dt} e^{-st} dt$  let  $u = e^{-st}$   $dv = \frac{df(t)}{dt} dt$ .  $\Rightarrow du = -se^{-st} dt$   $v = f(t)$

$$\Rightarrow \int_0^\infty u dv = e^{-st} f(t) \Big|_0^\infty - \int_0^\infty f(t) (-s) e^{-st} dt = -f(0) + s \int_0^\infty f(t) e^{-st} dt = [sF(s) - f(0)]$$

$n^{\text{th}}$  Derivative:  $L\left\{ \frac{d^n f(t)}{dt^n} \right\} = s^n F(s) - s^{n-1} f(0) - s^{n-2} f'(0) - \dots - f^{(n-1)}(0)$   
 $L\{g(t)\} = L\left\{ \frac{df(t)}{dt} \right\}$

Proof: let  $g(t) = \frac{df(t)}{dt}$  then  $\frac{dg(t)}{dt} = \frac{d^2 f(t)}{dt^2}$ .  $G(s) = sF(s) - f(0)$

$$L\left\{ \frac{dg(t)}{dt} \right\} = sG(s) - g(0) = s[sF(s) - f(0)] - f'(0) = s^2 F(s) - sf(0) - f'(0)$$

let  $h(t) = \frac{dg(t)}{dt}$  then  $L\left\{ \frac{dh(t)}{dt} \right\} = sH(s) - h(0) = s[s^2 F(s) - sf(0) - f'(0)] - g'(0)$

$$\Rightarrow L\left\{ \frac{dh(t)}{dt} \right\} = s^3 F(s) - s^2 f(0) - sf'(0) - f''(0) \quad \text{Keep repeating For the answer. Q.E.D}$$

S-Domain translation property

$$\text{If } L\{f(t)\} = F(s) \text{ then } L\{e^{-at} f(t)\} = F(s+a)$$

Proof:  $L[e^{-at} f(t)] = \int_0^\infty e^{-at} f(t) e^{-st} dt = \int_0^\infty e^{-(s+a)t} f(t) dt = F(s+a)$

Time-domain translation property

$$\text{If } L\{f(t)\} = F(s) \text{ then for } a > 0, L[f(t-a) u(t-a)] = e^{-as} F(s)$$

Proof:  $L[f(t-a) u(t-a)] = \int_0^\infty f(t-a) u(t-a) e^{-st} dt = \int_a^\infty f(t-a) e^{-st} dt \quad \text{let } \uparrow = t-a$

then  $\frac{d\uparrow}{dt} = 1 \Rightarrow d\uparrow = dt$ . For  $t=a$ ,  $\uparrow = a-a=0$ . For  $t=\infty$ ,  $\uparrow = \infty-a=\infty$

$$\Rightarrow \int_a^\infty f(t-a) e^{-st} dt = \int_0^\infty f(\uparrow) e^{-s(\uparrow+a)} d\uparrow = e^{-sa} \int_0^\infty f(\uparrow) e^{-s\uparrow} d\uparrow = [e^{-as} F(s)]$$

# Basic Laplace transformation

- THE FOLLOWING IS A COLLECTION OF COMMON TRANSFORM PAIRS

SIGNAL	$f(t)$	$F(s)$
1) IMPULSE	$\delta(t)$	1
2) STEP	$u(t)$	$\frac{1}{s}$
3) RAMP	$t u(t)$	$\frac{1}{s^2}$
4) EXPONENTIAL	$e^{-\alpha t} u(t)$	$\frac{1}{s+\alpha}$
5) DAMPED RAMP	$t e^{-\alpha t} u(t)$	$\frac{1}{(s+\alpha)^2}$
6) SINE	$\sin(\beta t) u(t)$	$\frac{\beta}{s^2 + \beta^2}$
7) COSINE	$\cos(\beta t) u(t)$	$\frac{s}{s^2 + \beta^2}$
8) DAMPED SINE	$e^{-\alpha t} \sin(\beta t) u(t)$	$\frac{\beta}{(s+\alpha)^2 + \beta^2}$
9) DAMPED COSINE	$e^{-\alpha t} \cos(\beta t) u(t)$	$\frac{(s+\alpha)}{(s+\alpha)^2 + \beta^2}$

## 9.3 Pole-Zero diagrams

In general  $F(s) = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}$

we factor the number  $\Rightarrow F(s) = K \cdot \frac{(s-z_1)(s-z_2) \dots (s-z_n)}{(s-p_1)(s-p_2) \dots (s-p_n)}$   $K = \frac{b_m}{a_n}$  (scale factor)

$$F(s) = \frac{N(s)}{D(s)}$$

X

Poles: value of  $s$  makes  $D(s)=0$

O

Zeros: values of  $s$  that makes  $N(s)=0$

$$F(s) = 0$$

b) MATLAB

- MATLAB CAN FIND THE LAPLACE TRANSFORM OF ANY FILE

```

% DEPENDS t & s
EDU> syms t s
EDU> f = exp(-2*t) + t*t - 1      % EX. ON p14
s =
exp(-2*t)+t*t-1                  % MATLAB RESPONSE
EDU> F = laplace (f, t, s)          % 2. TRANSFORM f(t)=F(s)
F =
1/(s+2)+t/s^2-1/s                % 2nd ORDER
1/(s+2)+t/s^2-1/s                % SAME AS P14
EDU> simplify (F)
ans =
2*(s+1)/(s+2)/s^2                % 2. FINDS COMMON DENOMINATOR
EDU> pretty (ans)

          s + 1
          -----
          2
          (s + 2) s

```

$\frac{s+1}{(s+2)s}$  2. MAKE REVERSE

#### 9.4 Inverse Laplace transformation

$$F(s) = K \frac{(s-z_1)(s-z_2)\dots(s-z_n)}{(s-p_1)(s-p_2)\dots(s-p_n)}$$

- if  $n > m \Rightarrow F(s)$  is called a "proper rational function"
- if denominators has no repeated roots ( $p_i \neq p_j$  for  $i \neq j$ )  $\Rightarrow F(s)$  has "simple poles"
- if a proper rational function has only simple poles, then it can be decomposed into a "partial fraction expansion" of the form.

$$F(s) = \frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \dots + \frac{k_n}{s-p_n} \quad k \text{ is called "residues"}$$

$$\Rightarrow f(t) = [k_1 e^{p_1 t} + k_2 e^{p_2 t} + \dots + k_n e^{p_n t}] u(t)$$

ex:  $F(s) = K \frac{(s-z_1)}{(s-p_1)(s-p_2)(s-p_3)} = \frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \frac{k_3}{s-p_3}$

times  $(s-p_1)$  both sides  $\Rightarrow (s-p_1) F(s) = \frac{k_1 (s-z_1)}{(s-p_2)(s-p_3)} = k_1 + \frac{k_2 (s-p_1)}{s-p_2} + \frac{k_3 (s-p_1)}{s-p_3}$

So we set  $s = p_1 \Rightarrow \frac{k_1 (s-z_1)}{(p_1-p_2)(p_1-p_3)} = k_1 + 0 + 0 = k_1 \quad \text{similar find } k_2 \text{ & } k_3$

$$\Rightarrow k_i = (s-p_i) F(s) \Big|_{s=p_i}$$

#### A) EXAMPLE

FIND THE WAVEFORM CORRESPONDING TO THE TRANSFORM

$$F(s) = \frac{2(s+3)}{s(s+1)(s+2)}$$

Solution:

SINCE  $n=3 > m=1$ , THEN

$$F(s) = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+2}$$

$$k_1 = s F(s) \Big|_{s=0} = \cancel{\frac{2(s+3)}{s(s+1)(s+2)}} \Big|_{s=0} = \frac{2(0+3)}{(0+1)(0+2)} = \frac{6}{2} = 3$$

$$k_2 = (s+1) F(s) \Big|_{s=-1} = \cancel{\frac{2(s+3)}{s(s+1)(s+2)}} \Big|_{s=-1} = \frac{2(-1+3)}{(-1)(-1+2)} = \frac{4}{-1} = -4$$

$$k_3 = (s+2) F(s) \Big|_{s=-2} = \cancel{\frac{2(s+3)}{s(s+1)(s+2)}} \Big|_{s=-2} = \frac{2(-2+3)}{(-2)(-2+1)} = \frac{2}{2} = 1$$

$$F(s) = \frac{3}{s} - \frac{4}{s+1} + \frac{1}{s+2}$$

$$f(t) = 3u(t) - 4e^{-t}u(t) + e^{-2t}u(t) \\ = 3 - 4e^{-t} + e^{-2t} \quad t > 0$$

Complex poles

$$F(s) = \dots + \frac{k}{s+a-j\beta} + \frac{k^*}{s+a+j\beta} + \dots$$

Since  $k = (s+a-j\beta) F(s) \Big|_{s=-a+j\beta}$  and  $k^* = (s+a+j\beta) F(s) \Big|_{s=-a-j\beta}$

FIND THE INVERSE TRANSFORM OF

$$F(s) = \frac{20(s+3)}{(s+1)(s^2+2s+5)}$$

$$ax^2 + bx + c$$

SOLUTION:

$$s^2 + 2s + 5 \text{ HAS ROOTS AT } s = \frac{-2 \pm \sqrt{4 - 4(5)}}{2} = -1 \pm j2$$

$$F(s) = \frac{k_1}{s+1} + \frac{k_2}{s+1-j2} + \frac{k_2^*}{s+1+j2}$$

$$k_1 = (s+1) F(s) \Big|_{s=-1} = \cancel{(s+1)} \frac{20(s+3)}{\cancel{(s+1)}(s^2+2s+5)} \Big|_{s=-1} = \frac{20(-1+3)}{(1-2+5)} = \frac{40}{4} = 10$$

$$f(t) = [10e^{-t} + 14.4 e^{-t} \cos(2t - 135^\circ)] \text{ u(t)}$$

$$k_2 = (s+1-j2) F(s) \Big|_{s=-1+j2}$$

$$= \cancel{(s+1-j2)} \frac{20(s+3)}{\cancel{(s+1)}(s+1-j2)(s+1+j2)} \Big|_{s=-1+j2}$$

$$= \frac{20(-1+j2+3)}{(-1-j2)(j2+1+j2)} = \frac{20(j2+2)}{(j2)(j4)} = -5-j5 = 7.07 \angle -135^\circ$$

NOTE:

$$k_3 = (s+1+j2) F(s) \Big|_{s=-1-j2} = \cancel{(s+1+j2)} \frac{20(s+3)}{\cancel{(s+1)}(s+1-j2)(s+1+j2)} \Big|_{s=-1-j2}$$

$$= \frac{20(-1-j2+3)}{(-1-j2)(-j2+1-j2)} = \frac{20(j2-2)}{(-j2)(-j4)} = -5+j5 = k_2^*$$

#### D) SUM OF RESIDUES

$$k_1 + k_2 + \dots + k_n = \begin{cases} 0 & \text{IF } n > m+1 \\ K & \text{IF } n = m+1 \end{cases}$$

PROOF:

$$\lim_{s \rightarrow \infty} s F(s) = \lim_{s \rightarrow \infty} \frac{K s^{m+1}}{s^n} = \lim_{s \rightarrow \infty} \left[ \frac{k_1 s}{s-p_1} + \frac{k_2 s}{s-p_2} + \dots + \frac{k_n s}{s-p_n} \right]$$

$$K \lim_{s \rightarrow \infty} \frac{s^{m+1}}{s^n} = k_1 + k_2 + \dots + k_n$$

$$\text{IF } n = m+1, \quad K \lim_{s \rightarrow \infty} \frac{s^{m+1}}{s^n} = K = k_1 + k_2 + \dots + k_n$$

$$\text{IF } n > m+1, \quad K \lim_{s \rightarrow \infty} \frac{s^{m+1}}{s^n} = 0 = k_1 + k_2 + \dots + k_n$$

QED

9.6 Laplace transformation solve differential equation.

eg:  $\frac{d^2x}{dt^2} + 4 \frac{dx}{dt} + 3x = e^{-t}, \quad x(0)=1, \quad \frac{dx(0)}{dt}=2$

$\Rightarrow [s^2 X(s) - s x(0) - s^0 X'(0)] + 4[s X(s) - s^0 X(0)] + 3 X(s) = \frac{1}{s+2}$

$$(s^2 X(s) - s - 2) + 4(s X(s) - 1) + 3 X(s) = \frac{1}{s+2}$$

$$X(s) [s^2 + 4s + 3] = \frac{1}{s+2} + s + 6 \Rightarrow \frac{(s+6)(s+2)+1}{s+2}$$


$$X(s) = \frac{s^2 + 8s + 13}{(s+1)(s+3)(s+2)} = \frac{k_1}{s+1} + \frac{k_2}{s+2} + \frac{k_3}{s+3}$$

$$\Rightarrow k_1 = (s+1) X(s) \Big|_{s=-1} = \frac{1-8+13}{2 \times 1} = 3, \quad \text{so as } k_2 = -1, \quad k_3 = -1$$

$$X(s) = \frac{3}{s+1} - \frac{1}{s+2} - \frac{1}{s+3} \Rightarrow X(t) = 3e^{-t} - e^{-2t} - e^{-3t} \quad (t>0)$$

# Chapter 10: S-Domain Circuit


## 10.1 Transformed Circuits

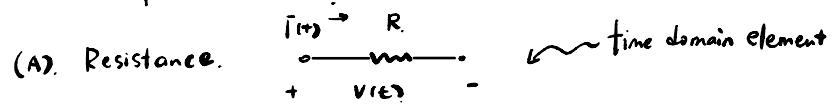

$$V(t) = R i(t) \quad L\{V(t)\} = L\{R i(t)\} = R L\{i(t)\}$$


$V(s) = R I(s)$

↷ S-Domain Ohm's law

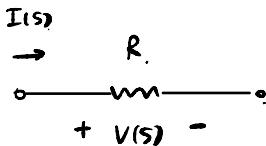



↷ S-Domain element.

## (B) Inductance

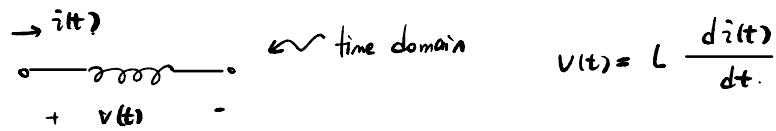


$$L\{V(t)\} = L\left\{L \frac{di(t)}{dt}\right\} = L \cdot L\left\{\frac{di(t)}{dt}\right\}$$

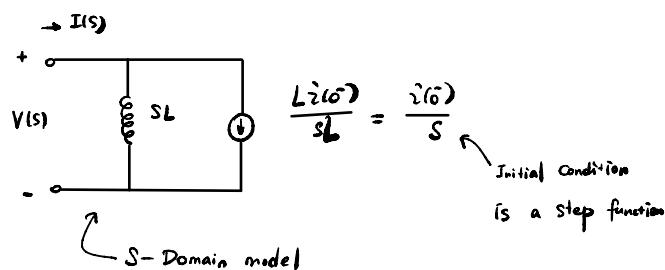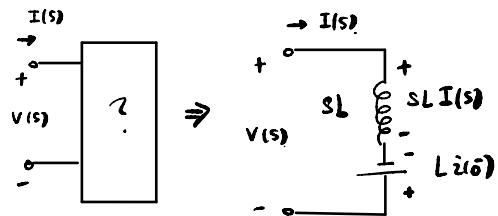
$$V(s) = L \left[ s I(s) - i(0) \right] = s L I(s) - L i(0) \quad \leftarrow S \text{ Domain.}$$



### (3) Capacitance

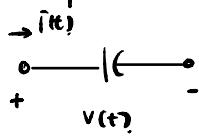  $V(t) = \frac{1}{C} \int_0^t i(x) dx + V_c(0)$
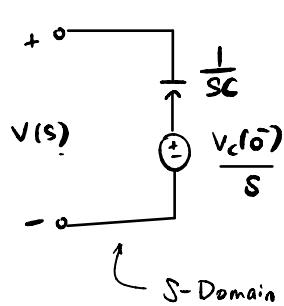
$$\mathcal{L}\{V(t)\} = \mathcal{L}\left\{\frac{1}{C} \int_0^t i(x) dx + V_c(0)\right\} \Rightarrow V(s) = \frac{1}{C} \cdot \frac{I(s)}{s} + \frac{V_c(0)}{s}$$




$$V(s) = \frac{1}{SC} I(s) + \frac{V_c(0)}{s}$$

### (B) Impedance and admittance.

$$V(s) = R I(s)$$


$$V(s) = sL I(s)$$

$$V(s) = \frac{1}{SC} I(s)$$

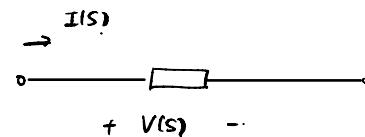

$$Z = \begin{cases} R \\ sL \\ \frac{1}{SC} \end{cases}$$

Eg: An example of S-Domain

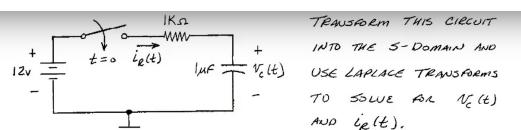


SOLUTION:

- STEP 1) FIND THE INITIAL CONDITIONS

WITH THE SWITCH OPEN FOR A LONG TIME,  $V_c(0^-) = 0$

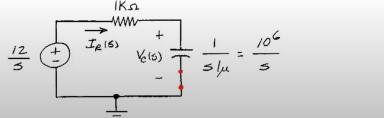- STEP 2) TRANSFORM CIRCUIT TO THE S-DOMAIN



- STEP 3) PERFORM S-DOMAIN CIRCUIT ANALYSIS

$$I_R(s) = \frac{\frac{12}{s}}{1k + \frac{10^6}{s}} = \frac{12}{(1k)s + 10^6} = \frac{12m}{s + 1k}$$

$$V_c(s) = \frac{12m}{s + 1k} \cdot \frac{10^6}{s} = \frac{12K}{s(s + 1k)}$$

- STEP 4) PERFORM PFE\* (WHERE NECESSARY)

$$V_c(s) = \frac{k_1}{s} + \frac{k_2}{s + 1k}$$

$$k_1 = s \cdot \frac{12K}{s(s + 1k)} \Big|_{s=0} = \frac{12K}{1k} = 12$$

- STEP 5) FIND THE INVERSE LAPLACE TRANSFORM

$$I_R(s) = \frac{12m}{s + 1k}$$

$$i_R(t) = 12m e^{-1k \cdot t} u(t)$$

$$= 12m e^{-t/\tau} u(t) A$$

$$V_c(s) = \frac{12}{s} - \frac{12}{s + 1k}$$


$$V_c(t) = 12u(t) - 12e^{-1k \cdot t} u(t)$$

$$= 12(1 - e^{-t/\tau}) u(t) V$$


- NOTE: Always express exponentials as  $e^{-t/\tau}$

WHERE  $\tau$  IS THE TIME CONSTANT


Practice Example:

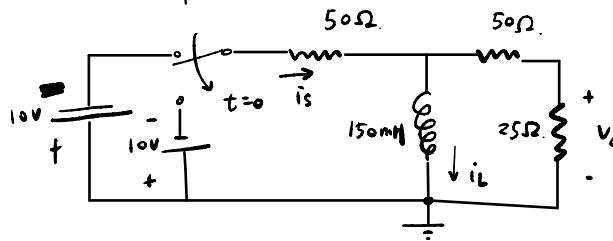
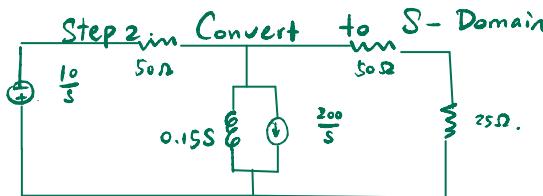
<Solution>: Step 1: Find  $i_L(0) = \frac{10V}{50\Omega} = 200mA$



Applied Superposition method:


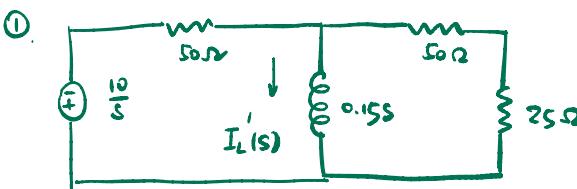


$$I_L'(s) = - \left( \frac{\frac{10}{s}}{50\Omega + 0.15s / (50\Omega + 25\Omega)} \right) \times \frac{\frac{1}{0.15s}}{0.15s + \frac{1}{50+25}}$$

$$= \frac{-40}{s(s+200)}$$

$$I_L''(s) = I_L''(s) = \frac{0.2(s-200)}{s(s+200)}$$

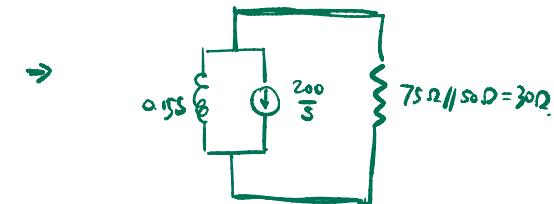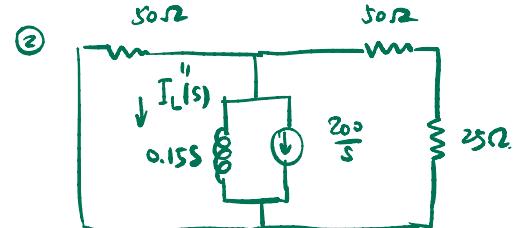Step 4:  $I_L(s) = \frac{-0.2}{s} + \frac{0.4}{s+200}$




$$\begin{aligned} I_L''(s) &= \frac{200m}{s} \times \left( \frac{1}{\frac{1}{0.15s} + \frac{1}{30}} \right) \div 0.15s \\ &= \frac{200m}{s} \cdot \left( \frac{1}{0.15s + \frac{1}{30}} \right) \times \frac{1}{0.15s} \\ &= \frac{0.2}{s+200} \end{aligned}$$

$\Rightarrow i_L(t) = -0.2u(t) + 0.4e^{-20t} u(t)$

# 10.2 Basic Circuit Analysis In S-Domain

## A) EXAMPLE 10.2 - REVISITED

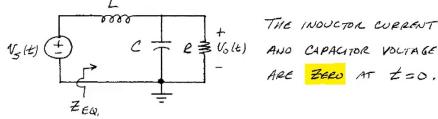

1) TRANSFORM THE CIRCUIT INTO THE S-DOMAIN AND FIND  $Z_{EQ}(s)$  AND  $V_o(s)$ .


2) EVALUATE 1) FOR  $L = 250\text{mH}$ ,  $C = 0.5\mu\text{F}$ ,  $R = 3\text{k}$  AND  $s = j\omega = j2000$ .

3) IF  $V_s(t) = 100 \cos(2000t)$ , FIND  $V_o(t)$  USING MATLAB. COMPARE WITH PSpice.

SOLUTION

13 / 28

1)

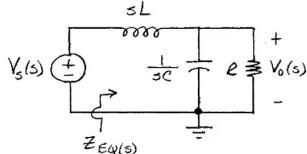

$$Z_{EQ} = sL + \frac{1}{sC + \frac{1}{sR}} = sL + \frac{R}{sCR + 1}$$

$$= \frac{s^2(LCR) + sL + R}{sCR + 1}$$

$$V_o(s) = V_s(s) \frac{\frac{R}{sCR + 1}}{\frac{R}{sCR + 1} + sL}$$

$$= V_s(s) \frac{R}{R + s^2LCR + sL}$$

$$= \frac{R}{s^2(LCR) + s(L) + R} V_s(s)$$

2)

$$Z_{EQ} = \frac{s^2(0.25)(0.5\mu)(2k) + s(0.25) + 3k}{s(0.5\mu)(3k) + 1}$$

$$= \frac{s^2(375\mu) + s(0.25) + 3k}{s(1.5m) + 1}$$

IF  $s = j\omega = j2000 \neq s^2 = -\omega^2 = -(2000)^2 = -4(10^6)$  THEN

$$Z_{EQ} = \frac{-4(10^6)(375\mu) + j(2k)(0.25) + 3k}{j(2k)(1.5m) + 1}$$

$$= \frac{-1.5k + j500 + 3k}{j + 1}$$

$$= \frac{1.5k + j500}{1 + j3} = \frac{1.5811k \angle 18.43^\circ}{3.162 \angle 71.57^\circ}$$

$$= 500 \angle -53.14^\circ \Omega \quad \leftarrow \text{SAME AS CH8 p25}$$

$$V_o = \frac{3k}{s^2(0.25)(0.5\mu)(3k) + s(0.25) + 3k} V_s(s)$$

$$= \frac{3k}{s^2(375\mu) + s(0.25) + 3k} V_s(s)$$

IF  $s = j\omega = j2000 \neq s^2 = -4(10^6)$  THEN

$$\begin{aligned} V_o &= \frac{3k}{-4(10^6)375\mu + j(2k)(0.25) + 3k} V_s(j\omega) \\ &= \frac{3k}{-1.5k + j500 + 3k} V_s(j\omega) \\ &= \frac{3k}{1.5k + j500} V_s(j\omega) \\ &= \frac{3k \angle 0^\circ}{1.5811k \angle 18.43^\circ} V_s(j\omega) \\ &= (1.89 \angle 18.43^\circ) V_s(j\omega) \end{aligned}$$

IF  $V_s(j\omega) = 100 \angle 0^\circ$  THEN  $V_o = 100 \angle 18.43^\circ \text{ V}$

$\hookrightarrow$  SAME AS  
CH8 p25  
CH8 p26

3) IF  $V_s(t) = 100 \cos(2000t)$  THEN

$$V_s(s) = 100 \frac{s}{s^2 + (2k)^2}$$

$$= \frac{100s}{s^2 + 4(10^6)}$$

AND

$$V_o(s) = \frac{3k}{s^2(375\mu) + s(0.25) + 3k} V_s(s)$$

$$= \frac{3k}{s^2 + s(666.6) + 3(10^6)} \frac{100s}{s^2 + 4(10^6)}$$

## 10.3. Circuit Theorems in the S-Domain

### A) PROPORTIONALITY

- FOR LINEAR RESISTIVE CIRCUITS THE PROPORTIONALITY THEOREM OF CH 3 STATES THAT ANY OUTPUT  $y$  IS PROPORTIONAL TO THE INPUT  $x$ , THAT IS,

$$y = Kx$$

- THE SAME IS TRUE FOR S-DOMAIN CIRCUITS

$$Y(s) = K(s) X(s)$$

WHERE  $K(s)$  IS AN S-DOMAIN RATIONAL FUNCTION.

IT IS SOMETIMES CALLED A "NETWORK FUNCTION".

Network Function =  $\frac{\text{Output}}{\text{Input}}$

### C) SUPERPOSITION

- FOR LINEAR RESISTIVE CIRCUITS, THE SUPERPOSITION THEOREM OF CH.3 STATES THAT ANY OUTPUT  $y$  OF A LINEAR CIRCUIT CAN BE WRITTEN AS

$$y = K_1 x_1 + K_2 x_2 + \dots + K_n x_n$$


WHERE  $x_1, x_2, \dots, x_n$  ARE CIRCUIT INPUTS AND

$K_1, K_2, \dots, K_n$  ARE SCALE FACTORS THAT DEPEND ON THE CIRCUIT.

- THE SAME IS TRUE FOR S-DOMAIN CIRCUITS.  
WHERE  $K_1(s), K_2(s), \dots, K_n(s)$  ARE NETWORK FUNCTIONS.
- SUPERPOSITION ALSO APPLIES TO GROUPS OF SOURCES.  
SINCE INITIAL CONDITIONS WERE SHOWN TO BE SOURCES IN THE S-DOMAIN, WE COULD GROUP


## 10.4 Node-Voltage Analysis in the S-Domain

### A) EXAMPLE 10.3

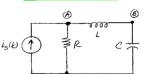

REARRANGE THE S-DOMAIN EQUATIONS BY INSPECTING FOR THIS CIRCUIT INCLUDING INITIAL CONDITIONS. FIND  $V_A(0)$

### B) CIRCUIT

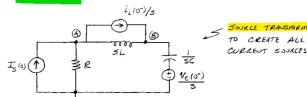

$$\begin{bmatrix} I_S - \frac{V_A(0)}{G} \\ \frac{V_A(0)}{L} + V_C(0)C \end{bmatrix} = \begin{bmatrix} G + \frac{1}{SL} & -\frac{1}{SL} \\ -\frac{1}{SL} & SC + \frac{1}{SL} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix}$$

$$V_A = \frac{\Delta A}{A} = \frac{\begin{vmatrix} I_S - \frac{V_A(0)}{G} & -\frac{1}{SL} \\ \frac{V_A(0)}{L} + V_C(0)C & SC + \frac{1}{SL} \end{vmatrix}}{\begin{vmatrix} G + \frac{1}{SL} & -\frac{1}{SL} \\ -\frac{1}{SL} & SC + \frac{1}{SL} \end{vmatrix}}$$

$$V_A = \frac{\Delta A}{A} = \frac{\begin{vmatrix} I_S & -\frac{1}{SL} \\ \frac{V_A(0)}{L} + V_C(0)C & SC + \frac{1}{SL} \end{vmatrix}}{\begin{vmatrix} G + \frac{1}{SL} & -\frac{1}{SL} \\ -\frac{1}{SL} & SC + \frac{1}{SL} \end{vmatrix}} = \frac{-I_S(SLC + 1) - V_C(0)(SLC) + V_C(0)C}{S^2 LCG + SC + G}$$

$$= \frac{(I_S - \frac{V_A(0)}{G})(SC + \frac{1}{SL}) - (-\frac{1}{SL})(\frac{V_A(0)}{G} + V_C(0)C)}{(G + \frac{1}{SL})(SC + \frac{1}{SL}) - (-\frac{1}{SL})(-\frac{1}{SL})}$$

$$= \frac{I_S(SC + \frac{1}{SL}) - I_L(0)(C + \frac{1}{SL} - \frac{1}{SL}) + V_C(0)\frac{C}{SL}}{SC + \frac{1}{SL} + \frac{C}{SL} + \frac{1}{SL} - \frac{1}{SL}}$$

$$= \frac{I_S(S^2 LC + 1) - I_L(0)(SLC) + V_C(0)C}{S^2 LCG + SC + G}$$

$$= \frac{I_S(S^2 LC + 1)}{S^2 LCG + SC + G} + \frac{-I_L(0)(SLC) + V_C(0)C}{S^2 LCG + SC + G}$$


ZERO-STATE  
RESPONSE

CIRCUIT DETERMINANT  
DUE TO ZERO  
INPUTS OR IC'S.

ZERO-INPUT  
RESPONSE


# 10.5 Mesh Current Analysis In the S-Domain

A) EXAMPLE

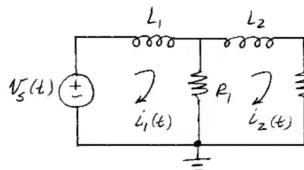


FORMULATE THE S-DOMAIN EQUATIONS BY INSPECTION INCLUDING INITIAL CONDITIONS

SOLUTION:

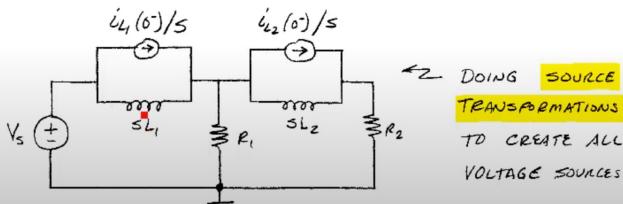


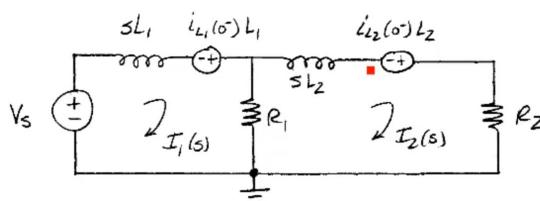DOING SOURCE TRANSFORMATIONS TO CREATE ALL VOLTAGE SOURCES



$$\begin{bmatrix} V_s + i_{L1}(0^-)L_1 \\ i_{L2}(0^-)L_2 \end{bmatrix} = \begin{bmatrix} sL_1 + R_1 & -R_1 \\ -R_1 & sL_2 + R_1 + R_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

10.6 FOR THE CIRCUIT SHOWN BELOW

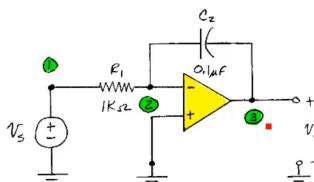

```

INTEGRATOR
VS 1 0 AC 2 -90 SIN (0 2 1K)
R1 1 2 1K
C2 2 0 .1U IC=0
EOP 3 0 0 2 100 MEG
.PROBE
.AC DEC 200 1K 10K
.TRAN 12.5U 2.5M 0 12.5U
.END

```

$$10^8 V_o \approx \infty \cdot V_x$$

RUN THE ABOVE PSPICE FILE AND COMPLETE:



One supplement pr

# S-Domain Conversion Order

8




## Element Transformations contd

Resistor

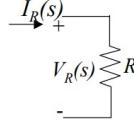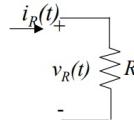

$$V_R(s) = RI_R(s)$$

Capacitor

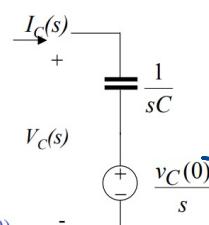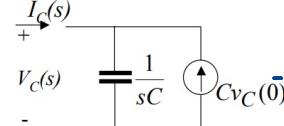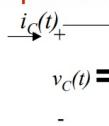




$$I_C(s) = sCV_C(s) - Cv_C(0^-) \quad V_C(s) = \frac{1}{sC}I_C(s) + \frac{v_C(0)}{s}$$

Note the source transformation rules apply!
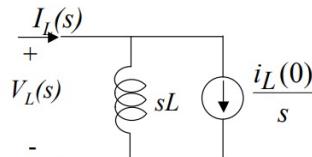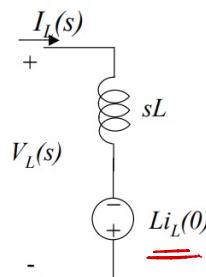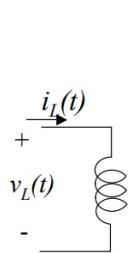
## Element Transformations contd

Inductors

$$V_L(s) = sLI_L(s) - Li_L(0) \quad I_L(s) = \frac{1}{sL}V_L(s) + \frac{i_L(0)}{s}$$



Complex power:  $\vec{I} = I_m \angle 0^\circ \quad \vec{I}^* = I_m \angle -90^\circ$

$$\vec{P} = \vec{V} \cdot \vec{I}^* = V_m I_m \angle \varphi_u - \varphi_i = V_m I_m \angle \varphi = V_m I_m \cos \varphi + j V_m I_m \sin \varphi = P + j Q$$

$$\vec{P} = \vec{V} \cdot \vec{I}^* = Z \vec{I} \cdot \vec{I}^* = Z \vec{I}^2 = (R + jX) \vec{I}^2 = R \vec{I}^2 + jX \vec{I}^2$$

$$\text{or } \vec{P} = \vec{V} \cdot \vec{I}^* = \vec{V} \cdot (\vec{V} \gamma)^* = \vec{V} \vec{\gamma}^* \cdot \vec{\gamma}^* = \vec{V} \vec{\gamma}^*$$

# Chapter 11: Network Functions

## 11.1 Definition of network function

$$\text{Network function} = T(s) = \frac{\text{zero-state response function}}{\text{input signal transform}} = \frac{Y(s)}{X(s)}$$


$$Y(s) = T(s) \cdot X(s) = \sum_{j=1}^N \frac{k_j}{s-p_j} + \sum_{\ell=1}^M \frac{k_\ell}{s-p_\ell}$$

$\underbrace{\hspace{1cm}}$        $\underbrace{\hspace{1cm}}$   
natural poles      forced poles

$$\Rightarrow y(t) = \sum_{j=1}^N k_j e^{p_j t} + \sum_{\ell=1}^M k_\ell e^{p_\ell t}$$


## 11.2 Network Functions of one & two Port Circuits

### (A) Driving point impedance.

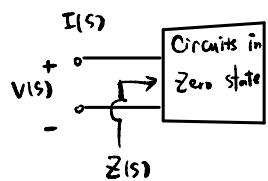

$$Z(s) = \frac{V(s)}{I(s)}$$

### (B) Transfer function

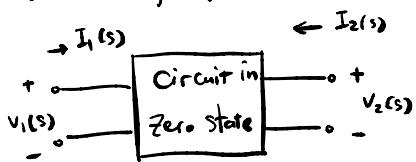

$$T_V(s) = \frac{V_2(s)}{V_1(s)}$$
 voltage transfer function

$$T_I(s) = \frac{I_2(s)}{I_1(s)}$$
 current transfer function

$$T_Y(s) = \frac{I_2(s)}{V_1(s)}$$
 transfer admittance

$$T_Z(s) = \frac{V_2(s)}{I_1(s)}$$
 transfer impedance

# 11.3 Network functions and Impulse response

"Impulse response" when input function  $x(t) = \delta(t)$ ,  $y(t) = h(t)$

$$Y(s) = H(s)$$

$$Y(s) = T(s) \cdot X(s) = T(s) \cdot 1 \stackrel{\Delta}{=} H(s)$$

$$\mathcal{L}\{h(t)\} = T(s) \quad Y(s) = \mathcal{L}^{-1}[H(s) \cdot X(s)]$$

在信号与系统或控制理论中，不同的符号各自有传统用途，但在不同的教材或论文里可能会出现一些符号混用或命名差异。以下是最常见的用法及其含义：

1.  $x(t), y(t)$

- 一般用于表示时域下的输入 (input) 信号和输出 (output) 信号。
- 相应地，它们的拉普拉斯变换通常记为\*\* $X(s), Y(s)**$ 。

2.  $h(t)$

- 一般表示系统的脉冲响应 (Impulse Response)，即当输入为单位冲激  $\delta(t)$  时，系统的输出信号。
- 它的拉普拉斯变换通常记为\*\* $H(s)**$ 。
- 有时在控制系统或某些场合，也可能把系统的脉冲响应记为  $g(t)$  或其他符号，但  $h(t)$  是最常见的约定。

3.  $H(s)$  或  $T(s)$  或  $G(s)$

- 在拉普拉斯域分析中，用于表示系统的传递函数 (Transfer Function)。
- 在“信号与系统”课程中，常用  $H(s)$  来代表系统函数；在“控制理论”中，可能更常见到  $G(s)$  或  $T(s)$  来表示系统的传递函数。
- 本质上，这些符号在功能上是等价的：都表示“输出对输入的拉普拉斯变换之比”，即

$$H(s) = \frac{Y(s)}{X(s)}$$

$$X(s) =$$

$$\mathcal{L}[x(t)] = 1$$

$$T(s) = H(s) = \frac{Y(s)}{X(s)} = Y(s)$$

拉普拉斯变化

$s \rightarrow$  differentiation.

$$\mathcal{L}[h(t)] = sH(s) - h(0)$$

$\frac{1}{s} \rightarrow$  integrator

$$\mathcal{L}\left[\int_0^t h(\tau) d\tau\right] = \frac{H(s)}{s}$$

## 11.4 Network function and Step response.

Step response: when input function  $x(t) = u(t)$ ,  $y(t) = g(t)$

$$Y(s) = T(s) \cdot X(s) = T(s) \cdot \frac{1}{s} = G(s) \quad Y(s) = G(s)$$

$$G(s) = \underbrace{\frac{k_0}{s}}_{\text{forced pole}} + \underbrace{\frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \dots + \frac{k_n}{s-p_n}}_{\text{natural pole}}$$

$$g(t) = \underbrace{k_0 u(t)}_{\text{forced response}} + \underbrace{\left[ k_1 e^{p_1 t} + k_2 e^{p_2 t} + \dots + k_n e^{p_n t} \right] u(t)}_{\text{natural response}}$$

## 11.6 Impulse response and Convolution

"Convolution"

$$y(t) = x(t) * h(t) = \int_{-\infty}^{\infty} x(\tau) \cdot h(t-\tau) d\tau$$

从图解: 由  $y(t) = h(t)$ ,  $x(t) = \delta(t)$ ,  $y(t) = h(t)$  来逆转换出  $T(s) = Y(s)$   
 把现在这个函数分无穷多个小块每一块  $\delta(t-\tau) = \delta(t) \cdot \delta(t-\tau)$

$$\text{若 } x(t) = u(t) \quad y(t) = g(t)$$

$$Y(s) = H(s) \cdot \frac{1}{s} \Rightarrow g(t) = \mathcal{L}^{-1} \left\{ \frac{H(s)}{s} \right\} = \int_0^t h(\tau) d\tau$$

$$\Rightarrow g(t) = \int_0^t h(\tau) d\tau \Leftrightarrow h(t) = \frac{d}{dt} g(t)$$

equivalence of S-Domain and t-domain Convolution.

$$Y(s) = H(s) \cdot X(s) = H(s) \left[ \int_0^\infty x(\uparrow) e^{-s\uparrow} d\uparrow \right] \sim \mathcal{L}[x(\uparrow)]$$

$$= \int_0^\infty [H(s) \cdot e^{-st}] \cdot x(t) dt$$

$$\cdot H(s) \cdot e^{-st} = \mathcal{L}[h(t-\uparrow) \cdot u(t-\uparrow)]$$

$$= \int_0^\infty h(t-\uparrow) u(t-\uparrow) \cdot e^{-st} dt$$

$$\therefore Y(s) = \int_0^\infty \left[ \int_0^\infty h(t-\uparrow) u(t-\uparrow) e^{-st} dt \right] x(\uparrow) d\uparrow$$

$$= \int_0^\infty \left[ \int_0^\infty h(t-\uparrow) u(t-\uparrow) x(\uparrow) d\uparrow \right] e^{-st} dt$$

$$= \int_0^\infty \left[ \int_0^t h(t-\uparrow) x(\uparrow) d\uparrow \right] e^{-st} dt$$

since  $u(t-\uparrow) = 0$

$t < \uparrow$   
 $\Rightarrow \uparrow > t$

$$\Rightarrow Y(s) = \mathcal{L} \left[ \int_0^t h(t-\uparrow) x(\uparrow) d\uparrow \right]$$

$$x(t) * h(t)$$

$$y(t) = \mathcal{L}^{-1}[Y(s)] = \mathcal{L}^{-1}[H(s) \cdot X(s)] = h(t) * x(t)$$

$$F_1(s) \cdot F_2(s) = \mathcal{L}[f_1(t) * f_2(t)]$$

$$\text{or } f_1(t) * f_2(t) = \mathcal{L}^{-1}[F_1(s) \cdot F_2(s)]$$

12-a

Frequency response

Review.  $s \leftrightarrow j\omega$ .  $T_v(s) = \frac{V_2(s)}{V_1(s)}$  or  $\frac{V_{out}(s)}{V_{in}(s)}$   $H(s) = T_v(s) \Big|_{V_1(s)=1}$   $G(s) = T_v(s) \Big|_{V_1(s)=\frac{1}{s}}$

Review of dB:

$$\Rightarrow G(s) = \frac{H(s)}{s}$$

Decibels (dB):  $Bel = 10 \log_{10} \left( \frac{P_{out}}{P_{in}} \right)$


Decibel (dB) =  $10 \log_{10} \left( \frac{P_{out}}{P_{in}} \right)$

Since  $P \propto V^2 \Rightarrow$  Decibel (dB) =  $10 \log_{10} \left( \frac{V_{out}}{V_{in}} \right)^2 = 20 \log_{10} \left( \frac{V_{out}}{V_{in}} \right)$



Power ratio:  $10 \log_{10} \left( \frac{P_{out}}{P_{in}} \right)$  . Voltage ratio:  $20 \log_{10} \left( \frac{V_{out}}{V_{in}} \right)$  Current ratio:  $20 \log_{10} \left( \frac{I_{out}}{I_{in}} \right)$

log Function

(a)  $F(j\omega) = K \Rightarrow |F|_{dB} = 20 \log(K)$

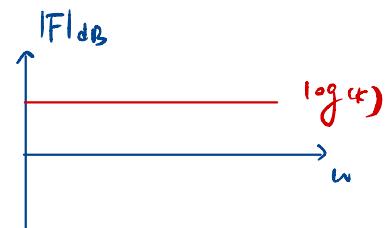


(b)  $F(j\omega) = j\omega \Rightarrow |F|_{dB} = 20 \log \sqrt{\omega^2 + \omega_0^2} = 20 \log(\omega)$

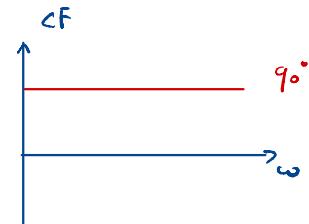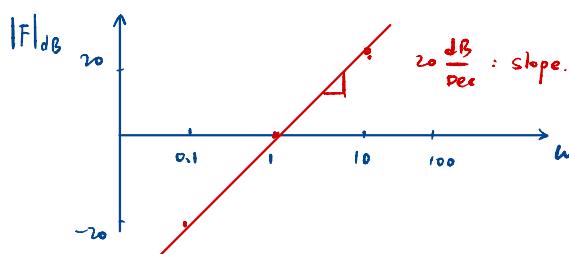

$<F = \tan^{-1} \left( \frac{\omega}{\omega_0} \right) = 90^\circ$

$$(c) F(s) = \frac{1}{s} \Rightarrow F(j\omega) = \frac{1}{j\omega}$$



$$|F|_{dB} = 20 \log |F| = 20(\log 1 - \log \omega) = -20 \log \omega$$

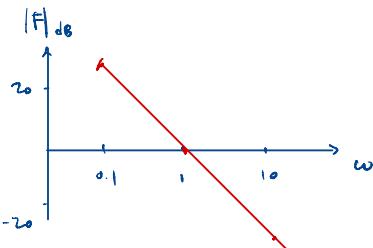

$$(d) F(j\omega) = 1 + j \frac{\omega}{\omega_c} \quad \omega_c = \text{constant.}$$

$$|F(j\omega)|_{dB} = 20 \log \sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}$$

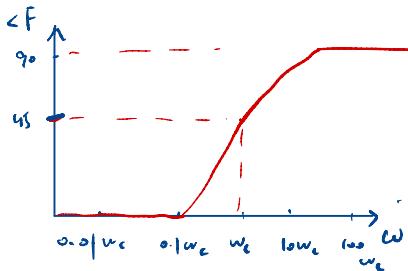
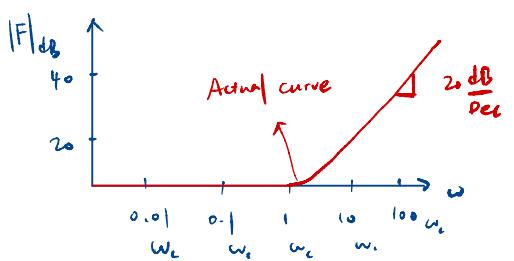
$$<F(j\omega) = \tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$



$$(e) F(j\omega) = \frac{1}{1 + j \frac{\omega}{\omega_c}}$$


$$|F(j\omega)|_{dB} = 20 \log(1) - 20 \log \sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2} = -20 \log \sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}$$
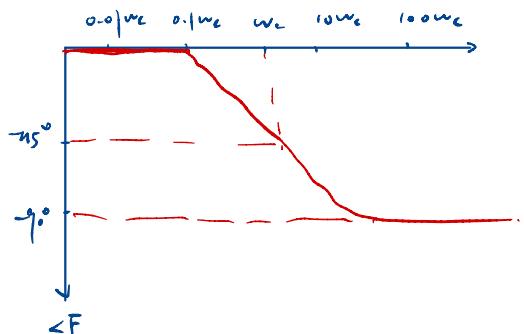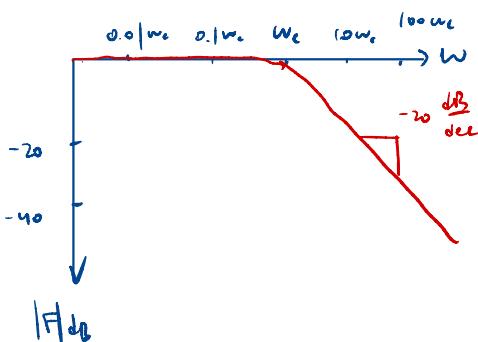
$$<F = \tan^{-1}(0) - \tan^{-1}\left(\frac{\omega}{\omega_c}\right) = \tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$





12-b

low-pass filter

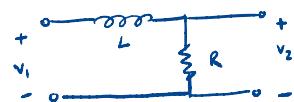

S-Domain

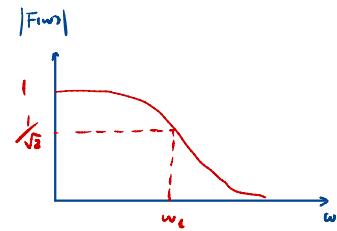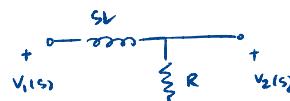

$$F(s) = \frac{V_2}{V_1} = \frac{R/L}{s + R/L}$$

$$F(j\omega) = \frac{R/L}{j\omega + R/L}$$


$$|F(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}}$$

$$\Theta(j\omega) = \tan^{-1}(0) - \tan^{-1}\left(\frac{\omega}{R/L}\right) = \tan^{-1}\left(\frac{\omega L}{R}\right)$$



$$|F(j\omega)| = \frac{R/L}{\sqrt{\omega_c^2 + (R/L)^2}} = \frac{1}{\sqrt{2}} |F(j\omega)|_{\max} = \frac{1}{\sqrt{2}} \frac{R/L}{\sqrt{\omega_c^2 + (R/L)^2}} \Rightarrow \boxed{\omega_c = \frac{R}{L}}$$

$$F(s) = \frac{\omega_c}{s + \omega_c}$$

high-pass filter

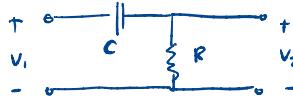

S-Domain

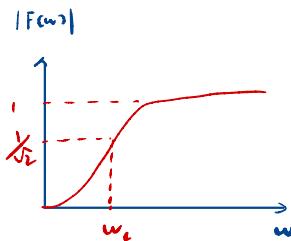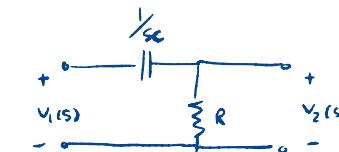

$$F(s) = \frac{V_2}{V_1} = \frac{R}{\frac{1}{sC} + R} = \frac{s}{s + \frac{1}{RC}}$$

$$F(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}}$$



$$|F(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (\frac{1}{RC})^2}}$$

$$\Theta(j\omega) = \tan^{-1}\left(\frac{\omega}{0}\right) - \tan^{-1}(\omega RC) = 90^\circ - \tan^{-1}(\omega RC)$$

$$|F(j\omega)| = \frac{\omega_c}{\sqrt{\omega_c^2 + (\frac{1}{RC})^2}} = \frac{1}{\sqrt{2}} \Rightarrow \boxed{\omega_c = \frac{1}{RC}}$$

$$F(s) = \frac{s}{s + \omega_c}$$

Band-Pass filter

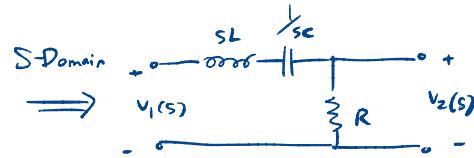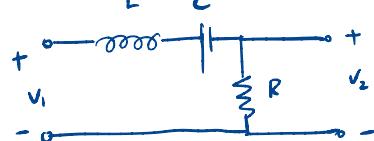

$$F(s) = \frac{v_2}{v_1} = \frac{R}{R + sL + \frac{1}{sC}} = \frac{\left(\frac{R}{L}\right) \cdot s}{s^2 + \left(\frac{R}{L}\right) \cdot s + \frac{1}{LC}} \Rightarrow F(j\omega) = \frac{j \left(\frac{R}{L}\right) \omega}{-\omega^2 + j \left(\frac{R}{L}\right) \omega + \frac{1}{LC}}$$

$$|F(j\omega)| = \frac{\omega \left(\frac{R}{L}\right)}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left[\omega \frac{R}{L}\right]^2}}$$

$$\theta(j\omega) = 90^\circ - \tan^{-1} \left[ \frac{\omega \left(\frac{R}{L}\right)}{\left(\frac{1}{LC}\right) - \omega^2} \right]$$

$$\frac{1}{LC} - \omega^2 = 0 \Rightarrow$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \sqrt{\omega_c \omega_{c2}}$$


$$|F(j\omega_0)| = \frac{1}{\sqrt{2}} |F(j\omega)_{\max}| = \frac{1}{\sqrt{2}} \Rightarrow$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$
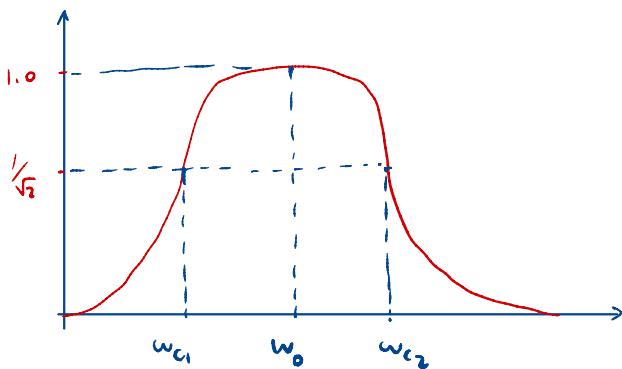
$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$


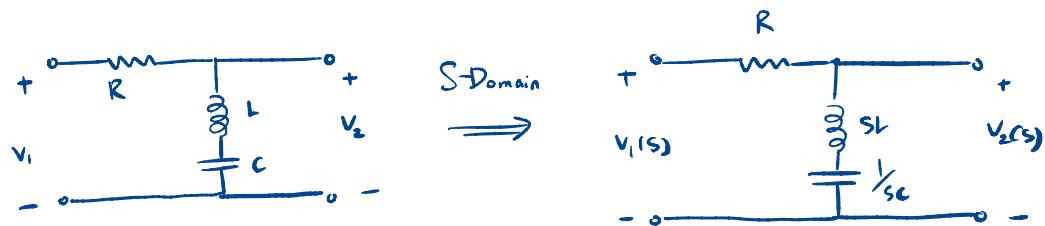
# Band-stop filter (or band rejected filter)



$$F(s) = \frac{V_2}{V_1} = \frac{sL + \frac{1}{sC}}{sL + \frac{1}{sC} + R} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \Rightarrow F(j\omega) = \frac{-\omega^2 + \frac{1}{LC}}{-\omega^2 + j\omega \frac{R}{L} + \frac{1}{LC}}$$

$$|F(j\omega)| = \frac{\left| \frac{1}{LC} - \omega^2 \right|}{\sqrt{\left[ \frac{1}{LC} - \omega^2 \right]^2 + \left[ \frac{\omega R}{L} \right]^2}} \quad \theta(j\omega) = -\tan^{-1} \left[ \frac{\frac{\omega R}{L}}{\frac{1}{LC} - \omega^2} \right]$$


$$\omega^2 - \frac{1}{LC} = 0 \Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}}$$

$$|F(j\omega_0)| = \frac{1}{\sqrt{2}} |F(j\omega)|_{\max} = \frac{1}{\sqrt{2}} \Rightarrow$$

$$\boxed{\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}}$$
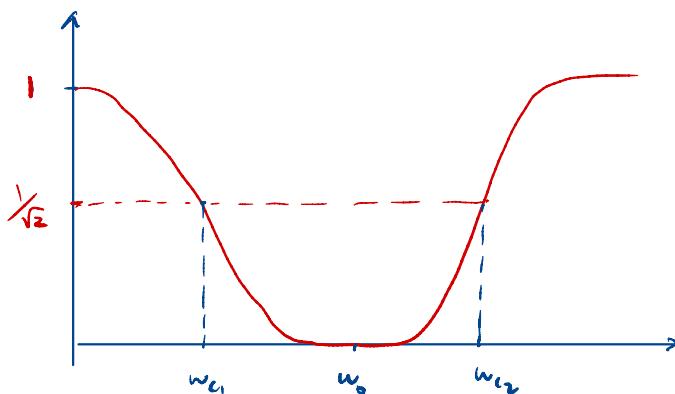
$$\boxed{\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}}$$



$$\text{Band width} = \omega_{c2} - \omega_{c1}$$

$$\text{Quality factor } Q = \frac{\sqrt{LC}}{R}$$

$$= \frac{\omega_0}{BW}$$

$$= \frac{\omega_{c1} + \omega_{c2}}{\omega_0}$$

13-a.

Frontier Series periodic function.


Suppose fits with a periodic  $T_0$ .  $T_0 = \frac{1}{f_0}$ , then we can deduct that:

$$f(t) = a_0 + \sum_{n=1}^{\infty} [a_n \cos(2\pi n f_0 t) + b_n \sin(2\pi n f_0 t)]$$

$$a_0 = \frac{1}{T_0} \int_{-T_0/2}^{T_0/2} f(t) dt \quad a_n = \frac{2}{T_0} \int_{-T_0/2}^{T_0/2} f(t) \cos\left(\frac{2\pi n t}{T_0}\right) dt \quad b_n = \frac{2}{T_0} \int_{-T_0/2}^{T_0/2} f(t) \sin\left(\frac{2\pi n t}{T_0}\right) dt$$

Quarter wave Periodic Symmetry

every  $\neq$  flip or symmetry

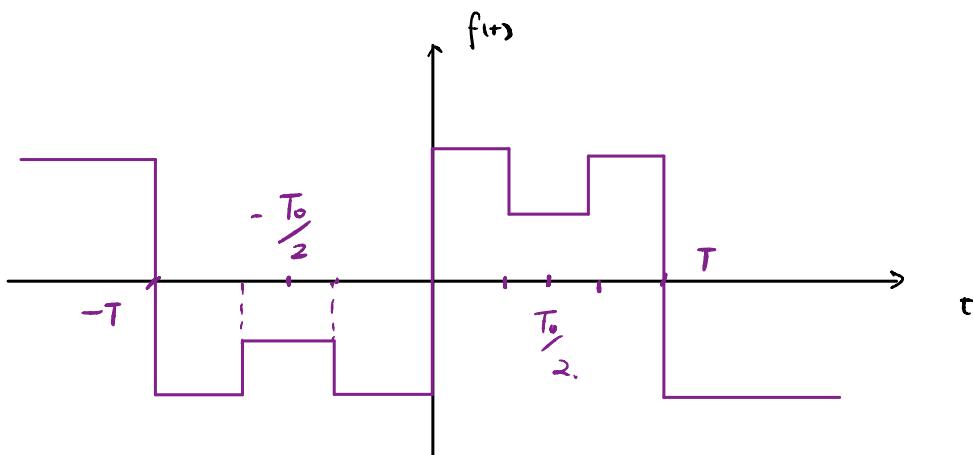

Half Wave Symmetry  $x(t + \frac{T}{2}) = -x(t)$

For even function

$$a_0 \neq 0 \quad a_n \neq 0 \quad b_n = 0$$

For odd function


$$a_0 = 0 \quad a_n = 0 \quad b_n \neq 0$$

15 a


$$\text{Flux} \quad \lambda = N \Phi.$$

$$\text{Voltage} \quad v = - \frac{d\lambda}{dt} = - N \frac{d\Phi}{dt} = - N \frac{d(Li)}{dt} = - NL \frac{di}{dt}$$


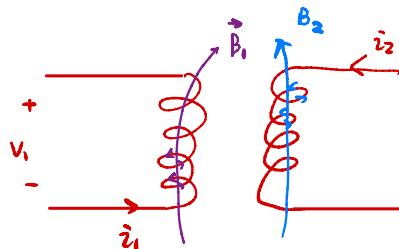
For mutual inductance  $v = -M \frac{di}{dt}$


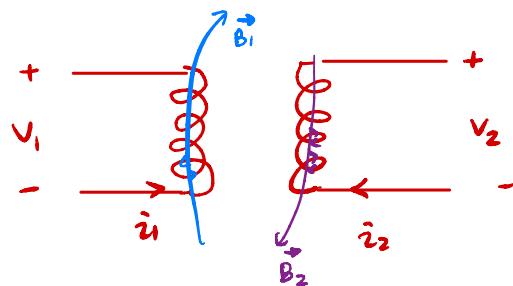
$$\left\{ \begin{array}{l} v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \\ v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} \end{array} \right.$$



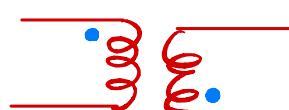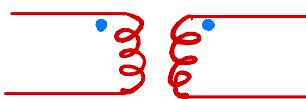
$$\left\{ \begin{array}{l} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{array} \right.$$



$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}.$$


$$v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

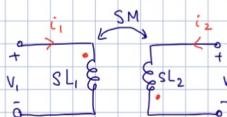on the frequency domain (Sinusoidal Steady State)



$$V_1 = S L_1 I_1(s) - S M I_2(s)$$


$$V_2 = S L_2 I_2(s) - S M I_1(s)$$

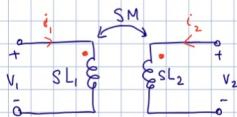

$$V_1 = S L_1 I_1(s) + S M I_2(s)$$

$$V_2 = S L_2 I_2(s) + S M I_1(s)$$

## ~~(c)~~) IDEAL TRANSFORMER

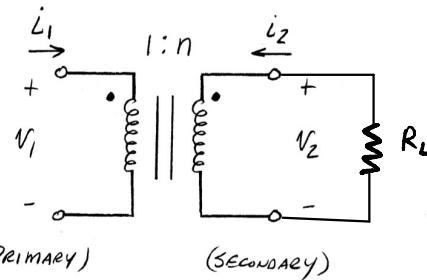

## Direction

$$V_2(t) = +n V_1(t)$$

$$i_2(t) = -\frac{1}{n} i_1(t)$$

$$V_2(t) = R_L \cdot (-i_2(t_1))$$

FOR THIS CASE :


$$\frac{V_2}{V_1} = +n \quad \notin \quad \frac{C_2}{C_1} = -\frac{1}{n}$$

$$\Rightarrow \frac{V_2(t)}{i_2(t)} = -R_L$$


$$\frac{V_1(t)}{z_1(t)} = \frac{\frac{1}{n}V_2(t)}{-niz_1(t)} = -\frac{1}{n^2} \left( \frac{V_2(t)}{z_1(t)} \right)$$

$$= - \frac{1}{n^2} (-R_L) = \frac{R_L}{n^2}$$

$$R_{EQ} = \frac{R_L}{\eta^2}$$


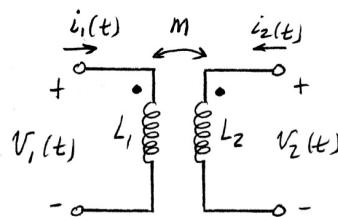


## TIME-DOMAIN CIRCUIT

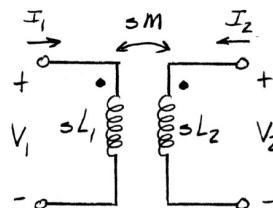

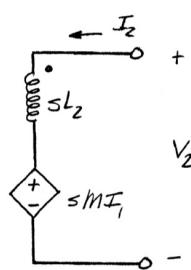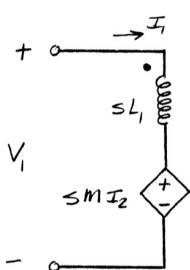
### 5-DOMAIN CIRCUIT

- THE S-DOMAIN EQUATIONS CAN BE MODELED AS THE FOLLOWING:




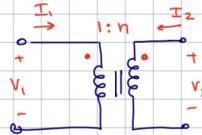The four possible configurations for an ideal transformer are:




$$I_2 = -\frac{I_1}{n}$$

$$V_2 = n V_1$$

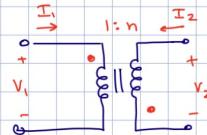


$$I_2 = \frac{I_1}{n}$$

$$V_2 = -n V_1$$

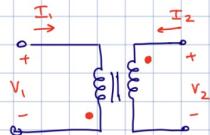

$$I_2 = \frac{I_1}{n}$$

$$V_2 = -n V_1$$

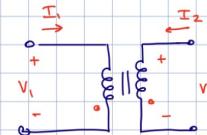

$$I_2 = -\frac{I_1}{n}$$

$$V_2 = n V_1$$

# Chapter 1b.

$$v(t) = V_A \cos(\omega t + \theta_v)$$

$\theta_v$  = voltage phasor angle.

$$i(t) = I_A \cos(\omega t + \theta_i)$$

$\theta_i$  = current phasor angle

$$\Rightarrow v(t) = I_A \cdot \cos(\omega t)$$

$$v(t) = V_A \cdot \cos(\omega t + \theta_v - \theta_i)$$

$$P = V_i = V_A \cdot I_A \cdot [\cos(\omega t + \theta_v - \theta_i)] [\cos(\omega t)]$$

tips:  $\cos \alpha \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$P = \frac{V_A \cdot I_A}{2} \left[ \cos((\omega t + \theta_v - \theta_i) - (\omega t)) + \cos((\omega t + \theta_v - \theta_i) + \omega t) \right]$$

$$= \frac{V_A \cdot I_A}{2} \left[ \cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v - \theta_i) \right]$$

$$= \underbrace{\frac{V_A I_A}{2} \cos(\theta_v - \theta_i)}_{DC Component} + \underbrace{\frac{V_A I_A}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) - \frac{V_A I_A}{2} \sin(\theta_v - \theta_i) \sin(2\omega t)}_{AC Component}$$

$$\Rightarrow P = P_{dc} + P \cos(2\omega t) - Q \sin(2\omega t)$$

$$P = \frac{V_A I_A}{2} \cos(\theta_v - \theta_i)$$



average power


$$Q = \frac{V_A I_A}{2} \sin(\theta_v - \theta_i)$$



reactive power


- For Purely resistive Circuits

$$P = P_{pc} + P \cdot \cos(2\omega t)$$

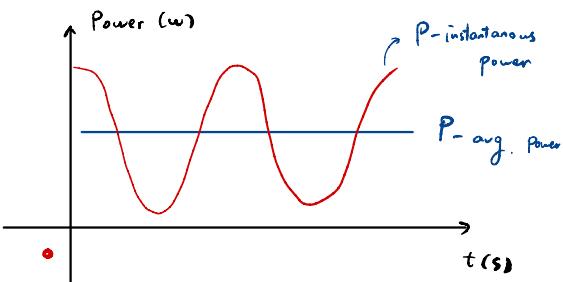


- For purely Inductive circuits

$$P = -Q \sin(2\omega t)$$

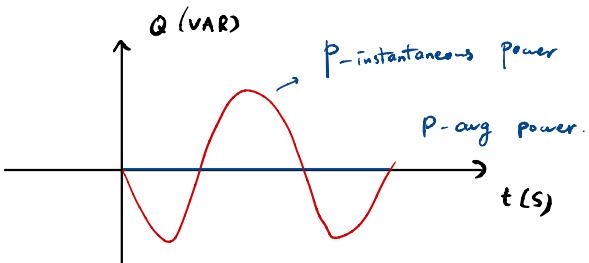

- For purely Capacitive power.

$$P = Q \cdot \sin(2\omega t)$$

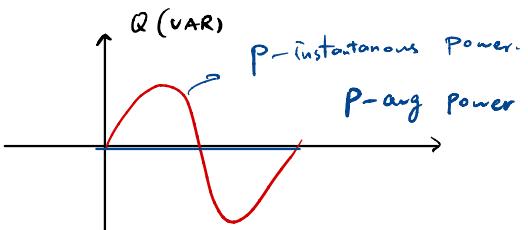

power factor.  $P_f = \cos(\theta_v - \theta_i)$

$$I_{rms} = \frac{I_A}{\sqrt{2}} \quad V_{rms} = \frac{V_A}{\sqrt{2}}$$

$$P = V_{rms} \cdot I_{rms} \cos(\theta_v - \theta_i)$$


$$Q = V_{rms} \cdot I_{rms} \cdot \sin(\theta_v - \theta_i)$$

Complex power S.

$$S = V \cdot I^* = V_{rms} \cdot I_{rms} \cdot e^{j(\theta_v - \theta_i)}$$

$$S = P + jQ = |S| \cdot \angle \theta \quad (\omega)$$
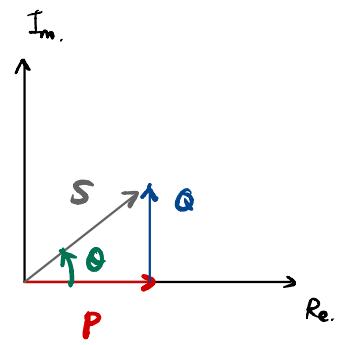
$$\theta = \tan^{-1}\left(\frac{Q}{P}\right)$$



$\theta = \theta_v - \theta_i > 0 \Rightarrow$  lagging power factor. (Inductive)

$\theta = \theta_v - \theta_i < 0 \Rightarrow$  leading power factor (Capacitive)


$$|S| = V_{rms} \cdot I_{rms}$$

$$P = V_{rms} \cdot I_{rms} \cos \theta$$

$$Q = V_{rms} \cdot I_{rms} \sin \theta$$

$$\underline{Z} = \frac{P + jQ}{I_{rms}^2}$$

# Three Phase Circuit.

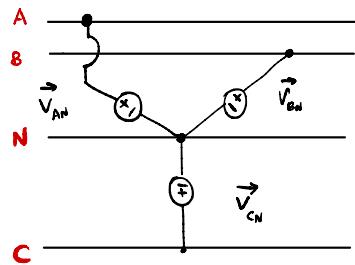

$$\vec{V}_{AB} = \vec{V}_{AN} - \vec{V}_{BN}$$

$$\vec{V}_{BC} = \vec{V}_{BN} - \vec{V}_{CN}$$

$$\vec{V}_{CA} = \vec{V}_{CN} - \vec{V}_{AN}$$

A "Balanced three phase source" produces phase voltage that satisfy :

$$|\vec{V}_{AN}| = |\vec{V}_{BN}| = |\vec{V}_{CN}| = V_p$$

$$V_L = \sqrt{3} V_p$$


And.  $\vec{V}_{AN} + \vec{V}_{BN} + \vec{V}_{CN} = 0 + j \cdot 0$

① positive phase (ABC)

$$\vec{V}_{AN} = V_p \angle 0^\circ$$

$$\vec{V}_{BN} = V_p \angle -120^\circ$$

$$\vec{V}_{CN} = V_p \angle -240^\circ$$

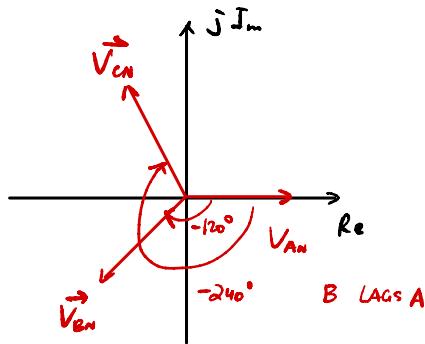


② Negative phase

$$\vec{V}_{AN} = V_p \angle 0^\circ$$

$$\vec{V}_{CN} = V_p \angle -120^\circ$$

$$\vec{V}_{BN} = V_p \angle -240^\circ$$

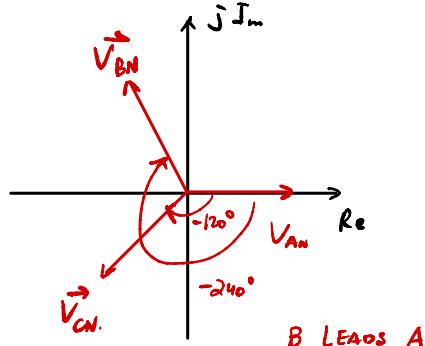


## RELATIONSHIPS \*


$$\begin{aligned}
 \vec{V}_{AB} &= \vec{V}_{AN} - \vec{V}_{BN} \\
 &= V_p \angle 60^\circ - V_p \angle -120^\circ \\
 &= V_p (1+j0) - V_p \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) \\
 &= V_p \left(\frac{3}{2} + j\frac{\sqrt{3}}{2}\right) = \sqrt{3} V_p \left(\frac{\sqrt{3}}{2} + j\frac{1}{2}\right) \\
 &= \underline{\sqrt{3} V_p \angle 30^\circ}.
 \end{aligned}$$

$$\begin{aligned}
 \vec{V}_{BC} &= \vec{V}_{BN} - \vec{V}_{CN} \\
 &= V_p \angle -120^\circ - V_p \angle -240^\circ \\
 &= V_p \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) - V_p \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) \\
 &= V_p (0 - j\sqrt{3}) \\
 &= \underline{\sqrt{3} V_p \angle -90^\circ}.
 \end{aligned}$$

$$\begin{aligned}
 \vec{V}_{CA} &= \vec{V}_{CN} - \vec{V}_{AN} & \Leftarrow & \\
 &= V_p \angle 240^\circ - V_p \angle 0^\circ & \Leftarrow & \\
 &= V_p \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) - V_p (1+j0) & \Leftarrow & \\
 &= V_p \left(-\frac{3}{2} + j\frac{\sqrt{3}}{2}\right) = \sqrt{3} V_p \left(-\frac{\sqrt{3}}{2} + j\frac{1}{2}\right) \\
 &= \underline{\sqrt{3} V_p \angle -210^\circ}.
 \end{aligned}$$

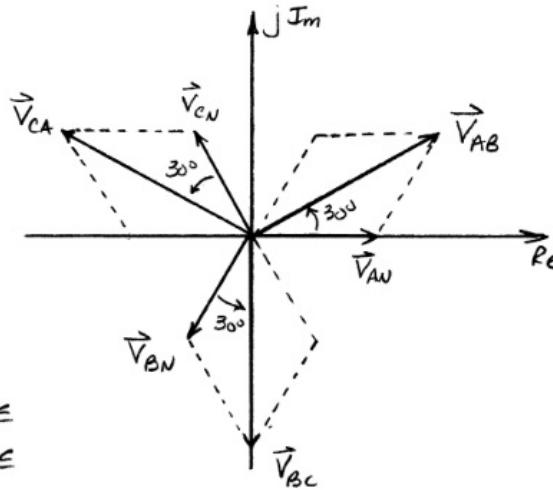

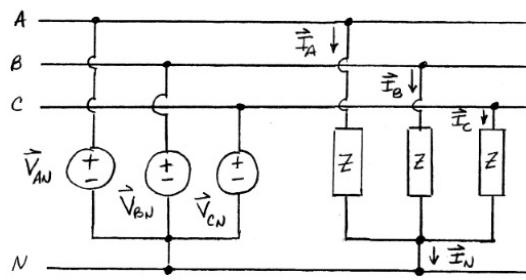
# $\text{Y}$ -Connected Source & $\text{Y}$ , Load



$\text{Y}$  电压 $\sqrt{3}$ 倍 电流不变


$\Delta$  电压不变 电流 $\sqrt{3}$ 倍

$$\begin{aligned}\vec{I}_A &= \frac{\vec{V}_{AN}}{Z} = \frac{V_p \angle 0^\circ}{|Z| \angle \theta} = \frac{V_p}{|Z|} \angle -\theta \quad \rightarrow I_L \\ \vec{I}_B &= \frac{\vec{V}_{BN}}{Z} = \frac{V_p \angle -120^\circ}{|Z| \angle \theta} = \frac{V_p}{|Z|} \angle -120^\circ - \theta \\ \vec{I}_C &= \frac{\vec{V}_{CN}}{Z} = \frac{V_p \angle -240^\circ}{|Z| \angle \theta} = \frac{V_p}{|Z|} \angle -240^\circ - \theta\end{aligned}\left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{array}{l} I_L = \frac{V_p}{|Z|} \\ \text{For A} \\ \text{Y-CONNECTED} \\ \text{LOAD} \end{array}$$

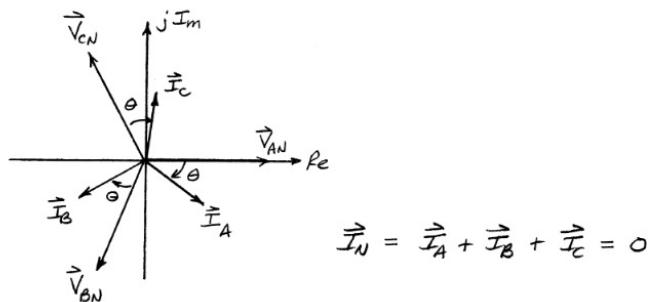

$$\begin{aligned}\vec{I}_L &= \vec{V}_{AN} \cdot \vec{I}_A^* + \vec{V}_{BN} \cdot \vec{I}_B^* + \vec{V}_{CN} \cdot \vec{I}_C^* \\ &= (V_p \angle 0^\circ) (I_L \angle \theta) + (V_p \angle -120^\circ) (I_L \angle 120^\circ + \theta) \\ &\quad + (V_p \angle -240^\circ) (I_L \angle 240^\circ + \theta) \\ &= V_p I_L \angle \theta + V_p I_L \angle \theta + V_p I_L \angle \theta \\ &= \boxed{3 V_p I_L \angle \theta} \\ &= 3 \frac{V_L}{\sqrt{3}} I_L \angle \theta = \boxed{\sqrt{3} V_L I_L \angle \theta}\end{aligned}$$
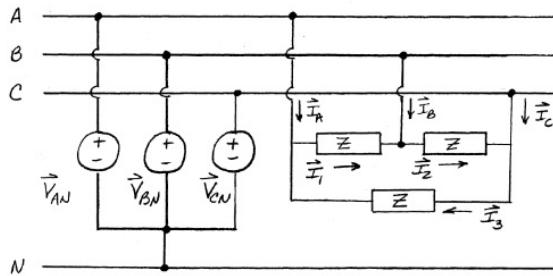
# Y Connected Source & $\Delta$ Circuit Source



CE 202 e-Notes.....Copyright © 2021 by Gregory M. Wierzba. All rights reserved.....Summer 2021.

(29)

- TO FIND THE TOTAL COMPLEX POWER WE NEED  
TO SOLVE FOR THE PHASE CURRENTS  $\vec{I}_1$ ,  $\vec{I}_2$  &  $\vec{I}_3$

$$\begin{aligned}\vec{I}_1 &= \frac{\vec{V}_{AB}}{Z} = \frac{V_L \angle 30^\circ}{|Z| \angle \theta} = \left( \frac{V_L}{|Z|} \right) \angle 30^\circ - \theta \\ \vec{I}_2 &= \frac{\vec{V}_{BC}}{Z} = \frac{V_L \angle -90^\circ}{|Z| \angle \theta} = \left( \frac{V_L}{|Z|} \right) \angle -90^\circ - \theta \\ \vec{I}_3 &= \frac{\vec{V}_{CA}}{Z} = \frac{V_L \angle -210^\circ}{|Z| \angle \theta} = \left( \frac{V_L}{|Z|} \right) \angle -210^\circ - \theta\end{aligned}\quad \left. \begin{array}{l} I_p = \frac{V_L}{|Z|} \\ \text{FOR A} \\ \Delta\text{-CONNECTED} \\ \text{LOAD} \end{array} \right\}$$

$$\begin{aligned}S_L &= \vec{V}_{AB} \cdot \vec{I}_1^* + \vec{V}_{BC} \cdot \vec{I}_2^* + \vec{V}_{CA} \cdot \vec{I}_3^* \\ &= (V_L \angle 30^\circ)(I_p \angle -30^\circ + \theta) + (V_L \angle -90^\circ)(I_p \angle 90^\circ + \theta) \\ &\quad + (V_L \angle -210^\circ)(I_p \angle 210^\circ + \theta) \\ &= V_L I_p \angle \theta + V_L I_p \angle \theta + V_L I_p \angle \theta \\ &= \boxed{3 V_L I_p \angle \theta}\end{aligned}$$


## BALANCED THREE-PHASE SYSTEM

Possible Three-Phase Load Configurations:

For a balanced wye-connected load,

$$Z_1 = Z_2 = Z_3 = Z_Y$$

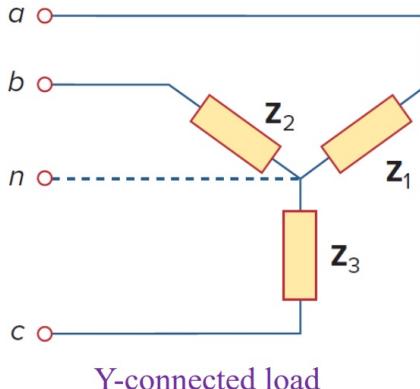where  $Z_Y$  is the load impedance per phase.



28

## BALANCED THREE-PHASE SYSTEM

Possible Three-Phase Load Configurations:


For a balanced delta-connected load,

$$Z_a = Z_b = Z_c = Z_\Delta$$

where  $Z_\Delta$  is the load impedance per phase.

Impedance relation between Y and  $\Delta$  connected load:
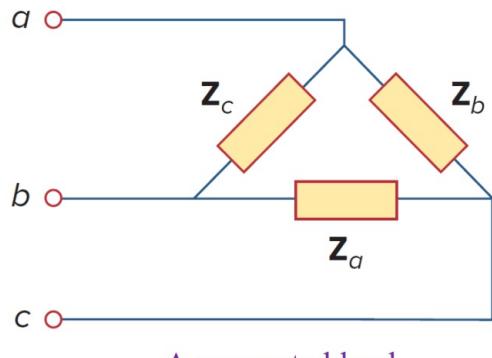
$$Z_\Delta = 3 \times Z_Y \quad \text{or} \quad Z_Y = \frac{1}{3} \times Z_\Delta$$



29