

1. 0 Since the switch is off
2. The DMM voltage shows the same value as the internal power supply voltage.  
Which is  $2.4930\text{ V}$
3.  $I_{\text{load}} = \frac{V_{\text{load}}}{R} = 2.0\text{ V} / 10\ \Omega = \underline{0.2\text{ A}}$
4.  $R_s = \frac{V_{\text{open}} - V_{\text{load}}}{I_{\text{load}}} = (2.5\text{ V} - 2.0\text{ V}) / 0.25\text{ A} = \underline{2\ \Omega}$
5.  $P_{\text{max}} = \frac{V_{\text{open}}^2}{4R_s} = \underline{0.78125\text{ W}}$
6.  $P_{\text{actual}} = V_{\text{open}} \times I_{\text{max}} = 2.5\text{ V} \times 500\text{ mA} = 1.25\text{ W}$   
 $P_{\text{max}} = 0.78125\text{ W} < P_{\text{actual}} = 1.25\text{ W} \Rightarrow \underline{\text{No}}$ , not able to deliver
7.  $R_{\text{bottom}} = \left( \frac{1\text{ M} \times 330\text{ k}}{1\text{ M} + 330\text{ k}} \right) \Omega = 248\text{ k}\Omega$   
 $V_{\text{node2}} = \frac{R_{\text{bottom}}}{R_{\text{bottom}} + R_{\text{top}}} V_{\text{ac}} = \left( \frac{0.248\text{ M}}{0.248\text{ M} + 1\text{ M}} \right) \times 240\text{ V}_{\text{rms}} = \underline{47.69\text{ V}_{\text{rms}}}$
8.  $V_{\text{input}} = 240\text{ V}$   $R_{\text{top}} = 10\text{ k}\Omega$   $R_{\text{bottom}} = 25.6\text{ k}\Omega$   
 $R_{\text{total}} = R_{\text{top}} + R_{\text{bottom}} = 35.6\text{ k}\Omega$   $P = \frac{V_{\text{input}}^2}{R_{\text{total}}} = \frac{(240\text{ V})^2}{(35.6\text{ k}\Omega)} = \underline{1.62\text{ W}}$
9.  $R_{\text{eq10x}} = \left( \frac{330\text{ k} \times 9\text{ M}}{330\text{ k} + 9\text{ M}} \right) = 318.4\text{ k}\Omega$   $V_{\text{node2}} = \left( \frac{318.4\text{ k}\Omega}{318.4\text{ k}\Omega + 1\text{ M}\ \Omega} \right) \times 240\text{ V}_{\text{rms}} = \underline{57.94\text{ V}_{\text{rms}}}$
10. The oscillation range is  $150\text{ V}_{\text{rms}}$ ,  $57.94\text{ V}_{\text{rms}} < 150\text{ V}_{\text{rms}} \Rightarrow \underline{\text{Within}}$