

### Post-lab 3. Xiangbo Cai

1. Yes. the voltage follower should have produced  $590\text{mV}$  based on our calculation and it did matched the data we observe

2. The op-amp has an output voltage swing limitation due to internal transistor. Therefore, the output voltage will drop and not reach  $+15\text{V}/-15\text{V}$


3. Based on my data.  $\frac{V_2}{V_1} = \frac{1.37}{1.93} = 0.71 \Rightarrow \text{dB} = 20 \log_{10}(0.71) = -2.97 \text{ dB} \approx -3 \text{ dB}$

This is very close to  $-3 \text{ dB}$ , just expected as cutoff frequency

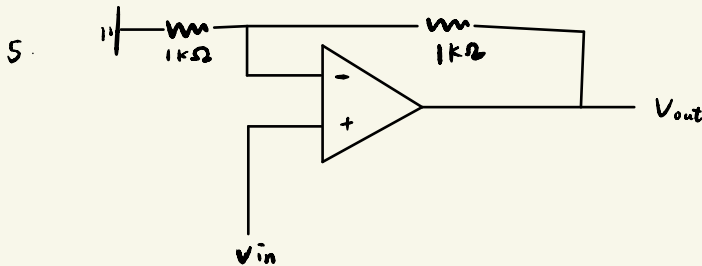4. No. it's not wise to do that.

At cutoff frequency, the filter's amplitude is already reduced by  $3 \text{ dB}$

That means your  $10 \text{ kHz}$  signal would be noticeably attenuated and phase-shifted



Extra Credit:

By definition  $dB = 10 \log_{10} \left( \frac{P_2}{P_1} \right)$   $P_2, P_1$  are power level

$$\text{Since } P = \frac{V^2}{R} \Rightarrow \frac{P_2}{P_1} = \frac{V_2^2/R}{V_1^2/R} = \left( \frac{V_2}{V_1} \right)^2$$

$$\Rightarrow dB = 10 \log_{10} \left( \frac{P_2}{P_1} \right) = 10 \log_{10} \left( \left( \frac{V_2}{V_1} \right)^2 \right) = 20 \log_{10} \left( \frac{V_2}{V_1} \right)$$

$$\text{Therefore voltage in dB} = 20 \log_{10} \left( \frac{V_2}{V_1} \right)$$