

ECE 201: Circuit & System I

Chapter 1:

SI system.

1) Length	m	4) Ampere	A
2) Mass	kg	5) Temperature	K
3) Time	s	6) Luminous intensity	Cd
		7) Voltage	V

A) Current

$$i = \frac{d\phi}{dt}$$

B) voltage

$$V = \frac{dw}{dq_f}$$

c) energy

$$p = \frac{dw}{dt} = \left(\frac{dw}{dq_f} \right) \cdot \left(\frac{dq_f}{dt} \right) = V \cdot i$$

$$\int_{t_0}^{t_1} p dt = \int_{t_0}^{t_1} \frac{dw}{dt} dt = \int_{t_0}^{t_1} dw = w(t_1) - w(t_0)$$

$$\therefore \Delta w = w(t_1) - w(t_0) = \int_{t_0}^{t_1} p dt$$

$$w(t_1) = \int_{t_0}^{t_1} p dt + w(t_0)$$

ECE 201: Circuit & System I

Chapter 1:

SI system.

1) Length	m	4) Ampere	A
2) Mass	kg	5) Temperature	K
3) Time	s	6) Luminous intensity	Cd
		7) Voltage	V

A) Current

$$i = \frac{d\phi}{dt}$$

B) voltage

$$V = \frac{dw}{dq_f}$$

c) energy

$$p = \frac{dw}{dt} = \left(\frac{dw}{dq_f} \right) \cdot \left(\frac{dq_f}{dt} \right) = V \cdot i$$

$$\int_{t_0}^{t_1} p dt = \int_{t_0}^{t_1} \frac{dw}{dt} dt = \int_{t_0}^{t_1} dw = w(t_1) - w(t_0)$$

$$\therefore \Delta w = w(t_1) - w(t_0) = \int_{t_0}^{t_1} p dt$$


$$w(t_1) = \int_{t_0}^{t_1} p dt + w(t_0)$$

* Standard Decimal Prefixes

10^{-18}	atto	a	10^3	milli	m
10^{-15}	fento	f	10^3	kilo	K
10^{-12}	pico	p	10^6	mega	M
10^{-9}	nano	n	10^9	giga	G
10^{-6}	micro	μ	10^{12}	tera	T

tips: when convert, the value should be 1~1000

(D) Passive Sign Convention

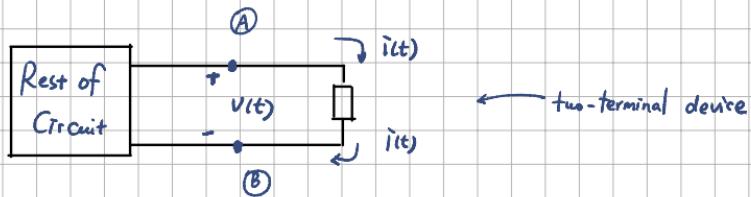


(1) If $u(t)$ & $i(t)$ is positive

- (a) A voltage drop exists from terminal (A) to terminal (B)
- (b) A voltage rise exists from terminal (B) to terminal (A)
- (c) A net positive charge is flowing from terminal (A) to terminal (B) in circuit
- (d) A net negative charge is flowing from terminal (B) to terminal (A) in circuit

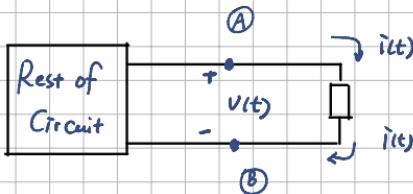(2) If current move through a drop in voltage. it charges lose energy

If current move through a rise in voltage. it charges gain energy



Charges gain energy. Power is generated ; Charges lose energy, power is absorbed

(3) Power Absorbed


- whenever the reference direction of current into a two-terminal device is in the direction of the reference voltage drop across the device then the power absorbed or dissipated is positive

$$P(t) = V(t) \cdot i(t) > 0 \quad (\text{Absorbed})$$

$$P(t) = V(t) \cdot \bar{i}(t) < 0 \quad (\text{Generated})$$


Q Negative power absorbed means power is generated

Q : Find Power absorbed/generate

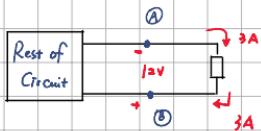

Solution :

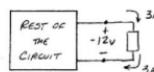
- REDRAWING THE CIRCUIT TO LOOK LIKE passive sign convention



$$\begin{aligned} \text{POWER ABSORBED} &= P \\ &= [-12V] [3A] = [-36W] \end{aligned}$$

Negative Power
Absorbed means
Power is Generated.

- (Q2) we could do the following

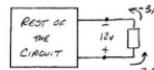

$$\begin{aligned} \text{POWER ABSORBED} &= P \\ &= [12V] [-3A] = [-36W] \end{aligned}$$

CURRENT IS ENTERING THE + TERMINAL WHICH IS THE DEFINITION OF POWER ABSORBED

Ground.

- Since voltage exists between two points it is often useful to define a common voltage reference point called ground.

- Common Symbols: $\frac{1}{=}$ or $\textcircled{1}$ or $\textcircled{\Delta}$

1) EXAMPLE


$$\begin{array}{c} V_A(t) \quad V_B(t) \quad V_C(t) \\ \bullet \qquad \bullet \qquad \bullet \\ \textcircled{A} \qquad \textcircled{B} \qquad \textcircled{C} \end{array} \qquad \qquad \begin{array}{c} \textcircled{A} \qquad \textcircled{B} \qquad \textcircled{C} \\ \bullet \qquad \bullet \qquad \bullet \\ + \qquad + \qquad + \end{array} \triangleq \begin{array}{c} V_A(t) \quad V_B(t) \quad V_C(t) \\ - \frac{\bullet}{\textcircled{1}} - \\ \textcircled{5} \end{array}$$

Ground (cont.)

- THE GROUND OR COMMON POINT IS ASSUMED TO BE THE - TERMINAL.
- A TWO TERMINAL DEVICE MAY BE BETWEEN POINTS \textcircled{A} AND $\textcircled{5}$ OR MAY NOT BE.
- ALTHOUGH WE ARE ASSIGNING A POLARITY TO V_A , V_B , V_C , THEIR ACTUAL VALUE MAY BE NEGATIVE.

Conservation of Power

i) EXAMPLE : GIVEN

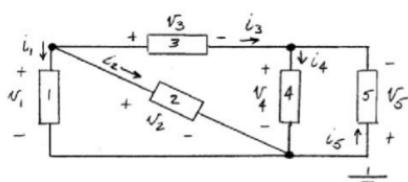

$p, v, \text{ and } i$ are related:

$$p = v * i$$

Also note passive sign convention

WHERE THE FOLLOWING QUANTITIES WERE MEASURED:

	DEVICE 1	DEVICE 2	DEVICE 3	DEVICE 4	DEVICE 5
V	+100V	?	+25V	+75V	-75V
I	?	+5mA	+5mA	?	+5mA
P	-1W	+500mW	?	+750mW	?

a) FIND THE MISSING QUANTITY

b) SUM THE ABSORBED POWER

SOLUTION:

$$i_1 = \frac{P_1}{V_1} = \frac{-1}{100} = [-10mA]$$

* Change i_1 to positive.

also need change direction

$$V_2 = \frac{P_2}{I_2} = \frac{500m}{5m} = [100V]$$

$$P_3 = V_3 i_3 = (25)(5m) = [125mW]$$

$$i_4 = \frac{P_4}{V_4} = \frac{750m}{75} = [10mA]$$

$$P_5 = V_5 i_5 = (-75)(5m) = [-375mW]$$

We could say that P1 and P5 generated 1.375 W and that P2, P3 and P4 absorbed 1.375 W.

b)

$$P_1 = -1W$$

$$P_2 = 0.5W$$

$$P_5 = -0.375W$$

$$P_3 = 0.125W$$

$$\hline -1.375W$$

$$P_4 = 0.750W$$

$$\hline 1.375W$$

May be, P1 and P5 are voltage sources and P2, P3 and P4 are resistances.

$$\sum \text{Power ABSORBED} = [0W]$$

Postulates

- Postulates are things that are assumed to be true. Given a set of postulates we can then derive theorems or properties

(a) Conservation of energy postulate

Energy cannot be created or destroyed. Although it can be changed from one to another, that is

$$\sum w_{\text{absorb}} = \sum w_{\text{generate}}$$

$$\sum_{i=1}^j \int p_{\text{absorb}} \cdot dt = \sum_{i=j+1}^n \int p_{\text{generate}} \cdot dt$$

$$\int \sum_{i=1}^j p_{\text{absorb}} \cdot dt = \int \sum_{i=j+1}^n p_{\text{generate}} \cdot dt$$

$$\therefore \sum_{i=1}^j p_{\text{absorb}} \cdot dt = \sum_{i=j+1}^n p_{\text{generate}} \cdot dt$$

QED *

⇒ Conservation of power

In a circuit. $\sum_{i=1}^n P_{AB_i} = 0$



one device

Supplemental Problems

51.1) THE CURRENT THROUGH A CIRCUIT ELEMENT IS 20mA. IF THE CHARGE OF 1 ELECTRON IS 1.6×10^{-19} C THEN THERE ARE $1/1.6 \times 10^{-19} = 6.25 \times 10^{18}$ ELECTRONS IN 1 COULOMB OF CHARGE.

FIND THE TOTAL CHARGE AND THE NUMBER OF ELECTRONS TRANSFERRED DURING AN INTERVAL OF $1\mu s$.

SOLUTION:


$$i = \frac{dq}{dt} \Rightarrow \int_{t_0}^{t_1} i dt = \int_{t_0}^{t_1} \frac{dq}{dt} dt = \int_{t_0}^{t_1} dq = q(t_1) - q(t_0)$$

- THIS IS THE TOTAL CHARGE TRANSFERRED* BETWEEN t_0 & t_1 ,

a) $\therefore \Delta q = \int_{t_0}^{t_1} i dt = \int_0^{1\mu s} (20m) dt = 20m(1\mu s) = [20nC]$

b) NUMBER OF ELECTRONS $\stackrel{\Delta}{=} n_E = 6.25(10^{18}) \frac{\text{ELECT}}{\text{C}} \cdot 20nC$
 $= [125(10^9)] \text{ ELECTRONS}$

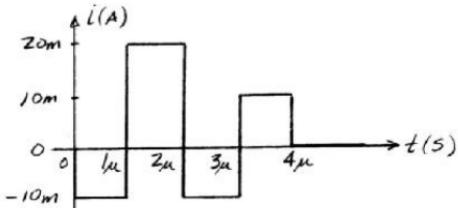51.2) GIVEN A PLOT OF CURRENT FLOWING PAST A REFERENCE POINT VERSUS TIME, PLOT THE CHARGE TRANSFERRED PAST THE REFERENCE POINT VERSUS TIME IF $q(0) = 0$ C.



SOLUTION: $q(t) = \int_{t_0}^t i(x) dx + q(t_0)$

a) $0 \leq t \leq 1\mu s$

$$q(t) = \int_0^t (-10m) dx + 0 = (-10m) \times \int_0^t 1 = -10m t$$

$\therefore q(1\mu s) = (-10m)(1\mu s) = -10nC$ \Rightarrow INITIAL CONDITION FOR THE NEXT TIME INTERVAL

b) $1\mu \leq t \leq 2\mu$

$$\begin{aligned}g(t) &= \int_{1\mu}^t (20m) dx + (-10n) = 20m(t - 1\mu) - 10n \\&= 20m t - 20m - 10n = (20m)t - 30n \quad \notin g(2\mu) = 10nC\end{aligned}$$

c) $2\mu \leq t \leq 3\mu$

$$\begin{aligned}g(t) &= \int_{2\mu}^t (-10m) dx + 10n = (-10m)(t - 2\mu) + 10n \\&= (-10m)t + 20m + 10n = (-10m)t + 30n \quad \notin g(3\mu) = 0C\end{aligned}$$



d) $3\mu \leq t \leq 4\mu$

$$\begin{aligned}g(t) &= \int_{3\mu}^t (10m) dx + 0 = 10m(t - 3\mu) \\&= 10m t - 30n \quad \notin g(4\mu) = 10nC\end{aligned}$$


e) $t \geq 4\mu$

$$g(t) = \int_{4\mu}^t 0 dt + 10n = 10nC$$

- GRAPHING THE RESULTS

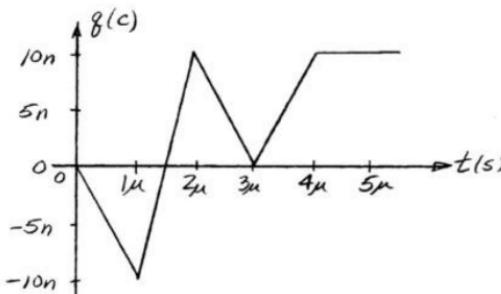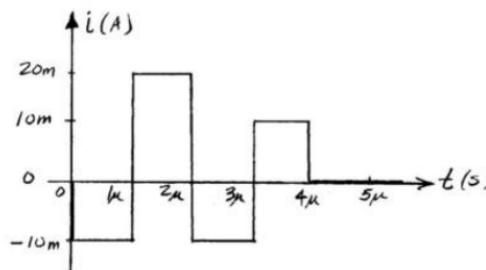

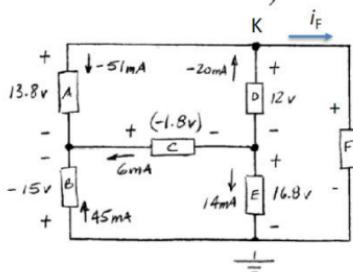51.4) USE THE CONSERVATION OF POWER TO FIND THE POWER ABSORBED BY ELEMENT F



Check:
 $V_F = 16.8 + 12 = 28.8 \text{ V}$
 $i_F = 892.8 \text{ m} / 28.8$
 $= 31 \text{ mA}$

Alternative:
KCL: $i_F = -20\text{m} - (-51\text{m})$
@K $= 31 \text{ mA}$

Power = $28.8 \times 31 \text{ mW}$
 $= 892.8 \text{ mW}$


SOLUTION: $\sum P_{AB} = 0$

a) ELEMENT	POWER ABSORBED
A	$(13.8)(-51\text{m}) = -703.8 \text{ mW}$
B	$(-15)(45\text{m}) = -675 \text{ mW}$
C	$(-1.8)(-6\text{m}) = 10.8 \text{ mW}$
D	$(12)(20\text{m}) = 240 \text{ mW}$
E	$(16.8)(14\text{m}) = 235.2 \text{ mW}$

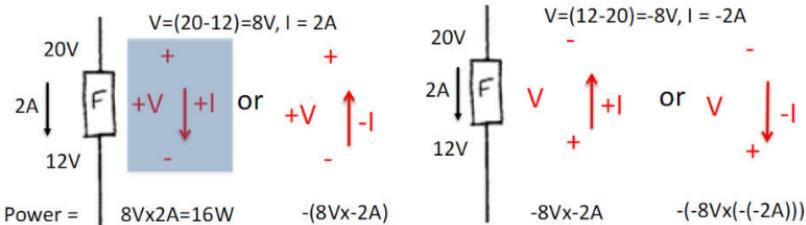b) $\sum P_{AB} = (10.8\text{m} + 240\text{m} + 235.2\text{m}) - (703.8\text{m} + 675\text{m}) + P_F$
 $= 486\text{m} - 1378.8\text{m} + P_F$
 $= -892.8 \text{ mW} + P_F$

SINCE $\sum P_{AB} = 0$, $P_F = 892.8 \text{ mW}$ It is an absorbing device,
Like a resistor.

Voltage and current possibilities on a Device F:




All are correct. It is better to choose +ve values of Voltage and Current and adjust the polarity of voltages and direction of current.

Chapter 2


Element Constraints

- (1) The interconnection of two or more electrical device is called an **electrical network**.
- (2) If an electrical network contains at least one closed path, then it is called a **circuit**.

closed path example:

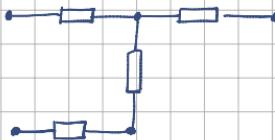

Not a circuit

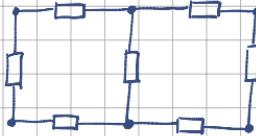

a circuit

(3) Device:

- An electrical device is a component that is treated as a separate entity
- Two-terminal devices are represented in general with a rectangle box




(4) circuit element

- To distinguish between the real device and its idealized model, the model will be called the **circuit elements**

Resistance Element



$$U = iR$$
$$i = \frac{U}{R}$$

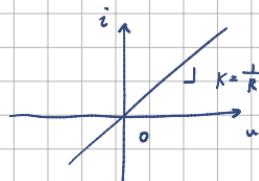

R is called resistance $\Omega = \frac{V}{A}$

(2) Sometimes it is convenient to use a called Conductance which is the reciprocal of resistance.

$$G = \frac{1}{R}$$

[G is conductance and has units of $\frac{A}{V}$ or siemens* $S = \Omega^{-1} = \frac{A}{V}$

(3) Power

$$P = V \cdot i = (iR) i = i^2 R$$
$$= V \cdot \frac{V}{R} = \frac{V^2}{R}$$

(always positive)


4) RESISTANCE DEVICES (OR RESISTOR)

- THE RESISTOR IS THE PHYSICAL DEVICE WHILE RESISTANCE IS THE IDEAL CONCEPT.*
- RESISTORS CAN BE APPROXIMATED OR MODELED UNDER MANY CONDITIONS AS AN IDEAL RESISTANCE
- MANY TYPES OF MATERIALS ARE USED TO MAKE RESISTORS. CARBON IS THE MOST COMMON.
- A TYPICAL CARBON COMPOSITION OR CARBON FILM RESISTOR IS CYLINDRICAL WITH MULTICOLORED BANDS (OR STAMPED NUMBERS) INDICATING THE NOMINAL VALUE



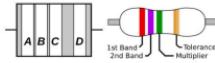a) COLOR CODE

$$R = (\underline{a} \ \underline{b} \times 10^{\underline{c}}) \pm \underline{d}$$



i) COLOR ⁺	VALUE	COLOR	VALUE
SILVER*	-2	YELLOW	4
GOLD*	-1	GREEN	5
BLACK	0	BLUE	6
BROWN	1	VIOLET	7
RED	2	GRAY	8
ORANGE	3	WHITE	9

+ FOR BANDS a, b, c

* ONLY OCCUR IN BAND c

ii) For Band d

$$\text{NO COLOR} = 20\%$$

$$\text{SILVER} = 10\%$$

$$\text{GOLD} = 5\%$$

iii) EXAMPLE : YELLOW - VIOLET - RED - GOLD

$$R = (\underline{4} \ \underline{7} \times 10^{\underline{2}}) \pm \underline{5\%} = 4.7K\Omega \pm 5\%$$

$$\therefore 4.7K(1-0.05) \leq R \leq 4.7K(1+0.05)$$

$$4.465K\Omega \leq R \leq 4.935K\Omega$$

b) STANDARD VALUES

Any other resistor will cost more!

i) ± 5 , ± 10 , $\pm 20\%$ RESISTORS

VALUE	TOL.	VALUE	TOL.	VALUE	TOL.
10	5, 10, 20	22	5, 10, 20	47	5, 10, 20
11	5	24	5	51	5
12	5, 10	27	5, 10	56	5, 10
13	5	30	5	62	5
15	5, 10, 20	33	5, 10, 20	68	5, 10, 20
16	5	36	5	75	5
18	5, 10	39	5, 10	82	5, 10
20	5	43	5	91	5

WHERE "VALUE" ARE THE POSSIBLE COMBINATIONS
OF BANDS a, b.


ii) $\pm 1\%$ RESISTORS

VALUE	VALUE	VALUE	VALUE	VALUE	VALUE
10.0	14.7	21.5	31.6	46.4	63.1
10.5	15.4	22.6	33.2	48.7	71.5
11.0	16.2	23.7	34.8	57.1	75.0
11.5	16.9	24.9	36.5	53.6	78.7
12.1	17.8	26.1	38.3	58.2	82.5
12.7	18.7	27.4	40.2	59.0	86.6
13.3	19.6	28.7	42.2	61.9	90.9
14.0	20.5	30.1	44.2	64.9	95.3

More expensive


c) SOME TYPES

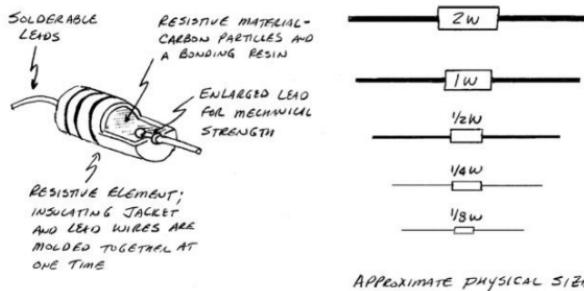i) CARBON COMPOSITION, $1\text{S}\Omega - 20\text{M}\Omega$, $\pm 5\%$, $\pm 10\%$, $\pm 20\%$ TOL




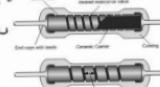ii) CARBON-FILM, $1\text{S}\Omega - 20\text{M}\Omega$, $\pm 1\%$, $\pm 2\%$, $\pm 5\%$ TOL

- MADE BY PLACING CERAMIC CORES IN A METHANE-FILLED FLASK AND HEATING IT UNTIL A CARBON FILM IS DEPOSITED ON THE CORES.
- AVAILABLE IN $\frac{1}{2}$, 1, AND 2 WATT SIZES LIKE ABOVE



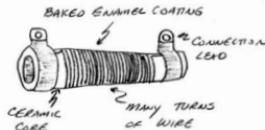
iii) WIRE-WOUND, $100\text{m}\Omega - 200\text{k}\Omega$, $\pm 0.1\% - \pm 2\%$ TOL



- AVAILABLE IN WATTS FROM 1W TO 250W

Large power absorbing resistors


(1) Open Circuit

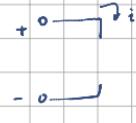


$$i = \frac{v}{R} \quad R \rightarrow \infty \Rightarrow 0$$

$v = \text{unspecified}$

$v-i$ Characteristic

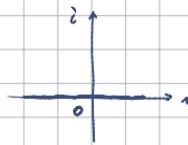


(2) Short circuit

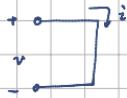


$$v = iR \quad R \rightarrow 0 \Rightarrow \infty$$

$i = \text{unspecified}$

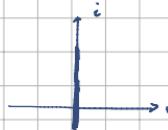


3) IDEAL SWITCH

Ideally, $R_{\text{OFF}} = \infty$

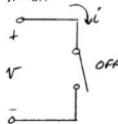

$\text{OFF} = \text{OPEN CIRCUIT}$

Ideally, $R_{\text{ON}} = 0$

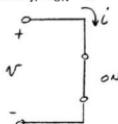

$\text{ON} = \text{SHORT CIRCUIT}$

b) $R_{\text{OFF}} \neq \infty$ BUT A LARGE VALUE


$$\begin{aligned} R_{\text{OFF}}(\text{WALL-SWITCH}) &= R_{\text{OFF}}(\text{RADIO-SWITCH}) \\ &= \text{RESISTANCE OF AIR} \\ &\approx 10^{15} \Omega \end{aligned}$$

4) NON-IDEAL OR REAL SWITCH


$$\begin{aligned} a) R_{\text{ON}} \neq 0 \text{ BUT A SMALL VALUE} \\ R_{\text{ON}}(\text{WALL-SWITCH}) &\approx 50 \text{ m}\Omega \\ R_{\text{ON}}(\text{RADIO-SWITCH}) &\approx 30 \text{ m}\Omega \end{aligned}$$

Ideal Sources


(1) Ideal Voltage Source

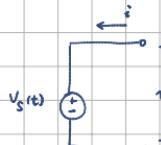



General Symbol

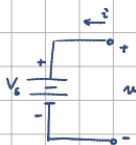


Special case: A battery

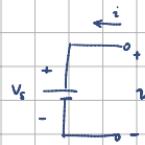


special case: A DC source

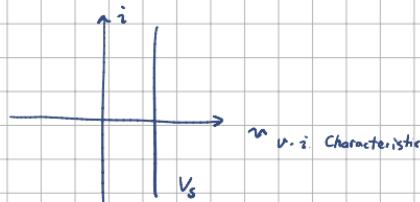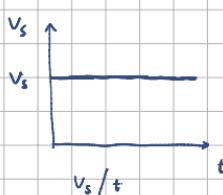




(2) Ideal Current Source

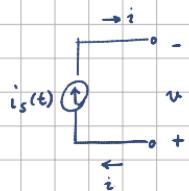

General Symbol

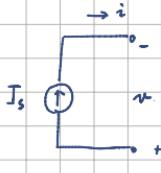

Special case. A DC Source

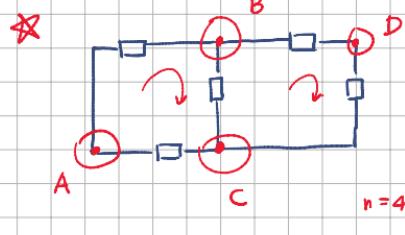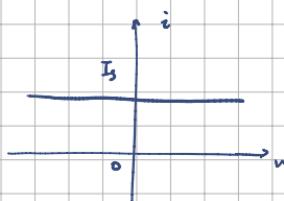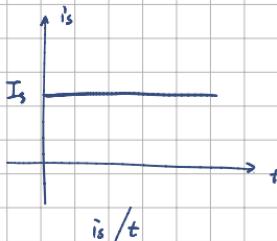


n : # of nodes


m : # of meshes (a closed loops that has no other loop)

b : # of branches (path that connects two nodes)

$$b = m + n - 1$$

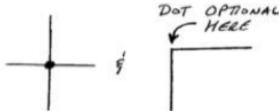


ELECTRICAL
CONNECTION

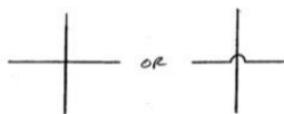

CROSSOVER WITH
NO CONNECTION



JACK
CONNECTION

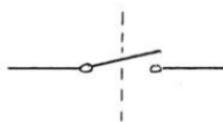

CONTROL LINE USED
TO OPEN OR CLOSE
A SWITCH

KCL (Inside node $\sum i =$ Outside node $\sum i$)

KVL (Rise of voltage = Drop of voltage)


* Resistance Rule : ① move through a resistor in the direction of the current,

this gives a change in the voltage of $-iR$

② move in the opposite direction of current. this gives a change in voltage iR

* Emf rule : ① move from $-$ to $+$, the change of voltage is $+V$

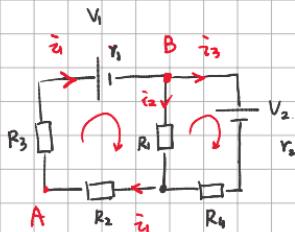② move from $+$ to $-$, the change of voltage is $-V$



$$\left. \begin{array}{l} i_1 = i_2 + i_3 \quad \text{① (KCL)} \\ -i_1 r_1 - V_1 - i_2 R_1 - i_1 R_2 - i_3 R_3 = 0 \quad \text{② (KVL)} \\ . -V_2 - i_3 r_2 - i_3 R_4 + i_2 R_1 = 0 \quad \text{③ (KVL)} \end{array} \right\}$$

* ΔV in two point : $\boxed{\Delta V = V_B - V_A = -i_1 R_3 - V_1 - i_1 r_1}$

Equivalent Circuit

(1) Series Resistance $R_{EQ} = \sum_{j=1}^k R_j$

(2) Parallel Resistance $R_{EQ} = \frac{1}{\sum_{j=1}^k \left(\frac{1}{R_j}\right)}$

k equal resistance $R_{EQ} = \frac{1}{\underbrace{\frac{1}{R_1} + \dots + \frac{1}{R_k}}_k} = \frac{R}{k}$

Proof : $R_{EQ} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_k}}$. Suppose $R_3 = \text{Smallest } R$.

$$R_{EQ} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_k}} < R_3$$



$$= \frac{R_3}{\frac{R_3}{R_1} + \frac{R_3}{R_2} + \dots + \frac{R_3}{R_k}} < R_3$$

$$= \frac{1}{\frac{R_3}{R_1} + \frac{R_3}{R_2} + \dots + \frac{R_3}{R_k}} < 1 \quad \checkmark \quad QED.$$

3.4 Equivalent Circuit

3) SOURCE TRANSFORMATIONS

[Back to Next Topic...](#)

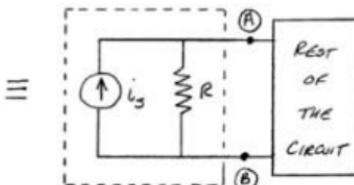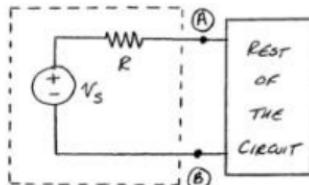


$$\text{WHERE } V_s = i_s R$$

and

$$i_s = \frac{V_s}{R} \Rightarrow V_s = i_s R$$




PROOF :

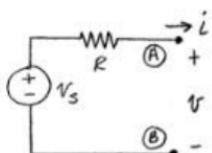

$$V_s = iR + v$$

$$i = \frac{V_s - v}{R}$$

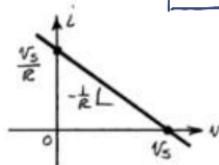
$$i = \left(-\frac{1}{R}\right)v + \frac{V_s}{R}$$



CIRCUIT

EQUNS


V-I CHARACTERISTICS

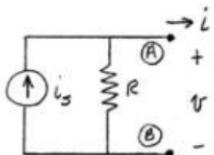

$$i_s = \frac{v}{R} + i$$

$$i = -\frac{v}{R} + i_s$$




$$i = \left(-\frac{1}{R}\right)v + i_s$$


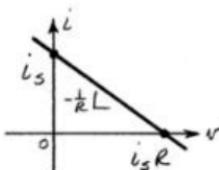


For these circuit to be equivalent, we need to have same v-i characteristics.




at terminal (A)-(B) we should let. $\frac{V_s}{R} = i_s$ And $V_s = i_s R$

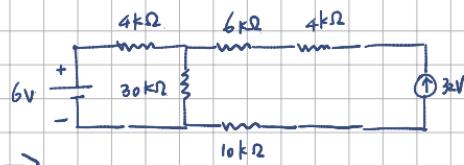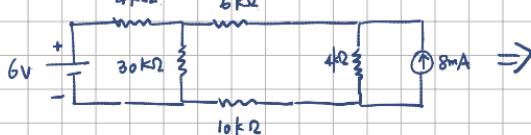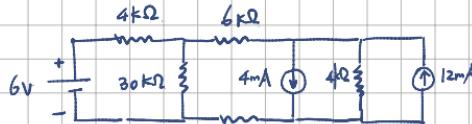Example . Find the power absorbed by 6V power source



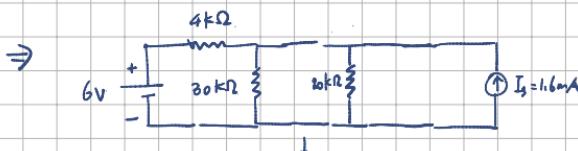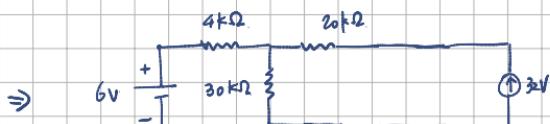
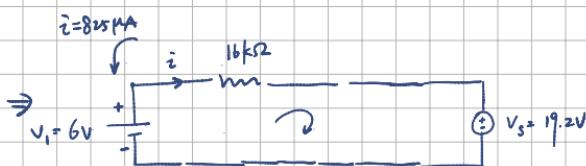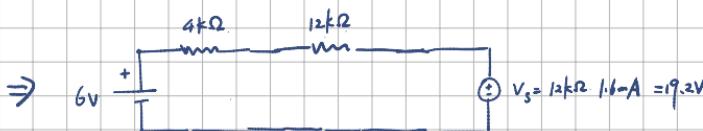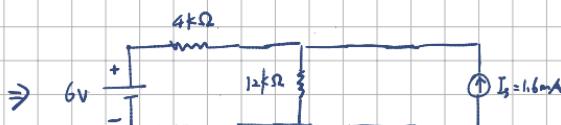
$$R_{eq} = \frac{30 \times 20}{30+20} \text{ k}\Omega = \frac{600}{50} \text{ k}\Omega = 12 \text{ k}\Omega$$




$$+v_i - iR - V_S = 0$$


$$6\text{V} - i \times 16 \text{ k}\Omega - 19.2\text{V} = 0 \Rightarrow i = \frac{6 - 19.2}{16} \text{ mA} = -0.825 \text{ mA} = -825 \mu\text{A}$$

$$P = v_i i = 6\text{V} \times (825 \mu\text{A}) = 4.95 \text{ mW} > 0 \quad (\text{Absorbed})$$

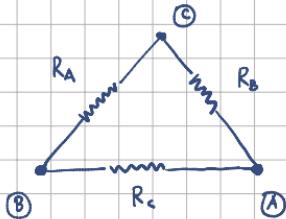$\text{Y} \rightleftharpoons \Delta$ Transformation



\equiv

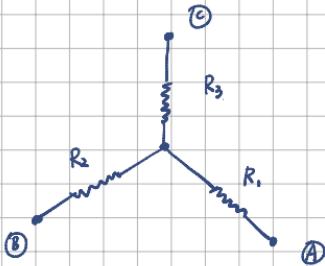

where

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$


$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

Note :

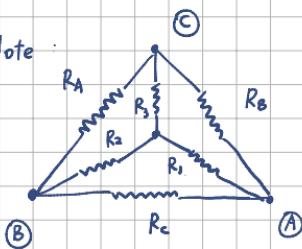


Δ -Resistance = Sum of product of γ -resistance in pairs
The opposite γ -resistance


γ -Resistance = Product of adjacent Δ -resistance
Sum of Δ -resistance

Chapter 3. Circuit Analysis Techniques


3.1 Node Voltage Analysis

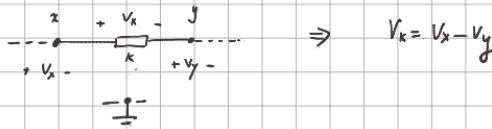

Special case:

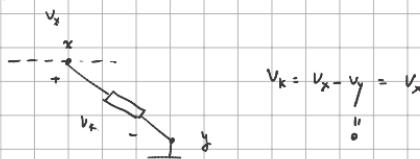

Writing node equation by inspection

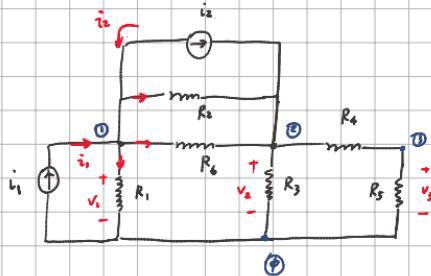

$$\text{Node 1: } i_1 - i_2 = \frac{1}{R_1} + (V_1 - V_2) \frac{1}{R_2} + (V_1 - V_2) \frac{1}{R_6}$$

$$= G_1 V_1 + (V_1 - V_2) G_2 + (V_1 - V_2) G_6$$

$$= (G_1 + G_2 + G_6) V_1 - (G_2 + G_6) V_2 + 0 V_3$$

$$\text{Node 2: } i_2 = (V_2 - V_1) (G_2 + G_6) + (V_2 - V_3) G_4 + V_2 G_5$$

$$= -(G_2 + G_6) V_1 + (G_2 + G_3 + G_4 + G_5) V_2 - G_4 V_3$$

$$\text{Node 3: } 0 = (V_3 - V_2) G_4 + V_3 G_5$$

$$= 0 \cdot V_1 - G_4 V_2 + (G_4 + G_5) V_3$$

Summarize

$$i_1 - i_2 = (G_1 + G_2 + G_6)u_1 - (G_2 + G_6)u_2 + 0 \cdot u_3$$

$$i_2 = -(G_2 + G_6)u_1 + (G_2 + G_3 + G_4 + G_6)u_2 - G_4u_3$$

$$0 = 0 \cdot u_1 - G_4 \cdot u_2 + (G_4 + G_5)u_3$$

\Rightarrow Matrix form

$$\begin{pmatrix} i_1 - i_2 \\ i_2 \\ 0 \end{pmatrix} = \begin{pmatrix} G_1 + G_2 + G_6 & -(G_2 + G_6) & 0 \\ -(G_2 + G_6) & (G_2 + G_3 + G_4 + G_6) & -G_4 \\ 0 & -G_4 & G_4 + G_5 \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix}$$

\Rightarrow In the general form

$$\begin{pmatrix} j_1 \\ j_2 \\ j_3 \end{pmatrix} = \begin{pmatrix} g_{11} & g_{12} & g_{13} \\ g_{21} & g_{22} & g_{23} \\ g_{31} & g_{32} & g_{33} \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \\ v_3 \end{pmatrix}$$

二. 结点方程

电子科技大学 bilibili

$$\left\{ \begin{array}{l} G_1(u_1 - u_2) + G_5(u_1 - u_3) = i_s \\ -G_1(u_1 - u_2) + G_2u_2 + G_3(u_2 - u_3) = 0 \\ -G_5(u_1 - u_3) + G_4u_3 - G_3(u_2 - u_3) = 0 \end{array} \right.$$


~~ 自电导
 互电导

$$\left\{ \begin{array}{l} (G_1 + G_5)u_1 - G_1u_2 - G_5u_3 = i_s \quad \text{流入结点 1 取正值} \\ -G_1u_1 + (G_1 + G_2 + G_3)u_2 - G_3u_3 = 0 \\ -G_5u_1 - G_3u_2 + (G_3 + G_4 + G_5)u_3 = 0 \end{array} \right.$$

电路分析基础

三. 举例说明


电子科技大学 bilibili

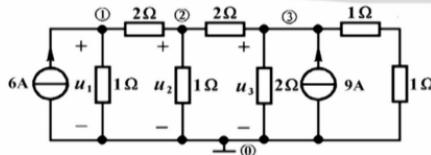

解：

$$\left\{ \begin{array}{l} (1 + 0.5)u_1 - 0.5u_2 = 6 \\ -0.5u_1 + (0.5 + 1 + 0.5)u_2 - 0.5u_3 = 0 \\ -0.5u_2 + (0.5 + 0.5 + 0.5)u_3 = 9 \end{array} \right.$$

电路分析基础

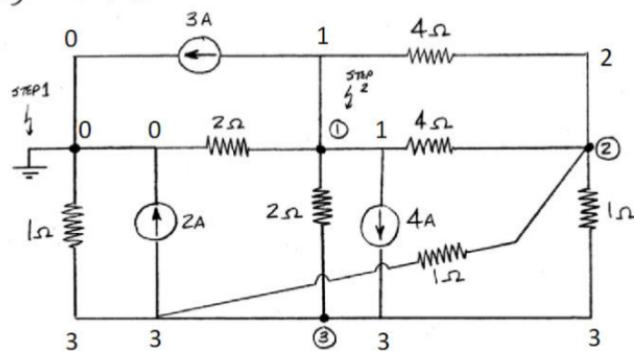

$$\begin{array}{l}
 \textcircled{1} \quad \begin{bmatrix} -3 & -4 \\ 0 & 0 \\ -2 & 4 \end{bmatrix} = \begin{bmatrix} \frac{1}{2} + \frac{1}{4} + \frac{1}{4} + \frac{1}{2} & -\left(\frac{1}{4} + \frac{1}{4}\right) & -\left(\frac{1}{2}\right) \\ -\left(\frac{1}{4} + \frac{1}{4}\right) & \left(\frac{1}{4} + \frac{1}{4} + 1 + 1\right) & -(1+1) \\ -\left(\frac{1}{2}\right) & -(1+1) & \left(\frac{1}{2} + 1 + 1 + 1\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} \\
 \textcircled{2} \quad \begin{bmatrix} -7 \\ 0 \\ 2 \end{bmatrix} = \begin{bmatrix} 1.5 & -0.5 & -0.5 \\ -0.5 & 2.5 & -2 \\ -0.5 & -2 & 3.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}
 \end{array}$$

1) Cramer's Rule

GIVEN A SET OF n -LINEAR EQUATIONS IN
 n -UNKNOWNs

$$\begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nn} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix}$$

$$[B] = [A][x]$$

IF THE DETERMINANT (Δ) OF A IS NOT ZERO,
 THEN THE SYSTEM HAS A UNIQUE SOLUTION

$$x_j = \frac{\Delta A_j}{\Delta A} \quad j=1, 2, \dots, n$$

④ Tips from linear algebra

1.5 Cramer's rule

($\frac{1}{2}$ if - ① # of function = # unknown ② $D \neq 0$)

$$\text{Eq: } \begin{cases} x_1 + x_2 + x_3 = 1 \\ x_1 - x_2 + 5x_3 = 6 \\ -x_1 + x_2 + 6x_3 = 9 \end{cases} \quad \left| \begin{array}{ccc|c} 1 & 1 & 1 & 1 \\ 1 & -1 & 5 & 6 \\ -1 & 1 & 6 & 9 \end{array} \right| \quad \text{系数行列式} \quad x_j = \frac{D_j}{D}$$

$$D = \left| \begin{array}{ccc|c} 1 & 1 & 1 & 1 \\ 1 & -1 & 5 & 6 \\ -1 & 1 & 6 & 9 \end{array} \right| \quad D_1 = \left| \begin{array}{cc|c} 6 & 1 & 5 \\ 9 & 1 & 6 \end{array} \right| \quad = \left| \begin{array}{ccc|c} 1 & 1 & 1 & 1 \\ 1 & 6 & 5 & 6 \\ -1 & 9 & 6 & 9 \end{array} \right| \quad D_3 = \left| \begin{array}{ccc|c} 1 & 1 & 1 & 1 \\ 1 & -1 & 5 & 9 \\ -1 & 1 & 1 & 9 \end{array} \right|$$

$$x_1 = \frac{D_1}{D} \quad x_2 = \frac{D_2}{D} \quad x_3 = \frac{D_3}{D}$$


④ Tips: minor m_{ij} Cofactor C_{ij} $C_{ij} = (-1)^{i+j} m_{ij}$

value of $\Delta A = a_{11}C_{11} + a_{12}C_{12} + \dots + a_{1n}C_{1n}$ (按行展开)


$$\text{Example: } \Delta A = \left| \begin{array}{ccc} 1 & 1 & 2 \\ -1 & 3 & 1 \\ 3 & -1 & -3 \end{array} \right|$$

$$= 1 \times (-1)^{1+1} \left| \begin{array}{cc} 3 & 1 \\ -1 & -3 \end{array} \right| + 1 \times (-1)^{1+2} \left| \begin{array}{cc} 1 & 2 \\ 3 & -3 \end{array} \right| + 2 \times (-1)^{1+3} \left| \begin{array}{cc} 1 & 1 \\ 3 & -1 \end{array} \right|$$

3.2 Mesh Current Analysis

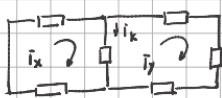

$$i_x + i_y = i_k$$

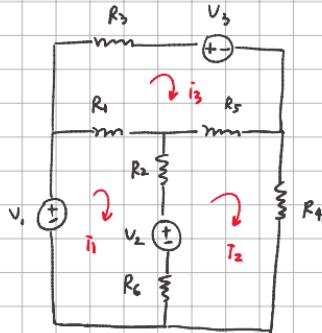

mesh 1:

$$V_1 - (i_1 - i_3) R_1 - (i_1 - i_2) (R_2 + R_6) + V_2 = 0$$

$$\therefore V_1 - V_2 = (R_1 + R_2 + R_6) i_1 - (R_2 + R_6) i_2 - R_1 i_3$$

mesh 2:

$$V_2 = -(R_2 + R_6) i_1 + (R_2 + R_4 + R_6) i_2 - R_5 i_3$$

mesh 3:

$$-V_3 = -R_1 i_1 - R_5 i_2 + (R_1 + R_3 + R_5) i_3$$

In matrix form

$$\begin{pmatrix} V_1 - V_2 \\ V_2 \\ -V_3 \end{pmatrix} = \begin{pmatrix} R_1 + R_2 + R_6 & -(R_2 + R_6) & -R_1 \\ -(R_2 + R_6) & R_2 + R_4 + R_5 + R_6 & -R_5 \\ -R_1 & -R_5 & R_1 + R_3 + R_5 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix}$$

In general

$$\begin{pmatrix} u_1 \\ u_2 \\ u_3 \end{pmatrix} = \begin{pmatrix} r_{11} & r_{12} & r_{13} \\ r_{21} & r_{22} & r_{23} \\ r_{31} & r_{32} & r_{33} \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix}$$

3.3 Superposition Principle



The response (voltage or current) from a number of independent sources acting simultaneously is simply the sum of the responses which would be produced by each of the independent sources acting alone with all the other independent sources set equal to zero.

Zero Source


(a) Setting Voltage source to be zero like a short circuit $V=0 \quad i=\infty$

(b) Setting Voltage source to be zero like a open circuit $i=0 \quad V=\infty$

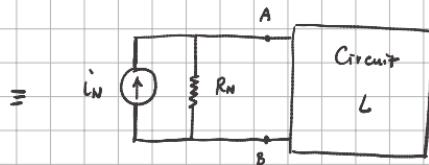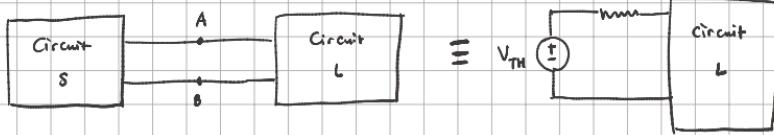3.4 Thevenin and Norton Equivalent Circuit



3.5 Maximum Signal Transfer

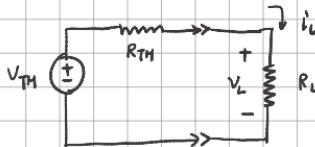

tips: Second derivative test

$$f''(x_0) \text{ continuous } f'(x_0) = 0$$

$$(a) f''(x_0) < 0 \quad f(x_0) \text{ has relative max}$$

$$(b) f''(x_0) > 0 \quad f(x_0) \text{ has relative min}$$

$$(c) f''(x_0) = 0 \quad \text{No conclusion}$$

$$P_{R_L} = i_L^2 \cdot R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 \cdot R_L$$

$$\frac{dP_{R_L}}{dR_L} = 0 \Rightarrow \left\{ \frac{d}{dR_L} \left[R_{TH} + R_L \right]^{-2} \right\} (V_{TH}^2 R_L) + (R_{TH} + R_L)^{-2} \frac{d}{dR_L} [V_{TH}^2 R_L] = 0$$

$$\Rightarrow R_{TH} = R_L \quad f''(x_0) = \left. \frac{d^2 P_{R_L}}{dR_L^2} \right|_{R_L=R_{TH}} < 0 \rightarrow \text{Relative max}$$

$$(1) \quad P_{R_L(\max)} = \left. \frac{V_{TH}^2}{(R_{TH} + R_L)^2} \cdot R_L \right|_{R_L=R_{TH}} = \frac{V_{TH}^2}{4R_{TH}}$$


$$(2) \quad \text{Since } i_N = \frac{V_{TH}}{R_{TH}} \quad P_{R_L(\max)} = \frac{i_N^2 R_{TH}^2}{4R_{TH}} = \frac{i_N^2 R_{TH}}{4}$$

$$(3) \quad \text{Also } P_{R_L(\max)} = \frac{V_{TH}^2}{4R_{TH}} = \frac{V_{TH} \cdot V_{TH}}{4R_{TH}} = \frac{V_{TH} \cdot (i_N R_{TH})}{4R_{TH}} = \frac{V_{TH}}{4} \cdot \frac{i_N}{R_{TH}}$$

$$(4) \quad \frac{i_L}{i_N} = \frac{\frac{V_{TH}}{R_{TH} + R_L}}{\frac{i_N}{R_{TH}}} = \frac{R_{TH}}{R_L + R_{TH}} = \frac{1}{\left(\frac{R_L}{R_{TH}} \right) + 1}$$

$$\frac{V_L}{V_{TH}} = \frac{\left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 \cdot R_L}{\frac{V_{TH}^2}{4R_{TH}}} = \frac{\left(\frac{R_L}{R_{TH}} \right)}{\left(\frac{R_L}{R_{TH}} \right) + 1}$$


$$(5) \quad \frac{P_{RL}}{P_{RL(max)}} = \frac{\left(\frac{V_{TH}}{R_L + R_{TH}} \right)^2 R_L}{\frac{V_{TH}^2}{4R_{TH}}} = \frac{\frac{4}{4} \left(\frac{R_L}{R_{TH}} \right)}{\left[\left(\frac{R_L}{R_{TH}} \right) + 1 \right]^2}$$

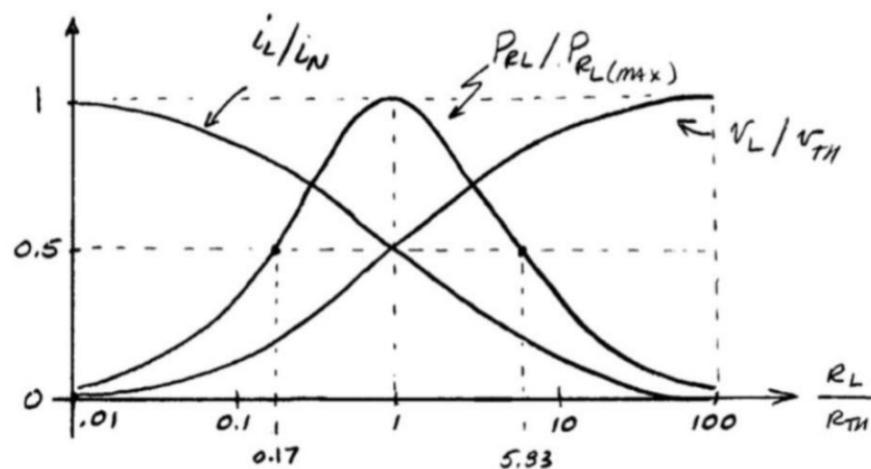

Chapter 4.

A) Dependent Voltage Sources

VCVS (Voltage Control Voltage Source)

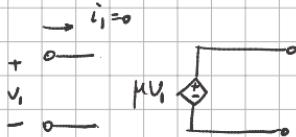

μ : 电压放大倍数.


CCVS (Current Control Voltage Source)



r: 转移电阻


B) Dependent Current Sources

VCCS (Voltage Control Current Source)

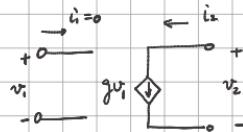


g: 转移电导


CCCS (Current Control Current Source)

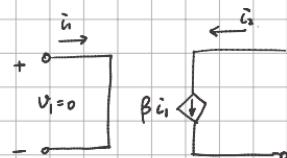


β: 电流放大倍数.

Operational Amplifier (OP-AMP)

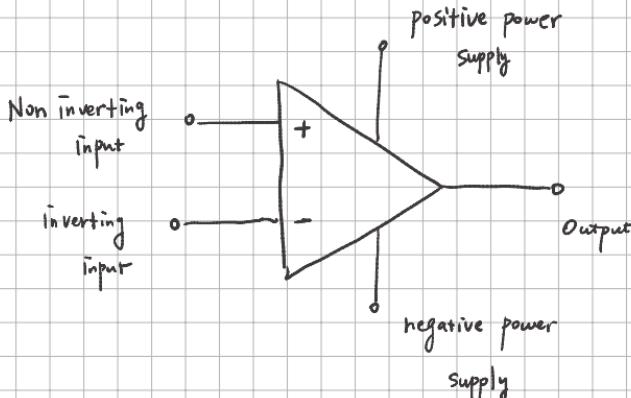


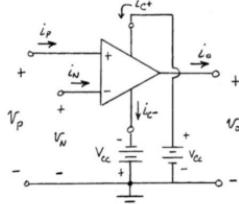

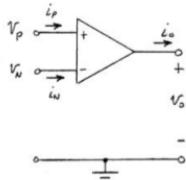CONNECTIONS NEEDED WITH
REFERENCE DIRECTIONS




SHORT-HAND NOTATION

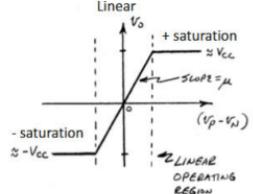

TRANSFER CHARACTERISTIC

Desired property of an OP-AMP, its operational range is when V_o is within $[-V_{CO}, V_{OO}]$.

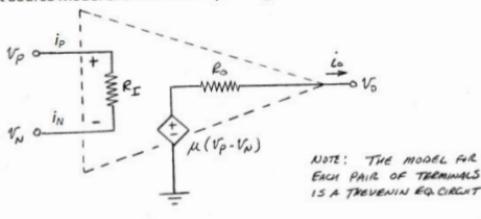Dependent Source Model of an OP-AMP Operating at Linear Mode



LINEAR REGION MODEL

B) COMMERCIAL OP-AMPS

$$1\text{M}\Omega < R_I < 1\text{T}\Omega$$

$$10\Omega < R_O < 100\Omega$$

$$100\text{k} < \mu < 100\text{M}$$

C) IDEAL OP-AMPS

- IF WE COULD MAKE THE PERFECT OP-AMP


$$R_I \rightarrow \infty \Omega$$

$$R_O \rightarrow 0 \Omega$$


$$\mu \rightarrow \infty$$

- WE KNOW HOW TO MODEL INFINITE AND ZERO
RESISTANCE, BUT WHAT ABOUT INFINITE GAIN?

-- Some feedback loop is needed

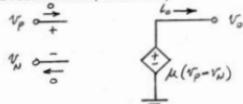


Open circuit
Also open circuit

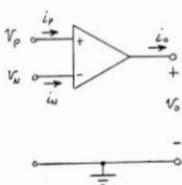


$$V_p = V_N$$

$$i_p = i_N = 0$$

运算放大器原理

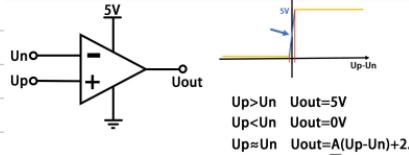

反相比例运算电路

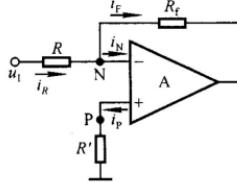

根据虚短虚断:

$$U_n = U_p = 0 \quad ip = i_N = 0$$

计算节点N的电流:

$$i_R = i_f = \frac{U_i}{R}$$


计算输出电压:

$$U_o = -i_f \cdot R_f = -\frac{U_i}{R} \times R_f$$

$$U_o = -\frac{R_f}{R} U_i$$

计算输入平衡电阻:

$$R' = R \parallel R_f$$

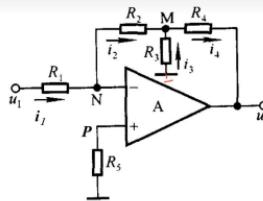

根据虚短虚断有: $i_1 = i_2 \quad U_N = U_P$

$$\text{第一步: } i_1 = i_2 = \frac{U_i}{R_1} \quad i_4 = i_2 + i_3$$

$$\text{第二步: } U_m = -i_2 R_2 = -i_3 R_3 \quad i_3 = i_2 \frac{R_2}{R_3} = \frac{U_i R_2}{R_1 R_3}$$


$$\text{第三步: } U_o = -i_2 R_2 - i_4 R_4 = -i_2 R_2 - (i_2 + i_3) R_4$$

$$= -i_2 R_2 - i_2 R_4 - i_3 R_4 = -i_2 (R_2 + R_4) - i_3 R_4$$

$$= -U_i \frac{R_2 + R_4}{R_1} - \frac{U_i R_2}{R_1 R_3} R_4 = -U_i \left(\frac{R_2 + R_4}{R_1} + \frac{R_2 R_4}{R_1 R_3} \right)$$

$$\text{第四步: } R_S = R_1 / [R_2 + (R_3 // R_4)]$$

T型网络反比例

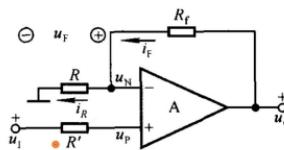

根据虚短虚断:

$$U_N = U_p = U_i \quad ip = i_N = 0$$

$$\therefore i_R = i_F = \frac{U_i}{R}$$


$$\therefore U_o = U_N + I_F R_f = U_i + \frac{U_i}{R} R_f$$

$$\therefore U_o = U_i \left(1 + \frac{R_f}{R} \right)$$

计算输入平衡电阻:

$$R' = R \parallel R_f$$

同相比例运算电路

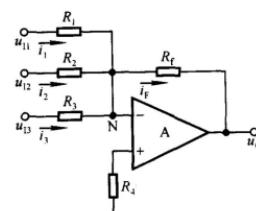

$$i_1 + i_2 + i_3 = i_f$$

$$U_o = -R_f i_f = -R_f (i_1 + i_2 + i_3)$$

$$U_o = -R_f \left(\frac{U_{11}}{R_1} + \frac{U_{12}}{R_2} + \frac{U_{13}}{R_3} \right)$$

$$= -\frac{R_f}{R_1} U_{11} - \frac{R_f}{R_2} U_{12} - \frac{R_f}{R_3} U_{13}$$


$$\text{当 } R_1 = R_2 = R_3 \text{ 时}$$

$$U_o = -\frac{R_f}{R_1} (U_{11} + U_{12} + U_{13})$$

$$R_4 = R_1 // R_2 // R_3 // R_f$$

反相求和运算电路

同相串和运算电路

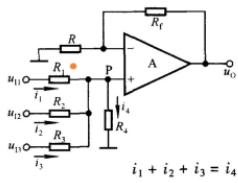

$$\begin{aligned} & \frac{u_{11} - u_p}{R_1} + \frac{u_{12} - u_p}{R_2} + \frac{u_{13} - u_p}{R_3} + \frac{u_{14} - u_p}{R_4} = \frac{u_p}{R_f} \\ & \therefore \frac{U_{11}}{R_1} - \frac{U_p}{R_1} + \frac{U_{12}}{R_2} - \frac{U_p}{R_2} + \frac{U_{13}}{R_3} - \frac{U_p}{R_3} + \frac{U_{14}}{R_4} - \frac{U_p}{R_4} = \frac{U_p}{R_f} \end{aligned}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) u_p = \frac{u_{11}}{R_1} + \frac{u_{12}}{R_2} + \frac{u_{13}}{R_3}$$

$$\therefore R_1 \parallel R_2 \parallel R_3 \parallel R_4 = R_p$$

$$\therefore \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{R_p}$$

$$u_p = R_p \left(\frac{u_{11}}{R_1} + \frac{u_{12}}{R_2} + \frac{u_{13}}{R_3} \right)$$

$$\therefore U_N = U_p$$

$$\therefore U_o = U_N \left(1 + \frac{R_f}{R} \right)$$

$$= \left(\frac{R_p}{R_1} U_{11} + \frac{R_p}{R_2} U_{12} + \frac{R_p}{R_3} U_{13} \right) \left(1 + \frac{R_f}{R} \right)$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) u_p = \frac{u_{11}}{R_1} + \frac{u_{12}}{R_2} + \frac{u_{13}}{R_3}$$

$$\therefore R_1 \parallel R_2 \parallel R_3 \parallel R_4 = R_p$$

$$\therefore \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{R_p}$$

$$u_p = R_p \left(\frac{u_{11}}{R_1} + \frac{u_{12}}{R_2} + \frac{u_{13}}{R_3} \right)$$

$$\therefore U_N = U_p$$

$$\therefore U_o = U_N \left(1 + \frac{R_f}{R} \right)$$

$$= \left(\frac{R_p}{R_1} U_{11} + \frac{R_p}{R_2} U_{12} + \frac{R_p}{R_3} U_{13} \right) \left(1 + \frac{R_f}{R} \right)$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) u_p = \frac{u_{11}}{R_1} + \frac{u_{12}}{R_2} + \frac{u_{13}}{R_3}$$

$$\therefore R_1 \parallel R_2 \parallel R_3 \parallel R_4 = R_p$$

$$\therefore \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{R_p}$$


$$u_p = R_p \left(\frac{u_{11}}{R_1} + \frac{u_{12}}{R_2} + \frac{u_{13}}{R_3} \right)$$

$$\therefore U_N = U_p$$

$$\therefore U_o = U_N \left(1 + \frac{R_f}{R} \right)$$


$$= \left(\frac{R_p}{R_1} U_{11} + \frac{R_p}{R_2} U_{12} + \frac{R_p}{R_3} U_{13} \right) \left(1 + \frac{R_f}{R} \right)$$

加减运算电路

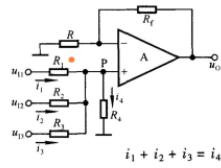

$$\begin{aligned} & \frac{u_{11} - u_p}{R_1} + \frac{u_{12} - u_p}{R_2} + \frac{u_{13} - u_p}{R_3} + \frac{u_{14} - u_p}{R_4} = \frac{u_p}{R_f} \\ & \therefore \frac{U_{11}}{R_1} - \frac{U_p}{R_1} + \frac{U_{12}}{R_2} - \frac{U_p}{R_2} + \frac{U_{13}}{R_3} - \frac{U_p}{R_3} + \frac{U_{14}}{R_4} - \frac{U_p}{R_4} = \frac{U_p}{R_f} \end{aligned}$$

差分比例运算电路

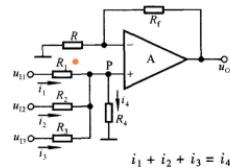


$$\begin{aligned} & \frac{u_{11} - u_p}{R_1} + \frac{u_{12} - u_p}{R_2} + \frac{u_{13} - u_p}{R_3} + \frac{u_{14} - u_p}{R_4} = \frac{u_p}{R_f} \\ & \therefore \frac{U_{11}}{R_1} - \frac{U_p}{R_1} + \frac{U_{12}}{R_2} - \frac{U_p}{R_2} + \frac{U_{13}}{R_3} - \frac{U_p}{R_3} + \frac{U_{14}}{R_4} - \frac{U_p}{R_4} = \frac{U_p}{R_f} \end{aligned}$$

积分运算


Chapter 6.

6.1 The capacity

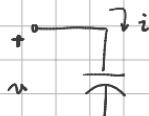

$$i(t) = C \cdot \frac{dv(t)}{dt}$$
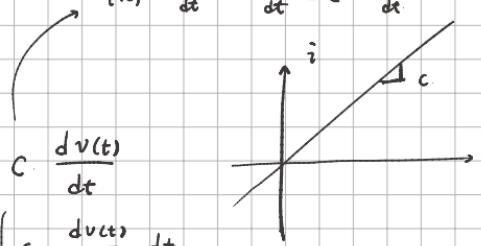
$$\int i(t) dt = \int C \frac{dv(t)}{dt} dt$$



$$\int_{t_0}^{t_1} i(t) dt = C \int_{t_0}^{t_1} dv(t) = C [v(t_1) - v(t_0)]$$

$$\Rightarrow V(t_1) = \frac{1}{C} \int_{t_0}^{t_1} i(t) dt + v(t_0)$$

$$P(t) = \frac{dW(t)}{dt} \Rightarrow \int P(t) dt = \int \frac{dW(t)}{dt} dt$$

$$\Rightarrow \int_{t_0}^{t_1} P(t) dt = \int_{t_0}^{t_1} dW(t) = w(t_1) - w(t_0)$$

$$\text{i.e. } w(t_1) = \int_{t_0}^{t_1} P(t) dt + w(t_0) = \int_{t_0}^{t_1} i(t) \cdot v(t) dt + w(t_0)$$


$$w(t) = \int_{t_1}^{t_0} i(t) v(t) dt + w(t_0) = \int_{t_0}^t \left[C \frac{dv(t)}{dt} \right] v(t) dt + w(t_0)$$

$$= C \int_{t_0}^t v(t) \frac{d(v(t))}{dt} dt + w(t_0) = \frac{1}{2} C \left[v(t) \right]^2 \Big|_{t_0}^t + w(t_0)$$

$$= \frac{1}{2} C v^2(t) - \frac{1}{2} C v^2(t_0) + w(t_0) = \boxed{\frac{1}{2} C v^2(t)} = \frac{1}{2} \frac{q^2(t)}{C}$$

$$P(t) = \frac{dW(t)}{dt} = \boxed{\frac{1}{2} C \frac{dV^2(t)}{dt}}$$

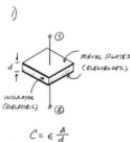E) Physical Device - Capacitor (See Appendix A)



A CAPACITOR CONSISTS OF TWO METAL PLATES SEPARATED BY AN INSULATOR.

CAPACITANCE INCREASES WHEN THE AREA OF THE PLATES, A , INCREASES AND IF THE DISTANCE, d , BETWEEN THE PLATES DECREASES.

2) SOME TYPES OF CAPACITORS




3) Capacitor - 5 numbers and 1 letter standard

$$\frac{A}{d} \leq \frac{1}{\epsilon_0} \Rightarrow C = (\frac{A}{d} \times 10^{-9}) \text{ pF} \pm 1\%$$

WHERE

$$d : R = \pm 20\% \quad K = \pm 10\% \quad J = \pm 5\% \\ G = \pm 2\% \quad F = \pm 1\%$$


6.2. The Inductor

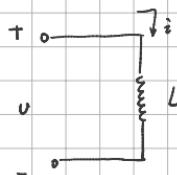

$$(\Phi(t) = L i(t))$$

$$\lambda(t) = L i(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

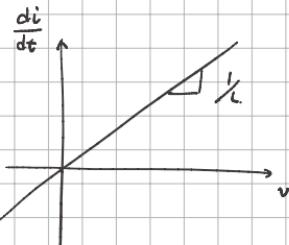

$$\text{Faraday law: } v(t) = \frac{d\Phi_B(t)}{dt} = \frac{d(L i(t))}{dt} = L \cdot \frac{di(t)}{dt}$$

$\lambda(t)$ represents magnetic flux linkage

$$\text{unit of } L \text{ is H} \quad |H| = \frac{wb}{A} \quad \lambda(t) \text{ unit is wb}$$

$$v(t) = L \cdot \frac{di(t)}{dt} \Rightarrow \int v(t) dt = \int L di(t)$$

$$\Rightarrow \int_{t_0}^{t_1} v(t) dt = \int_{t_0}^{t_1} L di(t) = L [i(t_1) - i(t_0)]$$


$$\Rightarrow i(t_1) = \frac{1}{L} \cdot \int_{t_0}^{t_1} v(t) dt + i(t_0)$$

$$P(t) = \frac{d w(t)}{dt} \Rightarrow \int P(t) dt = \int d w(t)$$


$$\int_{t_0}^{t_1} P(t) dt = \int_{t_0}^{t_1} d w(t) = w(t_1) - w(t_0)$$

$$\begin{aligned} \Rightarrow w(t_1) &= \int_{t_0}^{t_1} P(t) dt + w(t_0) = \int_{t_0}^{t_1} v(t) i(t) dt + w(t_0) \\ &= L \cdot \int_{t_0}^{t_1} \left[-\frac{d i(t)}{dt} \right] \cdot i(t) dt + w(t_0) \\ &= L \cdot \int_{t_0}^{t_1} -\dot{i}(t) d i(t) + w(t_0) \\ &= L \cdot \left[\frac{1}{2} \dot{i}^2(t) \right] \Big|_{t_0}^{t_1} + w(t_0) \\ &= L \left[\frac{1}{2} \dot{i}^2(t_1) - \frac{1}{2} \dot{i}^2(t_0) \right] + w(t_0) \\ &= \boxed{\frac{1}{2} L \dot{i}^2(t)} \end{aligned}$$

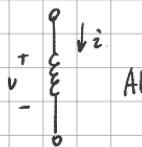
$$P(t) = \frac{d w(t)}{dt} = \boxed{\frac{1}{2} L \frac{d \dot{i}^2(t)}{dt}}$$




Absorbing power

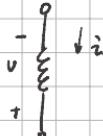

generating power

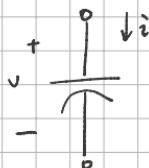


Absorbing power

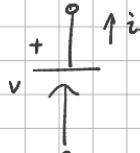


generating power

56.1) INTEGRATOR

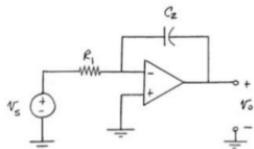FIND $V_o(t)$

SOLUTION :

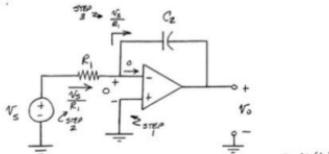


$$\begin{aligned} V_o(t_1) &= -V_{o_0} + 0 = -\left[\frac{1}{R_1 C_2} \int_{t_0}^{t_1} \frac{V_o}{R_1} dt + V_{o_0}(t_0)\right] + 0 \\ &= -\frac{1}{R_1 C_2} \int_{t_0}^{t_1} V_o(t) dt + V_o(t_0) \end{aligned}$$


OR DOING A CHANGE OF VARIABLE

$$V_o(t) = -\frac{1}{R_1 C_2} \int_{t_0}^t V_o(\tau) d\tau + V_o(t_0)$$

56.2) DIFFERENTIATOR

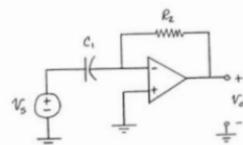FIND $V_o(t)$

SOLUTION :

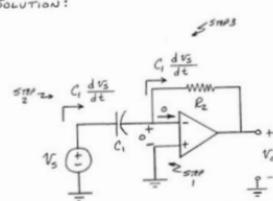

$$V_o = -C_1 \frac{d V_s}{dt} R_2 + 0$$

$$\therefore V_o = -R_2 C_1 \frac{d V_s(t)}{dt}$$


OP-AMP for Differentiator and Integrator

	$v_1(t) \xrightarrow{K} \int v_o(t) \xrightarrow{RC}$	$K = -\frac{1}{RC}$
	$v_1(t) \xrightarrow{K} \frac{d}{dt} v_o(t) \xrightarrow{-RC}$	$K = -RC$

Chapter 1: First and Second - Order Circuits

RC Circuits
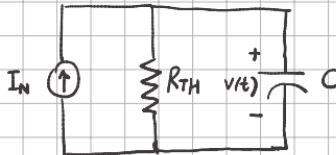
$$I_N = \frac{V(t)}{R_{TH}} + C \frac{dV(t)}{dt} = C \left[\frac{V(t)}{R_{TH}C} + \frac{dV(t)}{dt} \right]$$



$$\Rightarrow \frac{dV(t)}{dt} = -\frac{V(t)}{R_{TH}C} + \frac{I_N}{C} = -\frac{1}{R_{TH}C} [V(t) - I_N R_{TH}]$$

$$\Rightarrow \frac{1}{V(t) - I_N R_{TH}} dV(t) = -\frac{1}{R_{TH}C} dt$$

$$\Rightarrow \int_{t_0}^{t_1} \left(\frac{1}{V(t) - I_N R_{TH}} \right) dV(t) = \int_{t_0}^{t_1} \left(\frac{-1}{R_{TH}C} \right) dt$$

$$\Rightarrow \ln(V(t) - I_N R_{TH}) \Big|_{t_0}^{t_1} = -\frac{1}{R_{TH}C} (t_1 - t_0)$$

$$\Rightarrow \ln \left[\frac{V(t_1) - I_N R_{TH}}{V(t_0) - I_N R_{TH}} \right] = -\frac{1}{R_{TH}C} (t_1 - t_0)$$

$$\Rightarrow \frac{V(t_1) - I_N R_{TH}}{V(t_0) - I_N R_{TH}} = e^{-\frac{1}{R_{TH}C} (t_1 - t_0)}$$

$$\Rightarrow V(t_1) = I_N R_{TH} + \left[V(t_0) - I_N R_{TH} \right] e^{-\frac{(t_1 - t_0)}{R_{TH}C}}$$

$$\text{Assume } A_1 = I_N R_{TH} \quad B_1 = v(t_0) - I_N R_{TH} \quad \uparrow = R_{TH} C. \quad A_1 + B_1 = I_N R_{TH}$$

$$(a) \quad t = t_0 \quad v(t) = A_1 + B_1 e^{-(t-t_0)/\uparrow} = v(t_0)$$

$$(b) \quad t = \infty \quad v(t) = A_1 + B_1 e^{-\infty} = A_1 = I_N R_{TH}$$


$$\text{More general} \quad i_x(t) \quad v_x(t) = A_2 + B_2 e^{-\infty/\uparrow}$$

$$A_2 + B_2 = i_x(t_0) \quad v_x(t_0)$$

$$A_2 = i_x(t \rightarrow \infty) \quad v_x(t \rightarrow \infty)$$

$$\uparrow = R_{TH} C.$$

RL Circuit

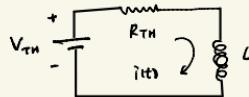

$$V_{TH} = R_{TH} \cdot i(t) + L \cdot \frac{di(t)}{dt}$$

For $V_L = L \cdot \frac{di(t)}{dt}$ (Formula)

$$\Rightarrow V_{TH} = L \left[\frac{R_{TH}}{L} i(t) + \frac{di(t)}{dt} \right] \Rightarrow \frac{di(t)}{dt} = - \frac{R_{TH}}{L} i(t) + \frac{V_{TH}}{L}$$

$$\Rightarrow \frac{di(t)}{dt} = - \frac{R_{TH}}{L} \left[i(t) - \frac{V_{TH}}{R_{TH}} \right]$$

$$\Rightarrow \int_{t_0}^{t_1} \frac{1}{i(t) - \frac{V_{TH}}{R_{TH}}} \frac{di(t)}{dt} = \int_{t_0}^{t_1} - \frac{R_{TH}}{L}$$

$$\Rightarrow \ln \left[i(t_1) - \frac{V_{TH}}{R_{TH}} \right] - \ln \left[i(t_0) - \frac{V_{TH}}{R_{TH}} \right] = - \frac{R_{TH}}{L} (t_1 - t_0)$$

$$\Rightarrow \frac{i(t_1) - \frac{V_{TH}}{R_{TH}}}{i(t_0) - \frac{V_{TH}}{R_{TH}}} = e^{-\frac{R_{TH}}{L} (t_1 - t_0)}$$

$$\Rightarrow i(t_1) = \frac{V_{TH}}{R_{TH}} + \left[i(t_0) - \frac{V_{TH}}{R_{TH}} \right] \cdot e^{-\frac{R_{TH}}{L} (t_1 - t_0)}$$

$$f(t) = A_1 + B_1 \cdot e^{-\frac{(t-t_0)}{\uparrow}} \quad A_1 = \frac{V_{TH}}{R_{TH}} \quad B_1 = i(t_0) - \frac{V_{TH}}{R_{TH}}$$

$$\uparrow = \frac{L}{R_{TH}}$$

$$\text{Formula: } f(t) = A + B \cdot e^{-\frac{(t-t_0)}{\uparrow}}$$

$$(a) \quad t = t_0 \quad f(t_0) = A + B$$

$$\uparrow = \frac{L}{R_{TH}}$$


$$(b) \quad t = \infty \quad f(\infty) = A$$

For L the current i (can't jump) but u (can jump)

For C the current i (can jump) but u (can't jump)

RC circuit [Period Sin Input]

$$i_N = I_A \cos \omega t$$

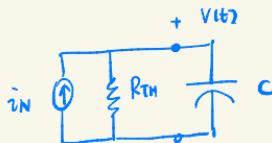

Based on formula.

$$\frac{dV(t)}{dt} + \frac{1}{R_M C} V(t) = \frac{I_A}{C} \cos \omega t$$

$$V(t) = Ae^{-t/\tau} + B \cos(\omega t + \theta) \quad \text{For } t \geq 0$$

$$\frac{dV(t)}{dt} = -\frac{A}{\tau} e^{-t/\tau} - B\omega \sin(\omega t + \theta)$$

$$\text{Therefore: } -\frac{A}{\tau} e^{-t/\tau} - B\omega \sin(\omega t + \theta) + \frac{1}{R_M C} \left[Ae^{-t/\tau} + B \cos(\omega t + \theta) \right] = \frac{I_A}{C} \cos \omega t$$

$$\text{Also } V(0) = A + B \cos \theta \quad \text{Form from trig \& math calculation.}$$

$$\theta = \tan^{-1}(-\omega \tau)$$

$$B = \frac{I_A}{c} \cdot \frac{\uparrow \frac{1}{\cos \theta}}{\omega^2 \tau^2 + 1}$$

$$A = V(0) - B \cos \theta = V_0 - \frac{I_A}{c} \cdot \frac{\uparrow}{\omega^2 \tau^2 + 1}$$

$$\Rightarrow V(t) = \underbrace{\left[V(0) - \frac{I_A}{c} \frac{\uparrow}{1 + \omega^2 \tau^2} \right]}_{\text{Natural response}} e^{-t/\tau} + \underbrace{\frac{I_A}{c} \frac{\uparrow}{\sqrt{1 + \omega^2 \tau^2}} \cos[\omega t - \tan^{-1}(\omega \tau)]}_{\text{forced response}}$$

Natural response

forced response.


RLC Circuit

$$i_R(\omega) = i_L(\omega) = i_C(\omega) = i(\omega)$$

$$= i_R(\omega) = i_C(\omega) = i(\omega)$$

$$V_C(\omega) = V_C(\omega) \quad V_R(\omega) = V_R(\omega) R_{TH}$$
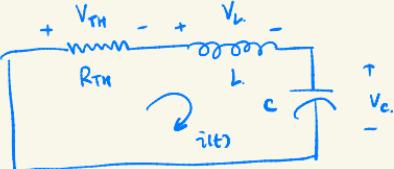
$$V_C(\omega) = -[i(\omega) \cdot R_{TH} + V_C(\omega)]$$



$$\therefore R_{TH} + L \cdot \frac{di}{dt} + V_C = 0 \quad \text{For } i_C = \frac{d\phi}{dt} = C \frac{dV}{dt} \Rightarrow i_C dt = C dV \Rightarrow V(t) = \frac{1}{C} \int_{t_0}^t i(x) dx + V(t_0)$$

$$\Rightarrow i \cdot R_{TH} + L \cdot \frac{di}{dt} + \frac{1}{C} \int_0^t i(x) dx + V_C(0) = 0 \quad \xrightarrow{\text{Differential from both sides.}}$$

$$\Rightarrow R_{TH} \cdot \frac{di}{dt} + L \cdot \frac{d^2i}{dt^2} + \frac{1}{C} \cdot i = 0 \quad \Rightarrow \boxed{\frac{d^2i}{dt^2} + \frac{R_{TH}}{L} \cdot \frac{di}{dt} + \frac{1}{LC} \cdot i = 0}$$

$$s^2 + \frac{R}{L} \cdot s + \frac{1}{LC} = 0 \quad \Delta = \frac{R^2}{L^2} - 4 \cdot \frac{1}{LC} = \frac{R^2 C^2 - 4LC}{L^2 C^2}$$

$$\textcircled{1} \quad \Delta > 0 \quad R^2 C^2 - 4LC > 0 \Rightarrow R^2 > 4 \frac{L}{C} \quad \text{Overdamped.} \quad S_1, S_2$$

$$\textcircled{2} \quad \Delta = 0 \quad R^2 C^2 - 4LC = 0 \Rightarrow R^2 = 4 \frac{L}{C} \quad \text{Critically damped.} \quad S_1$$

$$\textcircled{3} \quad \Delta < 0 \quad R^2 C^2 - 4LC < 0 \Rightarrow R^2 < 4 \frac{L}{C} \quad \text{Underdamped.}$$

$$\alpha_0 = \frac{R_{TH}}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

For Current $i(t)$

$$\text{Overdamped.} \quad i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$\text{Critically damped} \quad i(t) = (A_1 + A_2 t) e^{-\alpha t}$$

$$\text{Underdamped.} \quad i(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$$

$$\text{where } \alpha = \frac{R}{2L} \quad \omega_d = \sqrt{\frac{1}{LC} - \alpha^2} = \sqrt{\omega_0^2 - \alpha^2}$$

RCL Circuit Key points

$$\text{Equation: } \frac{d^2i}{dt^2} + \frac{R_{TH}}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

① $\alpha^2 > \omega_0^2$. Overdamped $S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$ $S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$

$$\alpha = \frac{R_{TH}}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t} \quad i(0) = A_1 + A_2 \quad ①$$

$$\frac{di(t)}{dt} = A_1 S_1 e^{S_1 t} + A_2 S_2 e^{S_2 t} \quad \frac{d^2i(t)}{dt^2} = A_1 S_1 S_2 e^{S_1 t} + A_2 S_2 S_1 e^{S_2 t} \quad ②$$

$$\text{Also } \frac{d^2i(t)}{dt^2} = \frac{V_L(t)}{L} = \frac{1}{L} \left[-V_{R_{TH}}(t) - V_C(t) \right]$$

Based on those two equation find A_1 & A_2

For $V_C(t)$ ① method 1. $V_C(t) = \frac{1}{C} \int_0^t i_C(t) dt + V_C(0^-)$

② method 2 $V_R(t) + V_L(t) + V_C(t) = 0 \rightarrow V_C(t) = -i(t) R - L \cdot \frac{di(t)}{dt}$

② $\alpha^2 = \omega_0^2$. Critically damped. $S_1 = S_2 = -\alpha = -\frac{R_{TH}}{2L}$

$$i(t) = (A_1 t + A_2) e^{-\alpha t} \quad i(0) = A_2$$

$$\frac{di(t)}{dt} = A_1 e^{-\alpha t} + (A_1 t + A_2)(-\alpha) e^{-\alpha t} \quad \frac{d^2i(t)}{dt^2} = (A_1 - \alpha A_2) e^{-\alpha t} = \frac{V_L(t)}{L} = \frac{1}{L} \left[-i(t) R_{TH} - V_C(t) \right]$$

③ $\alpha^2 < \omega_0^2$ $S_1 = -\alpha + j\omega_d = -\alpha + \sqrt{(-1)(\omega_0^2 - \alpha^2)} = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} = -\alpha + j\omega_d$

Same. $S_2 = -\alpha - j\omega_d$. where $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

$$i(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) = C_1 e^{-\alpha t} \cos(\omega_d t + \theta)$$

$$\frac{di(t)}{dt} = [C_1(-\alpha) e^{-\alpha t} \cos(\omega_d t + \theta) + C_1 e^{-\alpha t} \omega_d \sin(\omega_d t + \theta)]$$

$$i(0) = C_1 \cos \theta \quad ①$$

$$\frac{d^2i(t)}{dt^2} = -2C_1 \cos \theta - C_1 \omega_d \sin \theta = \frac{V_L(t)}{L} = \frac{1}{L} \left[-i(t) R_{TH} - V_C(t) \right] \quad ②$$